

PHYS 1441 – Section 001

Lecture #23

Monday, Dec. 4, 2017

Dr. Jaehoon Yu

- Chapter 30: Inductance
 - Mutual and Self Inductance
 - Energy Stored in Magnetic Field
 - Alternating Current and AC Circuits
 - AC Circuit W/ LRC
- Chapter 31: Maxwell's Equations
 - Expansion of Ampere's Law



Announcements

- Reading Assignments
 - CH30.10 and CH30.11
- Final exam
 - Date and time: 11am – 12:30pm, Monday, Dec. 11 in SH101
 - Comprehensive exam: covers CH21.1 through what we finish this Wednesday, Dec. 6
 - Bring your calculator but DO NOT input formula into it!
 - Cell phones or any types of computers cannot replace a calculator!
 - BYOF: You may bring a one 8.5x11.5 sheet (front and back) of **handwritten** formulae and values of constants
 - No derivations, word definitions or solutions of any kind!
 - No additional formulae or values of constants will be provided!




Inductance

- Changing magnetic flux through a circuit induce an emf in that circuit
- An electric current produces a magnetic field
- From these, we can deduce
 - A changing current in one circuit must induce an emf in a nearby circuit → Mutual inductance
 - Or induce an emf in itself → Self inductance



Mutual Inductance

- If two coils of wire are placed near each other, a changing current in one will induce an emf in the other.
- What is the induced emf, ε_2 , in coil2 proportional to?
 - Rate of the change of the magnetic flux passing through it
- This flux is due to current I_1 in coil 1
- If Φ_{21} is the magnetic flux in each loop of coil2 created by coil1 and N_2 is the number of closely packed loops in coil2, then $N_2\Phi_{21}$ is the total flux passing through coil2.
- If the two coils are fixed in space, $N_2\Phi_{21}$ is proportional to the current I_1 in coil 1, $N_2\Phi_{21} = M_{21} I_1$.
- The proportionality constant for this is called the Mutual Inductance and defined as $M_{21} = N_2\Phi_{21}/I_1$.
- The emf induced in coil2 due to the changing current in coil1 is

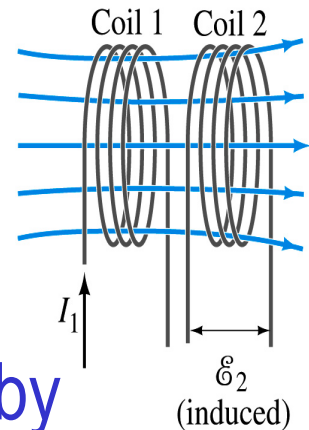

$$\varepsilon_2 = -N_2 \frac{d\Phi_{21}}{dt} = -\frac{d(N_2\Phi_{21})}{dt} = -M_{21} \frac{dI_1}{dt}$$



Mutual Inductance

- The mutual induction of coil2 with respect to coil1, M_{21} ,
 - is a constant and does not depend on I_1 .
 - depends only on “geometric” factors such as the size, shape, number of turns and relative position of the two coils, and whether a ferromagnetic material is present


What? Does this make sense?

 - The farther apart the two coils are the less flux can pass through coil, 2, so M_{21} will be less.
 - In most cases the mutual inductance is determined experimentally
 - Conversely, the changing current in coil2 will induce an emf in coil1
 - $\varepsilon_1 = -M_{12} \frac{dI_2}{dt}$
 - M_{12} is the mutual inductance of coil1 with respect to coil2 and $M_{12} = M_{21}$
 - We can put $M = M_{12} = M_{21}$ and obtain
 - SI unit for mutual inductance is henry (H)
- $\varepsilon_1 = -M \frac{dI_2}{dt}$ and $\varepsilon_2 = -M \frac{dI_1}{dt}$
- $1H = 1V \cdot s / A = 1\Omega \cdot s$



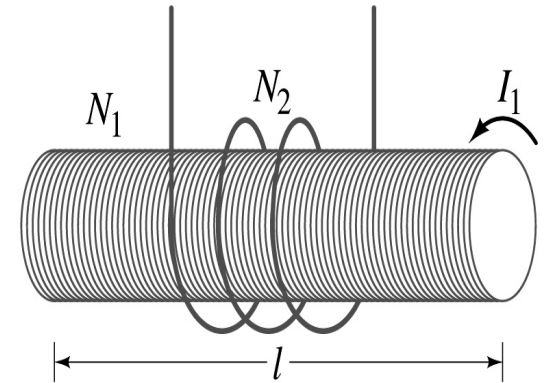Example 30 – 1

Solenoid and coil. A long thin solenoid of length l and cross-sectional area A contains N_1 closely packed turns of wire. Wrapped around it is an insulated coil of N_2 turns. Assuming all the flux from coil 1 (the solenoid) passes through coil 2, calculate the mutual inductance.



First we need to determine the flux produced by the solenoid.

What is the magnetic field inside the solenoid? $B = \frac{\mu_0 N_1 I_1}{l}$

Since the solenoid is closely packed, we can assume that the field lines are perpendicular to the surface area of the coils. Thus the flux through coil 2 is

$$\Phi_{21} = BA = \frac{\mu_0 N_1 I_1}{l} A$$

Thus the mutual inductance of coil 2 is $M_{21} = \frac{N_2 \Phi_{21}}{I_1} = \frac{N_2}{I_1} \frac{\mu_0 N_1 I_1}{l} A = \frac{\mu_0 N_1 N_2}{l} A$

Self Inductance

- The concept of inductance applies to a single isolated coil of N turns. How does this happen?
 - When a changing current passes through a coil
 - A changing magnetic flux is produced inside the coil
 - The changing magnetic flux in turn induces an emf in the same coil
 - This emf opposes the change in flux. Whose law is this?
 - Lenz's law
- What would this do?
 - When the current through the coil is increasing?
 - The increasing magnetic flux induces an emf that opposes the original current
 - This tends to impede its increase, trying to maintain the original current
 - When the current through the coil is decreasing?
 - The decreasing flux induces an emf in the same direction as the current
 - This tends to increase the flux, trying to maintain the original current



Self Inductance

- Since the magnetic flux Φ_B passing through N turn coil is proportional to current I in the coil, $N\Phi_B = LI$
- We define self-inductance, $\mathcal{L}$:

$$L = \frac{N\Phi_B}{I}$$

Self Inductance
- The induced emf in a coil of self-inductance $\mathcal{L}$ is
 - $\varepsilon = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$
 - What is the unit for self-inductance? $1H = 1V \cdot s/A = 1\Omega \cdot s$
- What does magnitude of $\mathcal{L}$ depend on?
 - Geometry and the presence of a ferromagnetic material
- Self inductance can be defined for any circuit or part of a circuit



So what in the world is the Inductance?

- It is an impediment onto the electrical current due to the existence of changing flux
- So what?
- In other words, it behaves like a resistance to the varying current, such as AC, that causes the constant change of flux
- But it also provides means to store energy, just like the capacitance



Self Inductance

- The concept of inductance applies to a single isolated coil of N turns. How does this happen?
 - When a changing current passes through a coil
 - A changing magnetic flux is produced inside the coil
 - The changing magnetic flux in turn induces an emf in the same coil
 - This emf opposes the change in flux. Whose law is this?
 - Lenz's law
- What would this do?
 - When the current through the coil is increasing?
 - The increasing magnetic flux induces an emf that opposes the original current
 - This tends to impede its increase, trying to maintain the original current
 - When the current through the coil is decreasing?
 - The decreasing flux induces an emf in the same direction as the current
 - This tends to increase the flux, trying to maintain the original current



Self Inductance

- Since the magnetic flux Φ_B passing through N turn coil is proportional to current I in the coil, $N\Phi_B = LI$
- We define self-inductance, $\mathcal{L}$:

$$L = \frac{N\Phi_B}{I}$$

Self Inductance
- The induced emf in a coil of self-inductance $\mathcal{L}$ is
 - $\varepsilon = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$
 - What is the unit for self-inductance? $1H = 1V \cdot s/A = 1\Omega \cdot s$
- What does magnitude of $\mathcal{L}$ depend on?
 - Geometry and the presence of a ferromagnetic material
- Self inductance can be defined for any circuit or part of a circuit



So what in the world is the Inductance?

- It is an impediment onto the electrical current due to the existence of changing flux
- So what?
- In other words, it behaves like a resistance to the varying current, such as AC, that causes the constant change of flux
- But it also provides means to store energy, just like the capacitance



Inductor

- An electrical circuit always contains some inductance but is normally negligibly small
 - If a circuit contains a coil of many turns, it could have large inductance
- A coil that has significant inductance, $\mathcal{L}$, is called an inductor and is express with the symbol 
 - Precision resistors are normally wire wound
 - Would have both resistance and inductance
 - The inductance can be minimized by winding the wire back on itself in opposite direction to cancel magnetic flux
 - This is called a “non-inductive winding”
- If an inductor has negligible resistance, inductance controls the changing current
- For an AC current, the greater the inductance the less the AC current
 - An inductor thus acts like a resistor to impede the flow of alternating current (not to DC, though. Why?)
 - The quality of an inductor is indicated by the term reactance or impedance



Example 30 – 3

Solenoid inductance. (a) Determine the formula for the self inductance $\mathcal{L}$ of a tightly wrapped solenoid (a long coil) containing N turns of wire in its length l and whose cross-sectional area is A . (b) Calculate the value of $\mathcal{L}$ if $N=100$, $l=5.0\text{cm}$, $A=0.30\text{cm}^2$ and the solenoid is air filled. (c) calculate $\mathcal{L}$ if the solenoid has an iron core with $\mu=4000\mu_0$.

What is the magnetic field inside a solenoid? $B = \mu_0 nI = \mu_0 NI / l$

The flux is, therefore, $\Phi_B = BA = \mu_0 NIA / l$

Using the formula for self inductance: $L = \frac{N\Phi_B}{I} = \frac{N \cdot \mu_0 NIA / l}{I} = \frac{\mu_0 N^2 A}{l}$

(b) Using the formula above

$$L = \frac{\mu_0 N^2 A}{l} = \frac{(4\pi \times 10^{-7} \text{ T} \cdot \text{m/A}) 100^2 (0.30 \times 10^{-4} \text{ m}^2)}{5.0 \times 10^{-2} \text{ m}} = 7.5 \mu\text{H}$$

(c) The magnetic field with an iron core solenoid is $B = \mu NI / l$

$$L = \frac{\mu N^2 A}{l} = \frac{4000 (4\pi \times 10^{-7} \text{ T} \cdot \text{m/A}) 100^2 (0.30 \times 10^{-4} \text{ m}^2)}{5.0 \times 10^{-2} \text{ m}} = 0.030 \text{ H} = 30 \text{ mH}$$



Energy Stored in the Magnetic Field

- When an inductor of inductance $\mathcal{L}$ is carrying current I which is changing at a rate dI/dt , energy is supplied to the inductor at a rate
 - $P = I\varepsilon = IL \frac{dI}{dt}$
- What is the work needed to increase the current in an inductor from 0 to I ?
 - The work, dW , done in time dt is $dW = Pdt = LI dI$
 - Thus the total work needed to bring the current from 0 to I in an inductor is

$$W = \int dW = \int_0^I LI dI = L \left[\frac{1}{2} I^2 \right]_0^I = \frac{1}{2} LI^2$$



Energy Stored in the Magnetic Field

- The work done to the system is the same as the energy stored in the inductor when it is carrying current I

- $$U = \frac{1}{2} LI^2$$

Energy Stored in a magnetic field inside an inductor

- This is compared to the energy stored in a capacitor, C , when the potential difference across it is V : $U = \frac{1}{2} CV^2$
- Just like the energy stored in a capacitor is considered to reside in the electric field between its plates
- The energy in an inductor can be considered to be stored in its magnetic field



Stored Energy in terms of B

- So how is the stored energy written in terms of magnetic field B?

- Inductance of an ideal solenoid without a fringe effect

$$L = \mu_0 N^2 A / l$$

- The magnetic field in a solenoid is $B = \mu_0 NI / l$

- Thus the energy stored in an inductor is

$$U = \frac{1}{2} LI^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{l} \left(\frac{Bl}{\mu_0 N} \right)^2 = \frac{1}{2} \frac{B^2}{\mu_0} \underbrace{Al}$$

$$U = \frac{1}{2} \frac{B^2}{\mu_0} Al \quad \text{E}$$

- Thus the energy density is

$$u = \frac{U}{V} = \frac{U}{Al} = \frac{1}{2} \frac{B^2}{\mu_0}$$

What is this?

Volume V

$$u = \frac{1}{2} \frac{B^2}{\mu_0} \quad \text{E density}$$

- This formula is valid in any region of space
- If a ferromagnetic material is present, μ_0 becomes μ .


What volume does Al represent?

The volume inside a solenoid!!



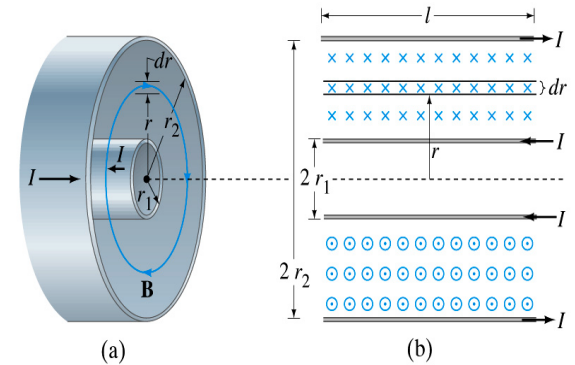Example 30 – 5

Energy stored in a coaxial cable. (a) How much energy is being stored per unit length in a coaxial cable whose conductors have radii r_1 and r_2 and which carry a current I ? (b) Where is the energy density highest?



(a) The total flux through l of the cable is $\Phi_B = \int B l dr = \frac{\mu_0 I l}{2\pi} \int_{r_1}^{r_2} \frac{dr}{r} = \frac{\mu_0 I l}{2\pi} \ln \frac{r_2}{r_1}$

Thus inductance per unit length for a coaxial cable is $\frac{L}{l} = \frac{\mu_0}{2\pi} \ln \frac{r_2}{r_1}$

Thus the energy stored per unit length is

$$\frac{U}{l} = \frac{1}{2} \frac{L I^2}{l} = \frac{\mu_0 I^2}{4\pi} \ln \frac{r_2}{r_1}$$


(b) Since the magnetic field is $B = \frac{\mu_0 I}{2\pi r}$

And the energy density is $u = \frac{1}{2} \frac{B^2}{\mu_0}$

The energy density is highest where B is highest. Since B is highest close to $r=r_1$, near the surface of the inner conductor.

LR Circuits

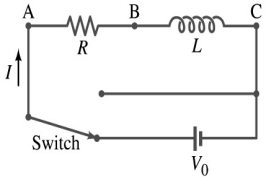
- What happens when an emf is applied to an inductor?
 - An inductor has some resistance, however negligible




- So an inductor can be drawn as a circuit of separate resistance and coil. What is the name this kind of circuit? **LR Circuit**

- What happens at the instance the switch is thrown to apply emf to the circuit?

- The current starts to flow, gradually increasing from 0
- This change is opposed by the induced emf in the inductor → the emf at point B is higher than point C
- However there is a voltage drop at the resistance which reduces the voltage across inductance
- Thus the current increases less rapidly
- The overall behavior of the current is a gradual increase, reaching to the maximum current $I_{\max} = V_0/R$.

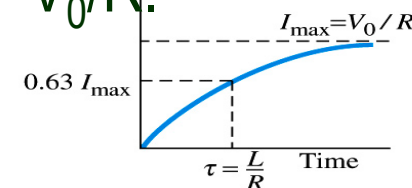

LR Circuits

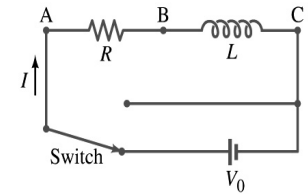

- This can be shown w/ Kirchhoff loop rules

- The emfs in the circuit are the battery voltage V_0 and the emf $\varepsilon = -\mathcal{L}(dI/dt)$ in the inductor opposing the current increase

- The sum of the potential changes through the circuit is

$$V_0 + \varepsilon - IR = V_0 - L dI/dt - IR = 0$$

- Where I is the current at any instance


- By rearranging the terms, we obtain a differential eq.

- $L dI/dt + IR = V_0$

- We can integrate just as in RC circuit

- So the solution is $-\frac{1}{R} \ln\left(\frac{V_0 - IR}{V_0}\right) = \frac{t}{L}$

- Where $\tau = L/R$

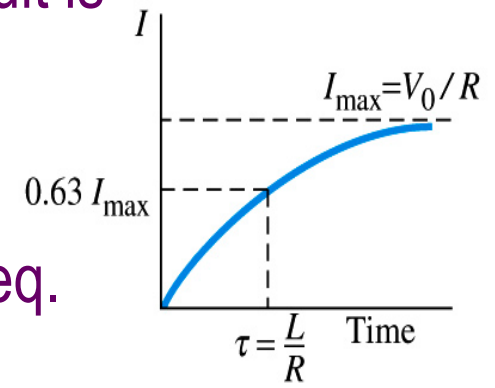


$$\int_{I=0}^I \frac{dI}{V_0 - IR} = \int_{t=0}^t \frac{dt}{L}$$

$$I = V_0 (1 - e^{-t/\tau}) / R = I_{\max} (1 - e^{-t/\tau})$$

- This is the time constant τ of the LR circuit and is the time required for the current I to reach 0.63 of the maximum

Discharge of LR Circuits

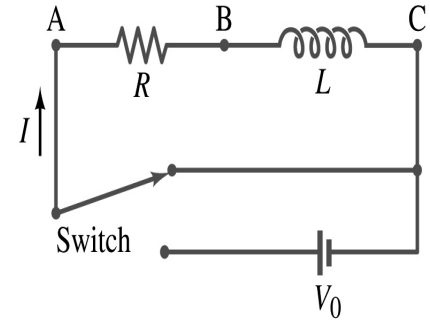
- If the switch is flipped away from the battery



- The differential equation becomes

- $L \frac{dI}{dt} + IR = 0$

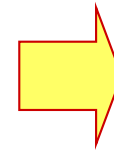
- So the integration is $\int_{I_0}^I \frac{dI}{IR} = \int_{t=0}^t \frac{dt}{L}$



$$\ln \frac{I}{I_0} = -\frac{R}{L} t$$

- Which results in the solution

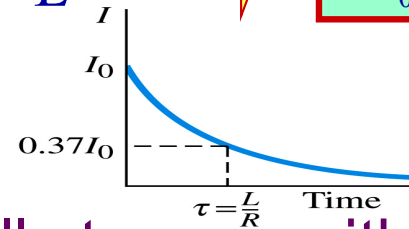
- $I = I_0 e^{-\frac{R}{L} t} = I_0 e^{-t/\tau}$



- The current decays exponentially to zero with the time constant $\tau = L/R$
- So there always is a reaction time when a system with a coil, such as an electromagnet, is turned on or off.
- The current in LR circuit behaves almost the same as that in RC circuit but the time constant is inversely proportional to R in LR circuit unlike the RC circuit

AC Circuit w/ Resistance only

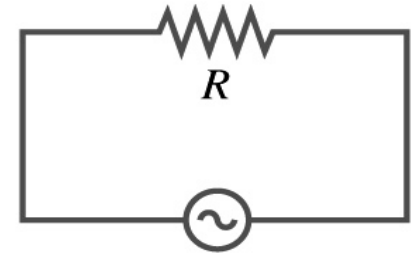- What do you think will happen when an AC source is connected to a resistor?
- From Kirchhoff's loop rule, we obtain




- Thus $V - IR = 0$

$$V = I_0 R \sin \omega t = V_0 \sin \omega t$$

– where $V_0 = I_0 R$

- What does this mean?

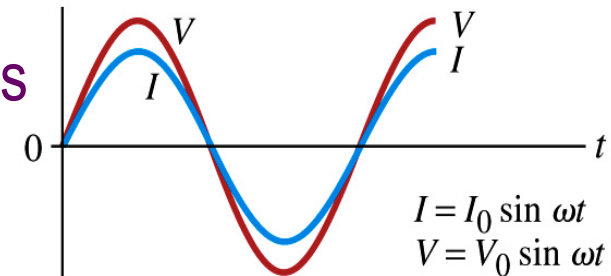- Current is 0 when voltage is 0 and current is in its peak when voltage is in its peak.
- Current and voltage are “in phase”



- Energy is lost via the transformation into heat at an average rate

$$\bar{P} = \bar{I} \bar{V} = I_{rms}^2 R = V_{rms}^2 / R$$

AC Circuit w/ Inductance only

- From Kirchhoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus



$$V = L \frac{dI}{dt} = L \frac{d(I_0 \sin \omega t)}{dt} = \omega L I_0 \cos \omega t$$

- Using the identity $\cos \theta = \sin(\theta + 90^\circ)$
- $V = \omega L I_0 \sin(\omega t + 90^\circ) = V_0 \sin(\omega t + 90^\circ)$
 - where $V_0 = \omega L I_0$
- What does this mean?

- Current and voltage are “out of phase by $\pi/2$ or 90° ”. In other words the current reaches its peak $1/4$ cycle after the voltage

- What happens to the energy?

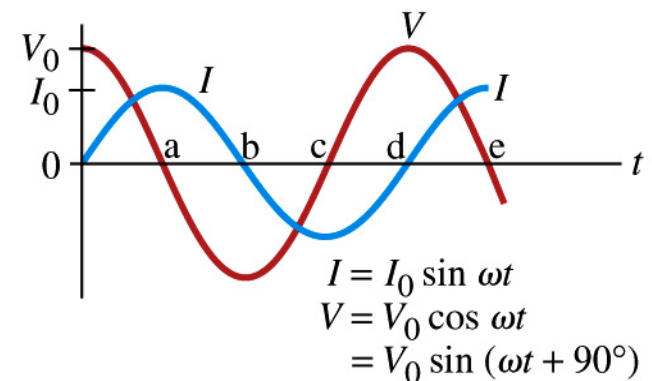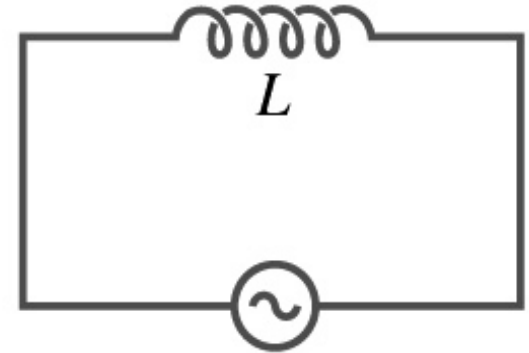- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the magnetic field
- Then released back to the source



AC Circuit w/ Inductance only

- How are the resistor and inductor different in terms of energy?
 - Inductor Stores the energy temporarily in the magnetic field and then releases it back to the emf source
 - Resistor Does not store energy but transforms it to thermal energy, losing it to the environment
- How are they the same?
 - They both impede the flow of charge
 - For a resistance R, the peak voltage and current are related to $V_0 = I_0 R$
 - Similarly, for an inductor we may write $V_0 = I_0 X_L$
 - Where X_L is the inductive reactance of the inductor $X_L = \omega L$ 0 when $\omega=0$.
 - What do you think is the unit of the reactance? Ω
 - The relationship $V_0 = I_0 X_L$ is not valid at a particular instance. Why not?
 - Since V_0 and I_0 do not occur at the same time



$$V_{rms} = I_{rms} X_L$$

is valid! 24

Example 30 – 9

Reactance of a coil. A coil has a resistance $R=1.00\Omega$ and an inductance of $0.300H$. Determine the current in the coil if (a) 120 V DC is applied to it; (b) 120 V AC (rms) at 60.0Hz is applied.

Is there a reactance for DC? Nope. Why not? Since $X_L = \omega L = 0$

So for DC power, the current is from Kirchhoff's rule ^{$\omega=0$} , $V - IR = 0$

$$I_0 = \frac{V_0}{R} = \frac{120V}{1.00\Omega} = 120A$$

For an AC power with $f=60\text{Hz}$, the reactance is

$$X_L = \omega L = 2\pi fL = 2\pi \cdot (60.0s^{-1}) \cdot 0.300H = 113\Omega$$


Since the resistance can be ignored compared to the reactance, the rms current is

$$I_{rms} \approx \frac{V_{rms}}{X_L} = \frac{120V}{113\Omega} = 1.06A$$



AC Circuit w/ Capacitance only

- What happens when a capacitor is connected to a DC power source?
 - The capacitor quickly charges up.
 - There is no steady current flow in the circuit
 - Since the capacitor prevents the flow of the DC current
- What do you think will happen if it is connected to an AC power source?
 - The current flows continuously. Why?
 - When the AC power turns on, charge begins to flow one direction, charging up the plates
 - When the direction of the power reverses, the charge flows in the opposite direction

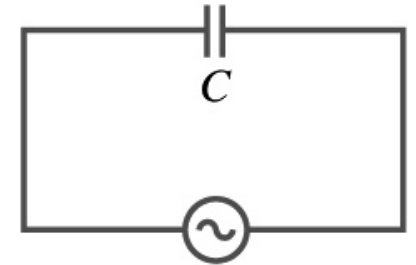


AC Circuit w/ Capacitance only

- From Kirchhoff's loop rule, we obtain

$$V = \frac{Q}{C}$$

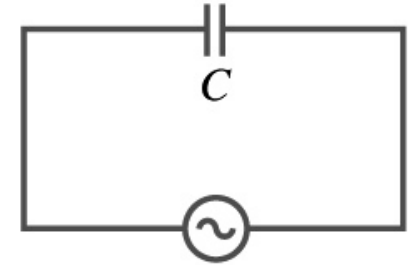- The current at any instance is $I = \frac{dQ}{dt} = I_0 \sin \omega t$



- The charge Q on the plate at any instance is

$$Q = \int_{Q=0}^Q dQ = \int_{t=0}^t I_0 \sin \omega t dt = -\frac{I_0}{\omega} \cos \omega t$$

- Thus the voltage across the capacitor is

$$V = \frac{Q}{C} = -I_0 \frac{1}{\omega C} \cos \omega t$$

- Using the identity $\cos \theta = -\sin(\theta - 90^\circ)$

$$V = I_0 \frac{1}{\omega C} \sin(\omega t - 90^\circ) = V_0 \sin(\omega t - 90^\circ)$$

- Where

- $V_0 = \frac{I_0}{\omega C}$




AC Circuit w/ Capacitance only

- So the voltage is $V = V_0 \sin(\omega t - 90^\circ)$
- What does this mean?
 - Current and voltage are “out of phase by $\pi/2$ or 90° ” but in this case, the voltage reaches its peak $1/4$ cycle after the current

- What happens to the energy?

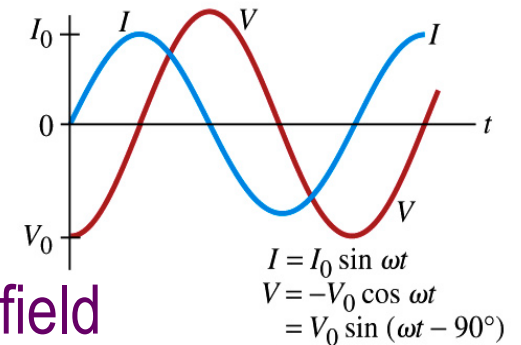- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the electric field
- Then released back to the source



- Applied voltage and the current in the capacitor can be written as $V_0 = I_0 X_C$

- Where the capacitive reactance X_C is defined as
- Again, this relationship is only valid for rms quantities

$$X_C = \frac{1}{\omega C}$$


Infinite
when
 $\omega=0$.



$$V_{rms} = I_{rms} X_C$$

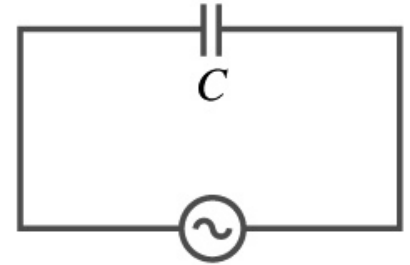Example 30 – 10

Capacitor reactance. What are the peak and rms current in the circuit in the figure if $C=1.0\mu\text{F}$ and $V_{\text{rms}}=120\text{V}$? Calculate for (a) $f=60\text{Hz}$, and then for (b) $f=6.0\times 10^5\text{Hz}$.



The peak voltage is $V_0 = \sqrt{2}V_{\text{rms}} = 120\text{V} \cdot \sqrt{2} = 170\text{V}$

The capacitance reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot (60\text{s}^{-1}) \cdot 1.0 \times 10^{-6}\text{F}} = 2.7\text{k}\Omega$$

Thus the peak current is


$$I_0 = \frac{V_0}{X_C} = \frac{170\text{V}}{2.7\text{k}\Omega} = 63\text{mA}$$

The rms current is

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120\text{V}}{2.7\text{k}\Omega} = 44\text{mA}$$


AC Circuit w/ LRC

- The voltage across each element is
 - V_R is in phase with the current
 - V_L leads the current by 90°
 - V_C lags the current by 90°
- From Kirchhoff's loop rule
- $V = V_R + V_L + V_C$
 - However since they do not reach the peak voltage at the same time, the peak voltage of the source V_0 will not equal $V_{R0} + V_{L0} + V_{C0}$
 - The rms voltage also will not be the simple sum of the three
- Let's try to find the total impedance, peak current I_0 and the phase difference between I_0 and V_0 .

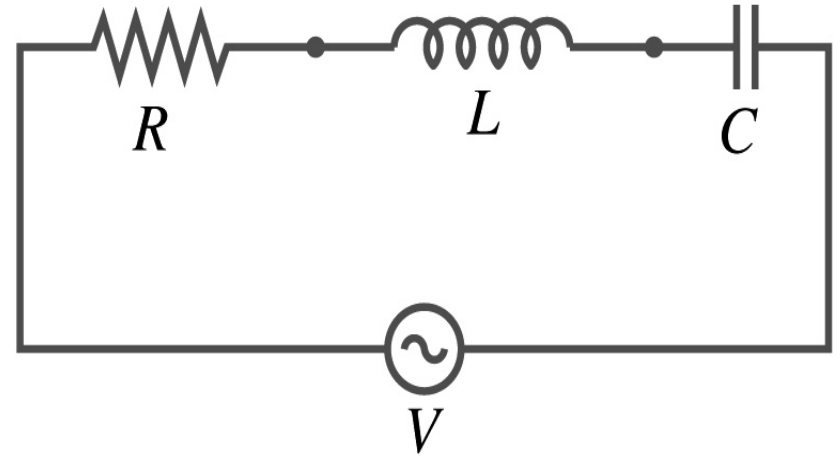

AC Circuit w/ LRC

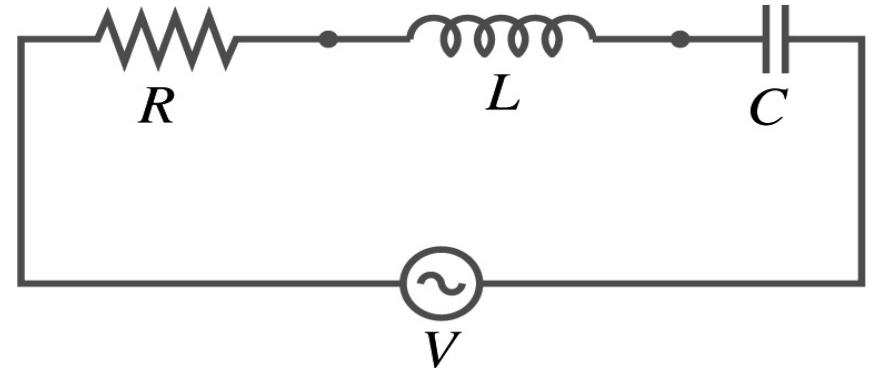- The current at any instance is the same at all point in the circuit
 - The currents in each elements are in phase
 - Why?
 - Since the elements are in series
 - How about the voltage?
 - They are not in phase.





- The current at any given time is

$$I = I_0 \sin \omega t$$

- The analysis of LRC circuit is done using the “phasor” diagram in which arrows are drawn in an xy plane to represent the amplitude of each voltage, just like vectors
 - The lengths of the arrows represent the magnitudes of the peak voltages across each element; $V_{R0} = I_0 R$, $V_{L0} = I_0 X_L$ and $V_{C0} = I_0 X_C$
 - The angle of each arrow represents the phase of each voltage relative to the current, and the arrows rotate at the angular frequency ω to take into account the time dependence.
 - The projection of each arrow on y axis represents voltage across each element at any given time

Phasor Diagrams

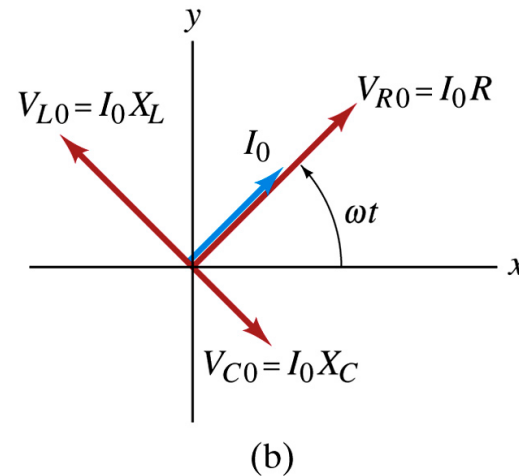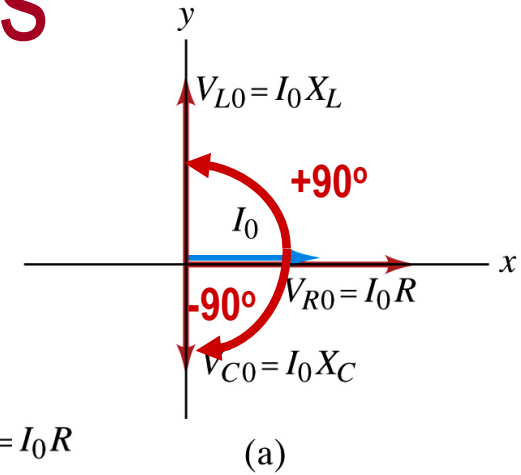- At $t=0$, $I=0$.
 - Thus $V_{R0}=0$, $V_{L0}=I_0X_L$, $V_{C0}=I_0X_C$
- At $t=t$, $I = I_0 \sin \omega t$




- Thus, the voltages (y-projections) are

$$V_R = V_{R0} \sin \omega t$$

$$V_L = V_{L0} \sin(\omega t + 90^\circ)$$

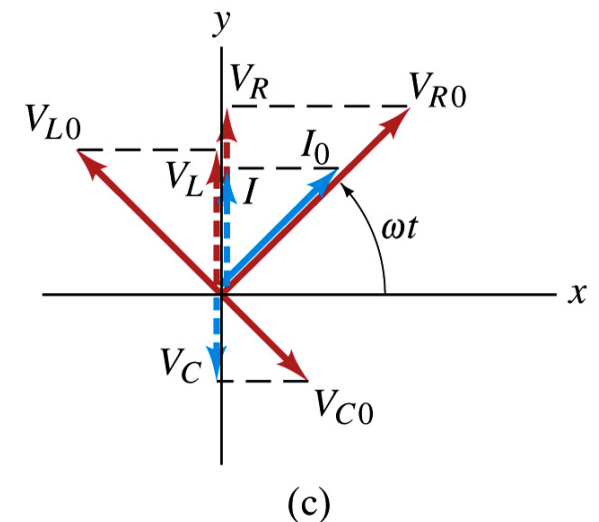
$$V_C = V_{C0} \sin(\omega t - 90^\circ)$$



AC Circuit w/ LRC

- Since the sum of the projections of the three vectors on the y axis is equal to the projection of their sum.

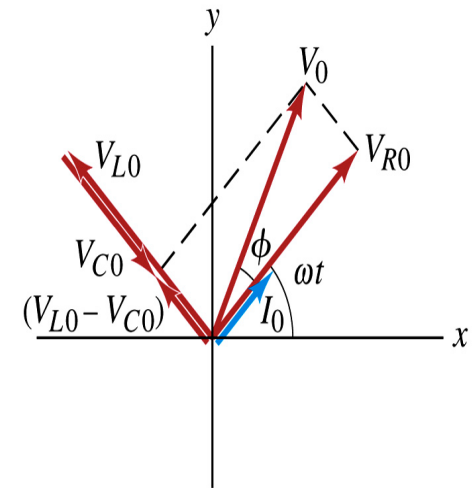- The sum of the projections represents the instantaneous voltage across the whole circuit which is the source voltage
- So we can use the sum of all vectors as the representation of the peak source voltage V_0 .



- V_0 forms an angle ϕ to V_{R0} and rotates together with the other vectors as a function of time, $V = V_0 \sin(\omega t + \phi)$
- We determine the total impedance Z of the circuit defined by the relationship $V_{rms} = I_{rms} Z$ or $V_0 = I_0 Z$
- From Pythagorean theorem, we obtain

$$V_0 = \sqrt{V_{R0}^2 + (V_{L0} - V_{C0})^2} = \sqrt{I_0^2 R^2 + I_0^2 (X_L - X_C)^2} = I_0 \sqrt{R^2 + (X_L - X_C)^2} = I_0 Z$$

- Thus the total impedance is $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$



AC Circuit w/ LRC

- The phase angle ϕ is

$$\tan \phi = \frac{V_{L0} - V_{C0}}{V_{R0}} = \frac{I_0 (X_L - X_C)}{I_0 R} = \frac{(X_L - X_C)}{R}$$

- or

$$\cos \phi = \frac{V_{R0}}{V_0} = \frac{I_0 R}{I_0 Z} = \frac{R}{Z}$$

- What is the power dissipated in the circuit?

- Which element dissipates the power?
- Only the resistor

- The average power is $\bar{P} = I_{rms}^2 R$

- Since $R = Z \cos \phi$

- We obtain

$$\bar{P} = I_{rms}^2 Z \cos \phi = I_{rms} V_{rms} \cos \phi$$

- The factor $\cos \phi$ is referred as the power factor of the circuit

- For a pure resistor, $\cos \phi = 1$ and $\bar{P} = I_{rms} V_{rms}$

- For a capacitor or inductor alone $\phi = -90^\circ$ or $+90^\circ$, so $\cos \phi = 0$ and $\bar{P} = 0$.

