

PHYS 1441 – Section 002

Lecture #10

Monday, Oct. 8, 2018

*Dr. **Jaehoon** Yu*

- Chapter 24 Capacitance etc..
 - Capacitors in Series or Parallel
 - Electric Energy Storage
 - Effect of Dielectric
 - Molecular description of Dielectric Material
- Chapter 25
 - Electric Current and Resistance

Today's homework is #7, due 11pm, Monday, Oct. 15!!





Announcements

- Quiz 2 results
 - Class average: 33/60
 - Equivalent to 55/100
 - Previous quiz: 74/100
 - Top score: 62/60
- Mid Term Exam
 - In class Wednesday, Oct. 17
 - Covers CH21.1 through what we cover in class Monday, Oct. 15 + appendix
 - Bring your calculator but DO NOT input formula into it!
 - Cell phones or any types of computers cannot replace a calculator!
 - BYOF: You may bring a one 8.5x11.5 sheet (front and back) of handwritten formulae and values of constants
 - No derivations, word definitions or solutions of any kind!
 - No additional formulae or values of constants will be provided!



Capacitors in Series or Parallel

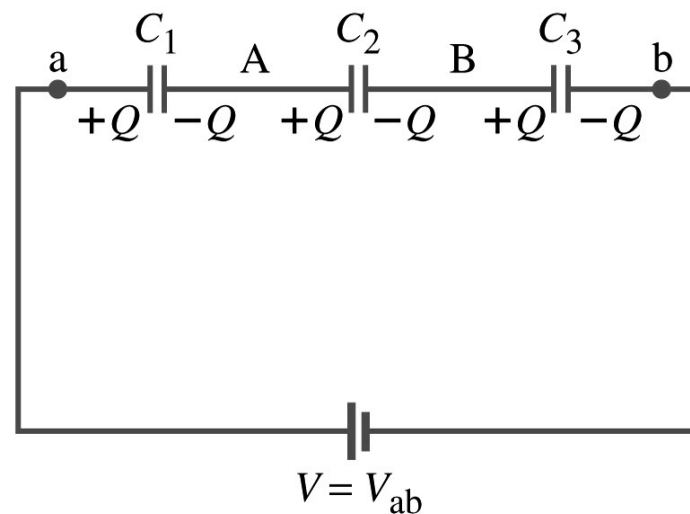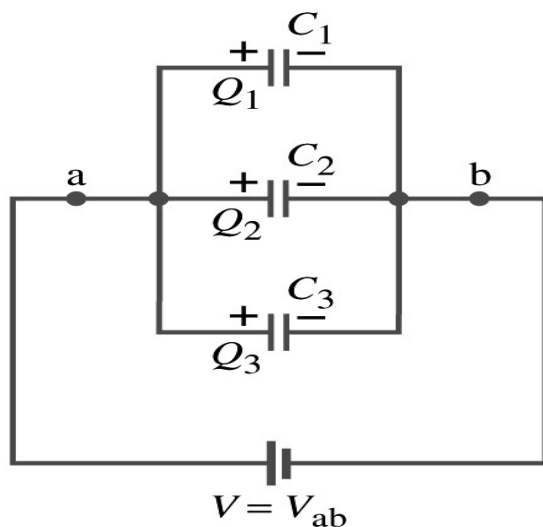- Capacitors may be used in electric circuits
- What is an electric circuit?
 - A closed path of conductors, usually wires connecting capacitors and other electrical devices, in which
 - Charges can flow
 - And includes a voltage source such as a battery
- Capacitors can be connected in various ways.
 - In parallel, in series or in combination




Capacitors in Parallel

- Parallel arrangement provides the same voltage across all the capacitors.

- Left hand plates are at V_a and right hand plates are at V_b
- So each capacitor plate acquires charges given by the formula

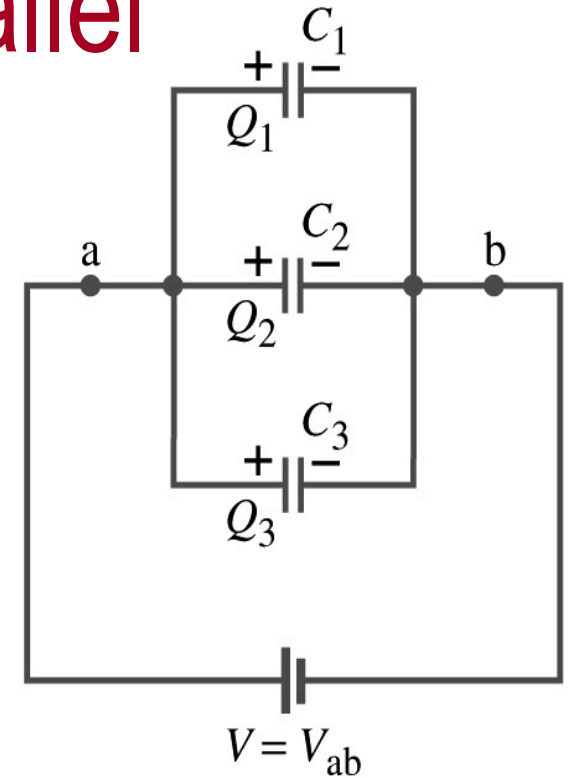- $Q_1 = C_1 V$, $Q_2 = C_2 V$, and $Q_3 = C_3 V$



- The total charge Q that must leave the battery is then
 - $Q = Q_1 + Q_2 + Q_3 = V(C_1 + C_2 + C_3)$
- Consider that the three capacitors behave like an equivalent one
 - $Q = C_{eq} V = V(C_1 + C_2 + C_3)$
- Thus the equivalent capacitance in parallel is $C_{eq} = C_1 + C_2 + C_3$

M

What is the net effect?


F

The capacitance increases!!!

Capacitors in Series

- Series arrangement is more interesting

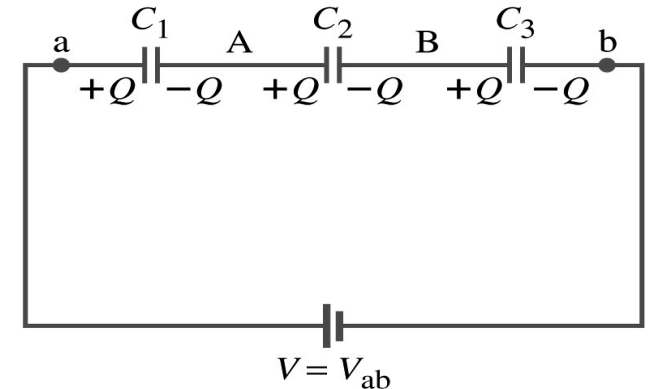- When battery is connected, $+Q$ flows to the left plate of C_1 and $-Q$ flows to the right plate of C_3 .
- Since capacitors in between were originally neutral, charges get induced to neutralize the ones in the middle.
- So the charge on each capacitor plate is the same value, Q . (**Same charge**)



- Consider that the three capacitors behave like an equivalent one

- $Q = C_{eq} V$

- The total voltage V across the system of three capacitors in series must be equal to the sum of the voltages across each capacitor.

- $V = V_1 + V_2 + V_3 = Q/C_1 + Q/C_2 + Q/C_3$

- Putting all these together, we obtain:

- $V = Q/C_{eq} = Q(1/C_1 + 1/C_2 + 1/C_3)$

- Thus the equivalent capacitance is

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


What is the net effect?



The capacitance smaller than the smallest C !!!

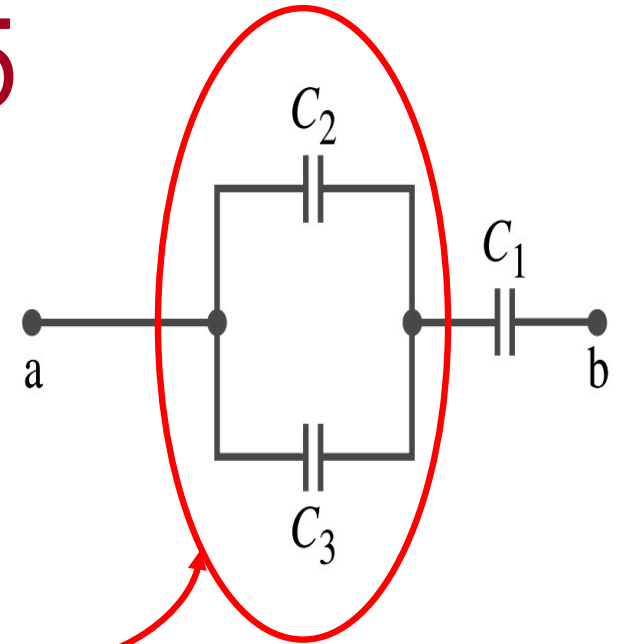Example 24 – 5

Equivalent Capacitor: Determine the capacitance of a single capacitor that will have the same effect as the combination shown in the figure. Take $C_1 = C_2 = C_3 = C$.



We should do these first!!

How? These are in parallel so the equivalent capacitance is:

$$C_{eq1} = C_1 + C_2 = 2C$$

Now the equivalent capacitor is in series with C_1 .

$$\frac{1}{C_{eq}} = \frac{1}{C_{eq1}} + \frac{1}{C_2} = \frac{1}{2C} + \frac{1}{C} = \frac{3}{2C} \quad \xrightarrow{\text{Solve for } C_{eq}} \quad C_{eq} = \frac{2C}{3}$$

Electric Energy Storage

- A charged capacitor stores energy.
 - The stored energy is the amount of the work done to charge it.
- The net effect of charging a capacitor is removing one type of charge from one plate and put them on to the other.
 - Battery does this when it is connected to a capacitor.
- Capacitors do not get charged immediately.
 - Initially when the capacitor is uncharged, no work is necessary to move the first bit of charge. Why?
 - Since there is no charge, there is no field that the external work needs to overcome.
 - When some charge is on each plate, it requires work to add more charges of the same sign due to the electric repulsion.



Electric Energy Storage

- The work needed to add a small amount of charge, dq , when a potential difference across the plate is V is: $dW=Vdq$.
- Since $V=q/C$, the work needed to store total charge Q is

$$W = \int_0^Q V dq = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

- Thus, the energy stored in a capacitor when the capacitor carries the charges $+Q$ and $-Q$ on each plate is

$$U = \frac{Q^2}{2C}$$

- Since $Q=CV$, we can rewrite

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$



Example 24 – 8

Energy store in a capacitor: A camera flash unit stores energy in a $150\mu\text{F}$ capacitor at 200V . How much electric energy can be stored?

Using the formula for stored energy. Umm.. Which one?

What do we know from the problem? C and V

So we use the one with C and V: $U = \frac{1}{2}CV^2$

$$U = \frac{1}{2}CV^2 = \frac{1}{2}(150 \times 10^{-6} \text{ F})(200\text{V})^2 = 3.0\text{J}$$

How do we get J from FV^2 ? $FV^2 = \left(\frac{C}{V}\right)V^2 = CV = C\left(\frac{J}{C}\right) = J$



Electric Energy Density

- The energy stored in a capacitor can be considered as being stored in the electric field between the two plates
- For a uniform field E between two plates, $V=Ed$ and $C=\epsilon_0 A/d$
- Thus the stored energy is

$$U = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) (Ed)^2 = \frac{1}{2} \epsilon_0 E^2 Ad$$

- Since Ad is the gap volume V , we can obtain the energy density, stored energy per unit volume, as

$$u = \frac{1}{2} \epsilon_0 E^2$$

**Valid for any space
that is vacuum**

Electric energy stored per unit volume in any region of space is proportional to the square of E in that region.

Dielectrics

- Capacitors have an insulating sheet of material, called dielectric, between the plates to
 - Increase breakdown voltage greater than that in air (3MV/m)
 - Apply higher voltage to the gap without the charge passing across
 - Allow the plates get closer together without touching
 - Increases capacitance (recall $C = \epsilon_0 A/d$)
 - Increase the capacitance by the dielectric constant
$$C = KC_0$$
 - Where C_0 is the intrinsic capacitance when the gap is vacuum

Dielectrics

- The value of dielectric constant K varies depending on the material (Table 24 – 1)
 - K for vacuum is 1.0000
 - K for air is 1.0006 (this is why permittivity of air and vacuum are used interchangeably.)
 - K for paper is 3.7
- Maximum electric field before breakdown occurs is called the dielectric strength. What is its unit?
 - V/m
- The capacitance of a parallel plate capacitor with a dielectric (K) filling the gap is

$$C = KC_0 = K\epsilon_0 \frac{A}{d}$$



Dielectrics

- A new quantity of the permittivity of a dielectric material is defined as $\epsilon = K\epsilon_0$
- The capacitance of a parallel plate capacitor with a dielectric medium filling the gap is


$$C = \epsilon \frac{A}{d}$$

- The energy density stored in an electric field E in a dielectric is

$$u = \frac{1}{2} K \epsilon_0 E^2 = \frac{1}{2} \epsilon E^2$$

Valid for any space w/ dielectric whose permittivity ϵ .

ProtoDUNE Dual Phase

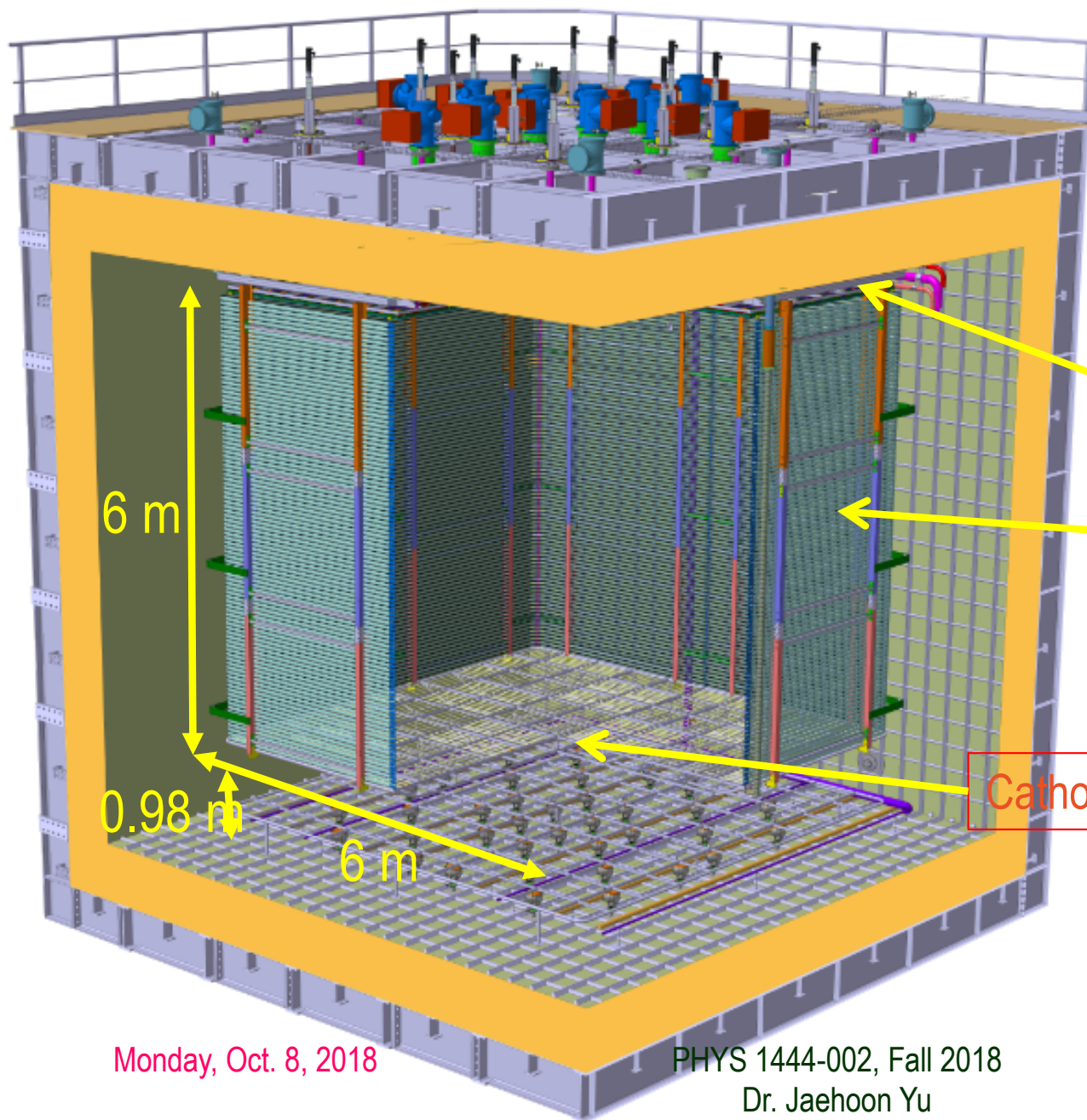

- Field Cage and cathode hangs off of the ceiling
- Essential to have light yet sturdy structure
- Based on modular concept as SP

Charge Readout Planes

Field Cage (common structural elements with SP)


Cathode



Monday, Oct. 8, 2018

PHYS 1444-002, Fall 2018
Dr. Jaehoon Yu

DUNE Dual Phase

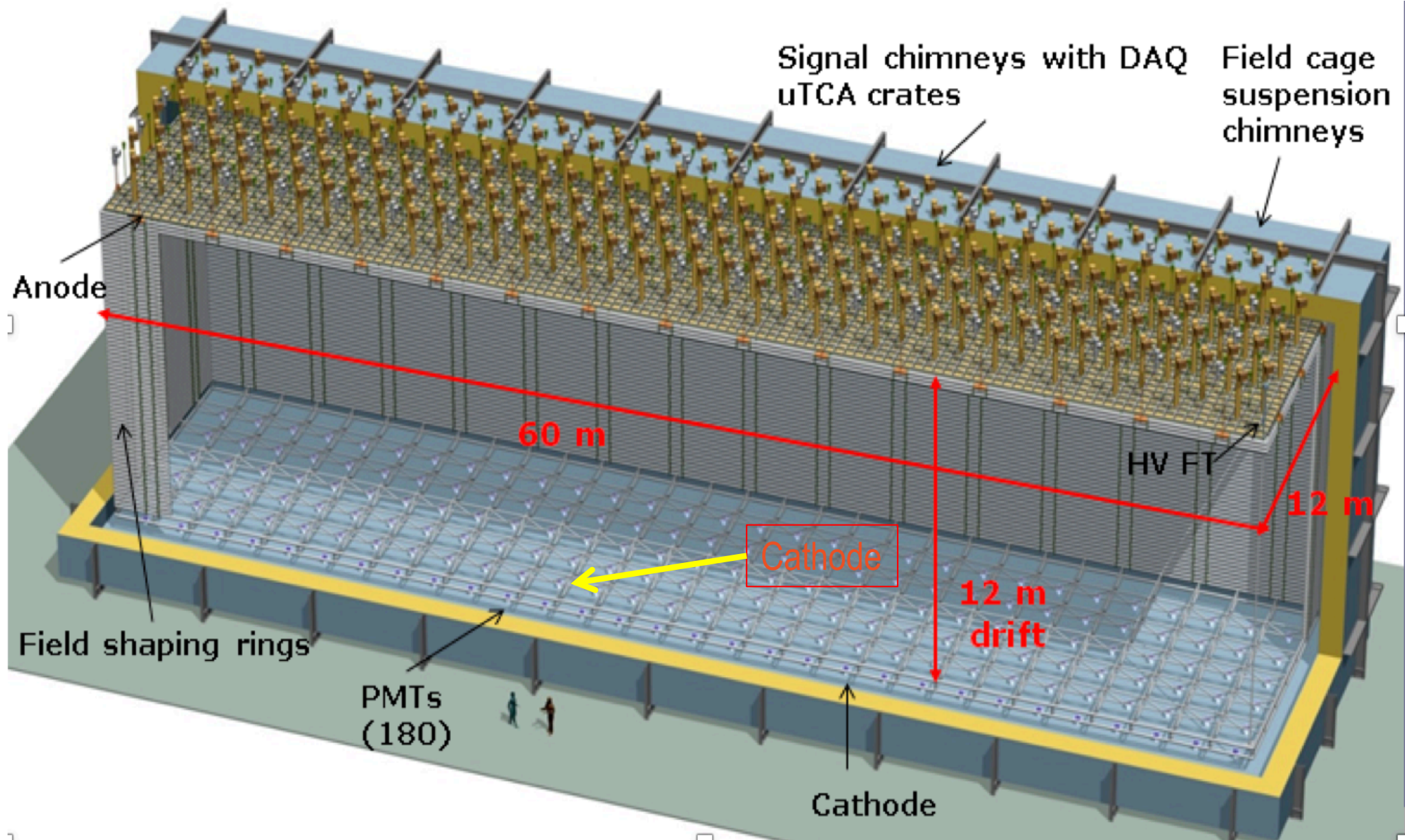

Monday, Oct. 8, 2018



PHYS 1444-002, Fall 2018
Dr. Jaehoon Yu

15