

PHYS 1441 – Section 002

Lecture #12

Monday, Oct. 15, 2018

*Dr. **Jaehoon** Yu*

- Chapter 25
 - Ohm's Law: Resistors, Resistivity
 - Electric Power
 - Alternating Current
 - Microscopic View of Electric Current
 - Ohm's Law in Microscopic View
 - EMF and Terminal Voltage

Today's homework is #8, due 11pm, Wednesday, Oct. 24!!



Announcements

- Reading Assignments: CH25.9 and 25.10
- Reminder: Mid Term Exam
 - In class this Wednesday, Oct. 17
 - Covers CH21.1 through CH25.10 + appendix
 - Bring your calculator but DO NOT input formula into it!
 - Cell phones or any types of computers cannot replace a calculator!
 - BYOF: You may bring a one 8.5x11.5 sheet (front and back) of handwritten formulae and values of constants
 - No derivations, word definitions or solutions of any kind!
 - No additional formulae or values of constants will be provided!
 - Do NOT miss the exam!! You will get an F!
- Mid-term grade discussions
 - From 12:00 – 2:30pm, Wednesday, Oct. 24 in my office (CPB342)
 - Last name starts with A – C (12 – 12:30), D– H (12:30 – 1), I – O (1 – 1:30), P – S (1:30 – 2:00), T – Z (2-2:30)



Special Extra Credit #4

- **Election Participation Exercise**
- For those with legal voting right: You can submit up to three “I Voted” sticker for 20 points total – one your own and up to two others who voted
- For those without legal voting right: You can submit up to four “I Voted” sticker for 20 points total
- Be sure to tape one side of the stickers on a sheet of paper with your name on it.
 - Write the precinct number the vote is cast, the full name of the person voted and the signature next to the relevant sticker
- None of the stickers can be from the same person on someone else’s extra credit or yours
- Deadline: Beginning of the class Wednesday, Nov. 7



Example 25 – 4

Flashlight bulb resistance: A small flashlight bulb draws 300mA from its 1.5V battery. (a) What is the resistance of the bulb? (b) If the voltage drops to 1.2V, how would the current change?


From Ohm's law, we obtain

$$R = \frac{V}{I} = \frac{1.5V}{300mA} = \frac{1.5V}{0.3A} = 5.0\Omega$$


Would the current increase or decrease, if the voltage reduces to 1.2V?

If the resistance did not change, the current is
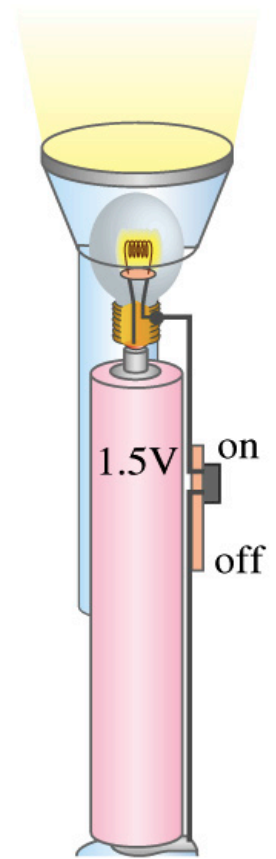
$$I = \frac{V}{R} = \frac{1.2V}{5.0\Omega} = 0.24A = 240mA$$



Ohm's Law: Resistors

- All electric devices offer resistance to the flow of current.
 - Filaments of light bulbs or heaters are wires with high resistance to cause electrons to lose their energy in the wire
 - In general connecting wires have lower resistance compared to other devices on the circuit
- In circuits, resistors are used to control the amount of current
 - Resistors offer resistance of less than one ohm to millions of ohms
 - Main types are
 - “wire-wound” resistors which consists of a coil of fine wire
 - “composition” resistors which are usually made of semiconductor carbon
 - thin metal films
- When drawn in the circuit, the symbol for a resistor is: 
- Wires are drawn simply as straight lines

Monday, Oct. 15, 2018




PHYS 1444-002, Fall 2018
Dr. Jaehoon Yu

Ohm's Law: Resistor Values

- Resistors have its resistance color-coded on its body
- The color-coding follows the convention below:

Color	Number	Multiplier	Tolerance
Black	0	$1=10^0$	
Brown	1	10^1	
Red	2	10^2	
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	
Gray	8	10^8	
White	9	10^9	
Gold		10^{-1}	5%
Silver		10^{-2}	10%
None			20%

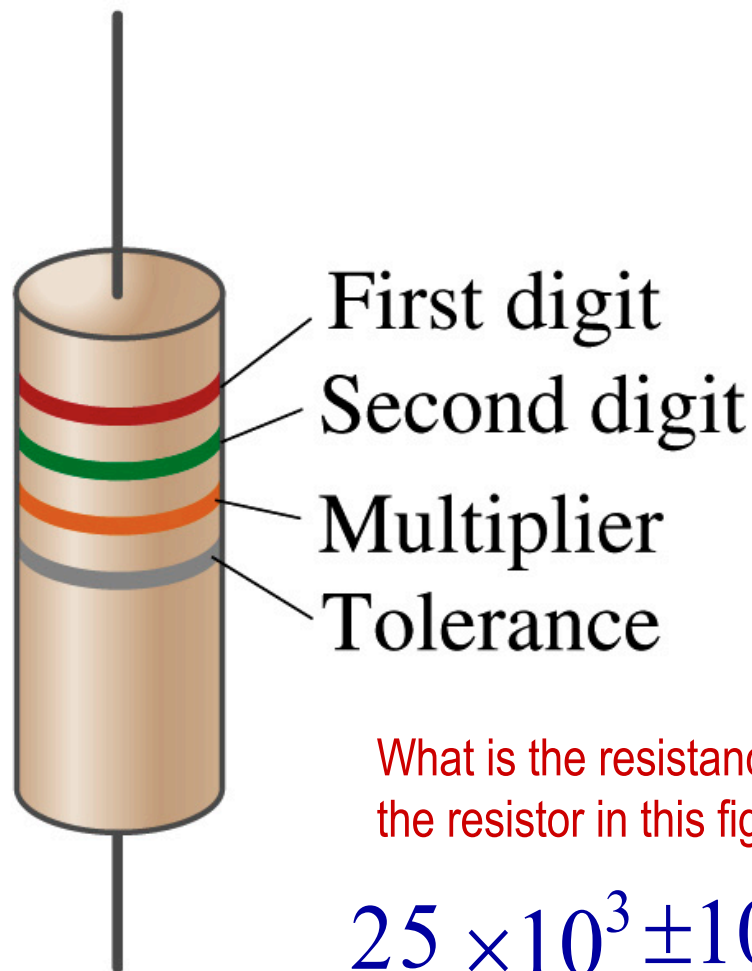


What is the resistance of the resistor in this figure?

$$25 \times 10^3 \pm 10\%$$

Resistivity

- It is experimentally found that the resistance R of a metal wire is directly proportional to its length l and inversely proportional to its cross-sectional area A
 - How would you formularize this? $R = \rho \frac{l}{A}$
 - The proportionality constant ρ is called the resistivity and depends on the material used. What is the unit of this constant?
 - ohm-m or $\Omega\text{-m}$
 - The values depends on purity, heat treatment, temperature, etc
 - How would you interpret the resistivity?
 - The higher the resistivity the higher the resistance
 - The lower the resistivity the lower the resistance and the higher the conductivity \rightarrow Silver has the lowest resistivity.
 - So silver is the best conductor
 - The reciprocal of the resistivity is called conductivity, σ ,

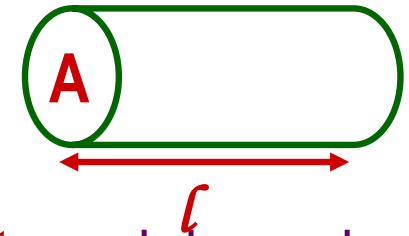

$$\sigma = \frac{1}{\rho}$$


Monday, Oct. 15, 2018



PHYS 1444-002, Fall 2018
Dr. Jaehoon Yu

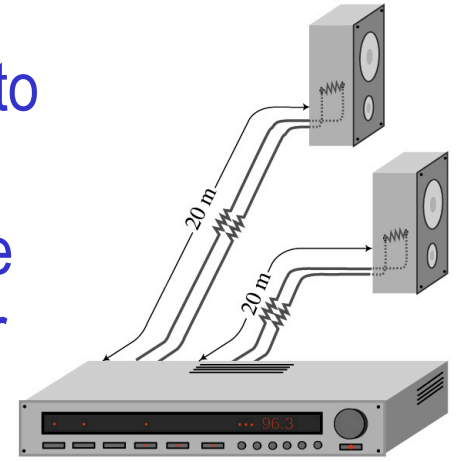Example 25 – 5

Speaker wires: Suppose you want to connect your stereo to remote speakers. (a) If each wire must be 20m long, what diameter copper wire should you use to keep the resistance less than $0.1\text{-}\Omega$ per wire? (b) If the current on each speaker is 4.0A , what is the voltage drop across each wire?



The resistivity of a copper is $\rho_{Cu} = 1.68 \times 10^{-8} \Omega \cdot m$ Table 25.1

From the formula for resistance, we can obtain the formula for area

$$R = \rho \frac{l}{A} \quad \text{Solve for A} \quad A = \rho \frac{l}{R} = \pi r^2$$

$$\text{Solve for d} \quad d = 2r = 2\sqrt{\frac{\rho l}{\pi R}} = 2\sqrt{\frac{1.68 \times 10^{-8} \Omega \cdot m \cdot 20m}{\pi \cdot 0.1\Omega}} = 2.1 \times 10^{-3} m = 2.1mm$$

From Ohm's law, $V=IR$, we obtain

$$V = IR = 4.0A \cdot 0.1\Omega = 0.4V$$

Example 25 – 6

Stretching changes resistance: A wire of resistance R is stretched uniformly until it is twice its original length. What happens to its resistance?

What is the constant quantity in this problem? The volume!

What is the volume of a cylinder of length L and radius r ? $V = AL = \pi r^2 L$

What happens to A if L increases factor two, $L'=2L$?

The cross-sectional area, A , halves. $A'=A/2$

The original resistance is $R = \rho \frac{l}{A}$

The new resistance is $R' = \rho \frac{L'}{A'} = \rho \frac{2L}{A/2} = 4\rho \frac{L}{A} = 4R$

The resistance of the wire increases by a factor of four if the length increases twice.

Temperature Dependence of Resistivity

- Do you think the resistivity depends on temperature?
 - Yes
- Would it increase or decrease with the temperature?
 - Increase
 - Why?
 - Because the atoms are vibrating more rapidly as temperature increases and are arranged in a less orderly fashion. So?
 - They might interfere more with the flow of electrons.
- If the temperature change is not too large, the resistivity of metals usually increase nearly linearly w/ temperature
$$\rho_T = \rho_0 [1 + \alpha (T - T_0)]$$
 - α is the temperature coefficient of resistivity
 - α of some semiconductors can be negative due to increased number of freed electrons.

Electric Power

- Why is the electric energy useful?
 - It can transform into different forms of energy easily.
 - Motors, pumps, etc, transform electric energy to mechanical energy
 - Heaters, dryers, cook-tops, etc, transforms electricity to thermal energy
 - Light bulb filament transforms electric energy to light energy
 - Only about 10% of the energy turns to light and the 90% lost via heat
 - Typical household light bulb and heating elements have resistance of order a few ohms to a few hundred ohms (what is the resistance of the filament of a 60W bulb?)
- How does the electric energy transforms to thermal energy?
 - Flowing electrons collide with the vibrating atoms of the wire.
 - In each collision, part of electron's kinetic energy is transferred to the atom it collides with.
 - The kinetic energy of wire's bound atoms increases, and thus the temperature of the wire increases.
 - The increased thermal energy can be transferred as heat through conduction and convection to the air in a heater or to food on a pan, through radiation to bread in a toaster or radiated as light.




Electric Power

- How do we find out the power transformed by an electric device?
 - What is definition of the power?
 - The rate at which work is done or the energy is transformed
- What is the energy transformed when an infinitesimal charge dq moves through a potential difference V ?
 - $dU = Vdq$
 - If dt is the time required for an amount of charge dq to move through the fixed potential difference V , the power P is
 - $P = dU/dt = V dq/dt$ ← **What is this?**
 - Thus, we obtain $P = VI$. In terms of resistance $P = I^2 R = \frac{V^2}{R}$
 - What is the unit? **Watts = J/s**
 - What kind of quantity is the electrical power?
 - Scalar
 - $P=IV$ can apply to any devices while the formula with resistance can only apply to devices that has resistance.



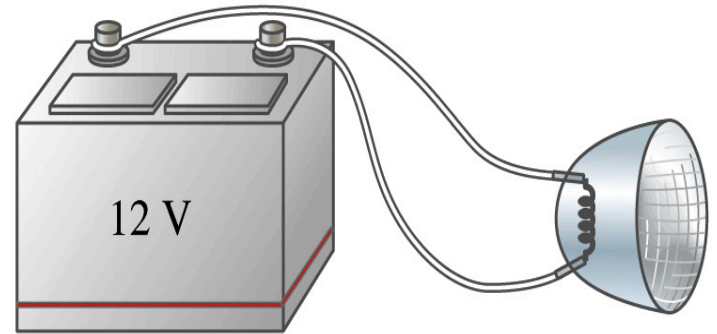Example 25 – 8

Headlights: Calculate the resistance of a 40-W automobile headlight designed for 12V.



40-W Headlight

Since the power is 40W and the voltage is 12V, we use the formula with V and R.


$$P = \frac{V^2}{R}$$




$$R = \frac{V^2}{P} = \frac{(12V)^2}{40W} = 3.6\Omega$$

Power in Household Circuits

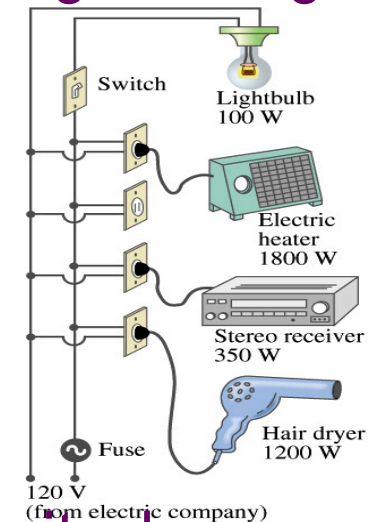
- Household devices usually have small resistance
 - But since they draw current, if they become large enough, wires can heat up (overloaded)
 - Why is using thicker wires safer?
 - Thicker wires has less resistance, lower heat
 - Overloaded wire can set off a fire at home- How do we prevent this?
 - Put in a switch that would disconnect the circuit when overloaded



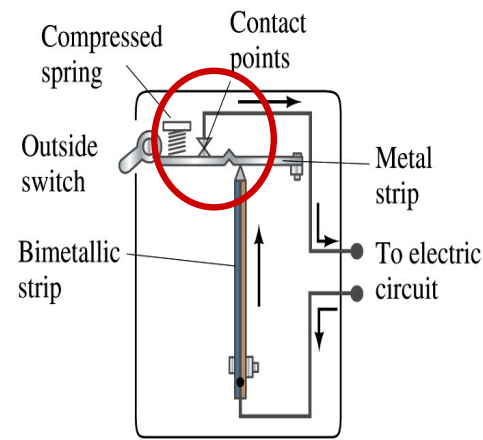- Fuse or circuit breakers
- They open up the circuit when the current is over certain value



(b) Circuit breaker (closed)

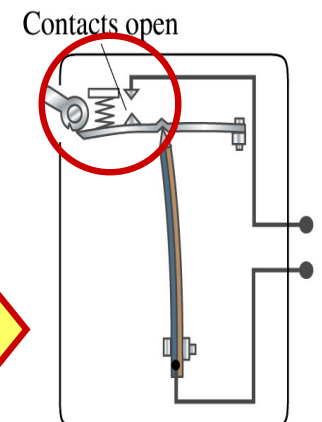

(c) Circuit breaker (open)

Monday, Oct. 15, 2018




PHYS 1444-002, Fall 2018
Dr. Jaehoon Yu

Example 25 – 11

Will a fuse blow?: Determine the total current drawn by all the devices in the circuit in the figure.

The total current is the sum of current drawn by individual device.
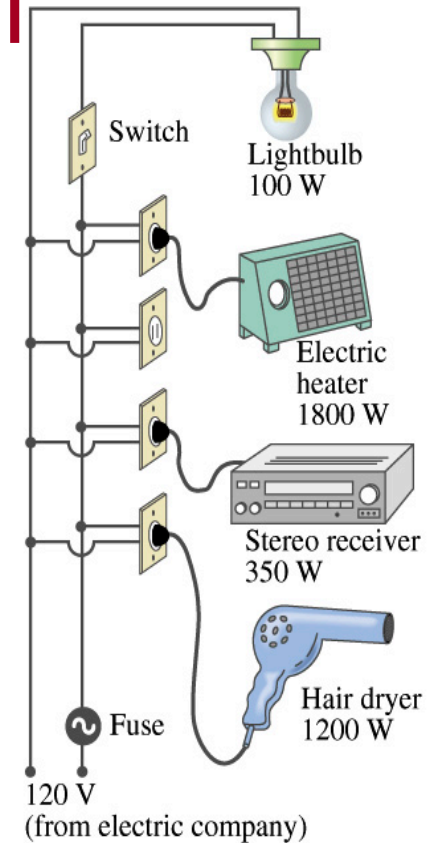
$$P = IV \quad \text{Solve for } I \quad I = P/V$$



Bulb $I_B = 100W/120V = 0.8A$

Heater $I_H = 1800W/120V = 15.0A$

Stereo $I_S = 350W/120V = 2.9A$

Dryer $I_D = 1200W/120V = 10.0A$

Total current



$$I_T = I_B + I_H + I_S + I_D = 0.8A + 15.0A + 2.9A + 10.0A = 28.7A$$

What is the total power? $P_T = P_B + P_H + P_S + P_D = 100W + 1800W + 350W + 1200W = 3450W$



Alternating Current

- Does the direction of the flow of current change while a battery is connected to a circuit?
 - No. Why?
 - Because its source of potential difference stays put.
 - This kind of current is called the Direct Current (DC), and it does not change its direction of flow while the battery is connected.
 - How would DC look as a function of time?
 - A straight line
- Electric generators at electric power plant produce alternating current (AC)
 - AC reverses direction many times a second
 - AC is sinusoidal as a function of time
- Most the currents supplied to homes and business are AC.

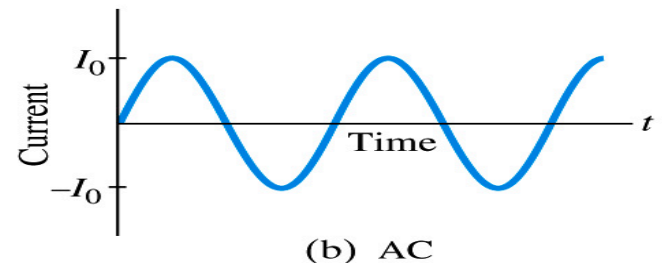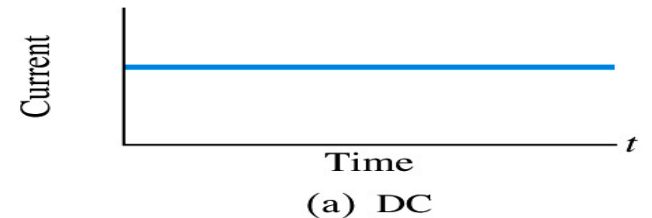

Monday, Oct. 15, 2018



PHYS 1444-002, Fall
Dr. Jaehoon Yl

The Alternating Current

- The voltage produced by an AC electric generator is sinusoidal

- This is why the current is sinusoidal

- Voltage produced can be written as

$$V = V_0 \sin 2\pi ft = V_0 \sin \omega t$$

- What are the maximum and minimum voltages?

- V_0 ($-V_0$) and 0

- The potential oscillates between $+V_0$ and $-V_0$, the peak voltage or the amplitude


- What is f ?

- The frequency, the number of complete oscillations made per second. What is the unit of f ? What is the normal size of f in the US?

- $f=60\text{Hz}$ in the US and Canada.

- Many European countries have $f=50\text{Hz}$.

- $\omega=2\pi f$

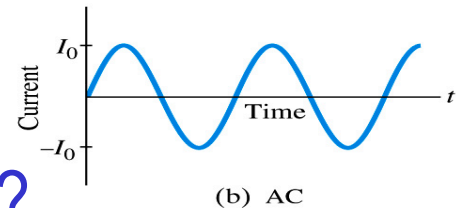

Alternating Current

- Since $V=IR$, if a voltage V exists across a resistance R , the current I is

$$I = \frac{V}{R} = \frac{V_0}{R} \sin 2\pi ft = I_0 \sin \omega t$$


What is this?

- What are the maximum and minimum currents?
 - I_0 ($-I_0$) and 0.
 - The current oscillates between $+I_0$ and $-I_0$, the peak currents or the amplitude. The current is positive when electron flows to one direction and negative when they flow the opposite.
 - AC is as many times positive as negative. What's the average current?
 - Zero. So there is no power and no heat is produced in a heater?
 - Yes there is! The electrons actually flow back and forth, so power is delivered.

Power Delivered by Alternating Current

- AC power delivered to a resistance is:

$$P = I^2 R = I_0^2 R \sin^2 \omega t$$

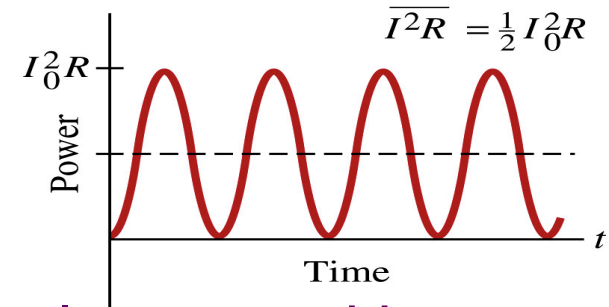

- Since the current is squared, the power is always positive
- The average power delivered is $\bar{P} = \frac{1}{2} I_0^2 R$
- Since the power is also $P = V^2/R$, we can obtain

$$P = \left(V_0^2 / R \right) \sin^2 \omega t$$

Average power

$$\bar{P} = \frac{1}{2} \left(\frac{V_0^2}{R} \right)$$

- The average of the square of current and voltage are important in calculating power:

$$\overline{I^2} = \frac{1}{2} I_0^2$$

$$\overline{V^2} = \frac{1}{2} V_0^2$$

Power Delivered by Alternating Current

- The square root of each of these are called root-mean-square, or rms:

$$I_{rms} = \sqrt{I^2} = \frac{I_0}{\sqrt{2}} = 0.707I_0$$

$$V_{rms} = \sqrt{V^2} = \frac{V_0}{\sqrt{2}} = 0.707V_0$$

- rms values are called effective values
 - These are useful quantities since they can substitute current and voltage directly in power, as if they are in DC

$$\bar{P} = \frac{1}{2} I_0^2 R = I_{rms}^2 R$$

$$\bar{P} = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{rms}^2}{R}$$


$$\bar{P} = I_{rms} V_{rms}$$

- In other words, an AC of peak voltage V_0 or peak current I_0 produces as much power as DC voltage of V_{rms} or DC current I_{rms} .
- So normally, rms values in AC are specified or measured.
 - US uses 115V rms voltage. What is the peak voltage?
 - $V_0 = \sqrt{2} V_{rms} = \sqrt{2} \cdot 115V = 162.6V$
 - Europe uses 240V
 - $V_0 = \sqrt{2} V_{rms} = \sqrt{2} \cdot 240V = 340V$



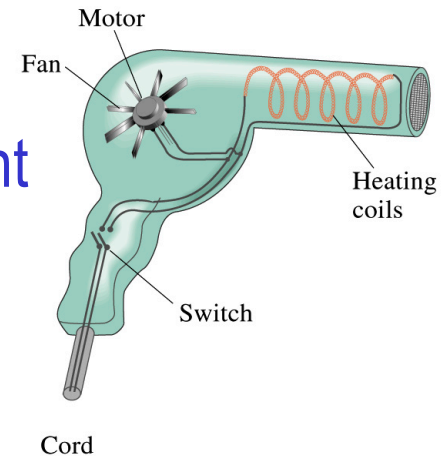Example 25 – 13

Hair Dryer. (a) Calculate the resistance and the peak current in a 1000-W hair dryer connected to a 120-V AC line. (b) What happens if it is connected to a 240-V line in Britain?



The rms current is:
$$I_{rms} = \frac{\bar{P}}{V_{rms}} = \frac{1000W}{120V} = 8.33A$$

The peak current is:
$$I_0 = \sqrt{2}I_{rms} = \sqrt{2} \cdot 8.33A = 11.8A$$

Thus the resistance is:
$$R = \frac{\bar{P}}{I_{rms}^2} = \frac{1000W}{(8.33A)^2} = 14.4\Omega$$

(b) If connected to 240V in Britain ...


The average power provide by the AC in UK is

$$\bar{P} = \frac{V_{rms}^2}{R} = \frac{(240V)^2}{14.4\Omega} = 4000W$$

So? The heating coils in the dryer will melt!

Microscopic View of Electric Current

- When a potential difference is applied to the two ends of a wire w/ uniform cross-section, the direction of electric field is parallel to the walls of the wire, this is possible since the charges are moving
- Let's define a microscopic vector quantity, the current density, \mathbf{j} , the electric current per unit cross-sectional area
 - $j = I/A$ or $I = jA$ if the current density is uniform
 - If not uniform $I = \int \vec{j} \cdot d\vec{A}$
 - The direction of \mathbf{j} is the direction the positive charge would move when placed at that position, generally the same as \mathbf{E}
- The current density exists on any point in space while the current I refers to a conductor as a whole so a macroscopic

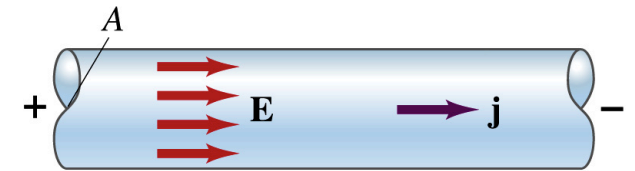


Microscopic View of Electric Current

- The direction of \mathbf{j} is the direction of a positive charge. So in a conductor, since negatively charged electrons move, the direction is $-\mathbf{j}$.
- Let's think about the current in a microscopic view again:
 - When voltage is applied to the end of a wire
 - Electric field is generated by the potential difference
 - Electrons feel force and get accelerated
 - Electrons soon reach to a steady average speed due to collisions with atoms in the wire, called drift velocity, \mathbf{v}_d
 - The drift velocity is normally much smaller than electrons' average random speed.

Monday, Oct. 15, 2018



PHYS 1444-002, Fall 201
Dr. Jaehoon Yu

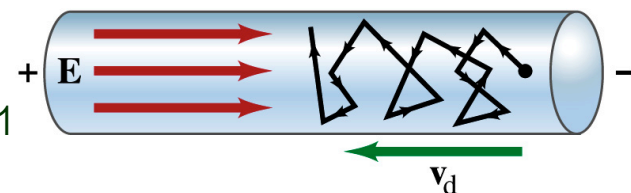

Microscopic View of Electric Current

- The drift velocity of electrons in a wire is only about 0.05mm/s. How could we get light turned on immediately then?
 - While the electrons in a wire travels slow, the electric field travels essentially at the speed of light. Then what is all the talk about electrons flowing through?
 - It is just like water. When you turn on the facet, water flows right off the facet despite the fact that the water travels slow.
 - Electricity is the same. Electrons fill the conductor wire and when the switch is flipped on or a potential difference is applied, the electrons close to the positive terminal flows into the bulb.
 - Interesting, isn't it? Why is the field travel at the speed of light then?

