

PHYS 1444 – Section 002

Lecture #23

Monday, Nov. 25, 2019

Dr. Jaehoon Yu

- Chapter 30: Inductance
 - LR Circuit
 - LC circuit and EM Oscillation
 - AC circuit with Inductor Only & Capacitor Only
- Chapter 31: Maxwell's equations
 - Expansion of Ampere's Law
 - Gauss' Law for Magnetism
 - Production of EM Waves
 - Light as EM Waves




Announcements

- Reading assignments: CH30.7 – 30.11
- Planetarium Extra Credit: bring to class Mon. Dec. 2
 - Be sure to tape one end of the ticket stub on a sheet of paper with your name on it
- Final comprehensive exam
 - In class 1:00 – 2:20pm, Wednesday, Dec. 4
 - Covers: CH21.1 – what we finish Monday, Dec. 2
 - Bring your calculator but DO NOT input formula into it!
 - Cell phones or any types of computers cannot replace a calculator!
 - BYOF: You may bring a one 8.5x11.5 sheet (front and back) of handwritten formulae and values of constants for the quiz
 - No derivations, word definitions, set ups or solutions of any problems!
 - NO MAXWELL's Equations!!
 - No additional formulae or values of constants will be provided!
- No class this Wednesday, Nov. 27
 - Happy Thanksgiving!
- Course evaluation survey!!



LR Circuits

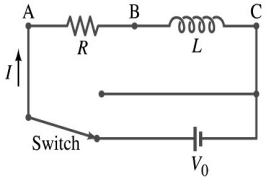
- What happens when an emf is applied to an inductor?
 - An inductor has some resistance, however negligible




- So an inductor can be drawn as a circuit of separate resistance and coil. What is the name this kind of circuit? **LR Circuit**

- What happens at the instance the switch is thrown to apply emf to the circuit?

- The current starts to flow, gradually increasing from 0
- This change is opposed by the induced emf in the inductor → the emf at point B is higher than point C
- However there is a voltage drop at the resistance which reduces the voltage across inductance
- Thus the current increases less rapidly
- The overall behavior of the current is a gradual increase, reaching to the maximum current $I_{\max} = V_0/R$.

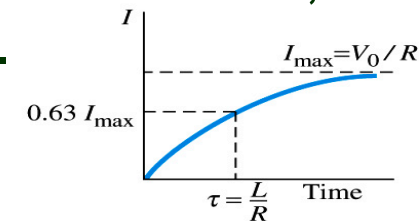

LR Circuits

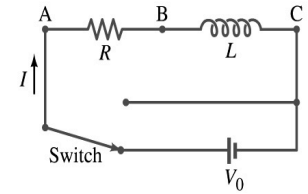

- This can be shown w/ Kirchhoff loop rules

- The emfs in the circuit are the battery voltage V_0 and the emf $\mathcal{E} = -L(dI/dt)$ in the inductor opposing the current increase

- The sum of the potential changes through the circuit is

$$V_0 + \mathcal{E} - IR = V_0 - L dI/dt - IR = 0$$

- Where I is the current at any instance


- By rearranging the terms, we obtain the differential eq.

- $L dI/dt + IR = V_0$

- We can integrate just as in RC circuit

- So the solution is $-\frac{1}{R} \ln\left(\frac{V_0 - IR}{V_0}\right) = \frac{t}{L}$

- Where $\tau = L/R$

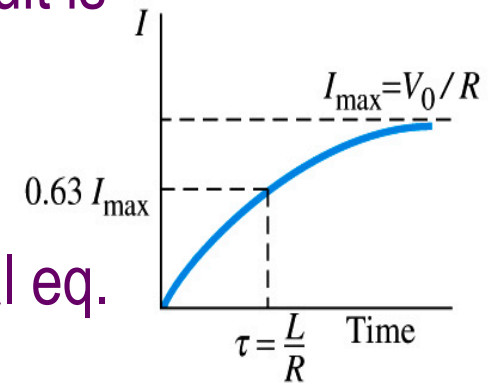


$$\int_{I=0}^I \frac{dI}{V_0 - IR} = \int_{t=0}^t \frac{dt}{L}$$

$$I = V_0 (1 - e^{-t/\tau}) / R = I_{\max} (1 - e^{-t/\tau})$$

- This is the time constant τ of the LR circuit and is the time required for the current I to reach 0.63 of the maximum

Discharge of LR Circuits

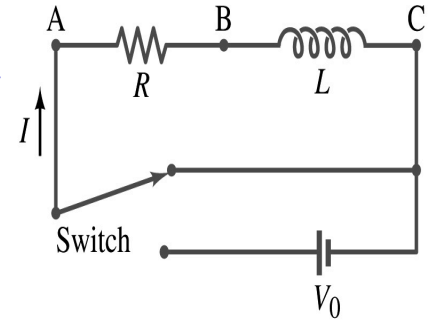
- If the switch is flipped away from the battery



- The differential equation becomes

- $L \frac{dI}{dt} + IR = 0$

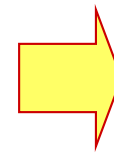
- So the integration is $\int_{I_0}^I \frac{dI}{IR} = - \int_{t=0}^t \frac{dt}{L}$



$$\ln \frac{I}{I_0} = - \frac{R}{L} t$$

- Which results in the solution

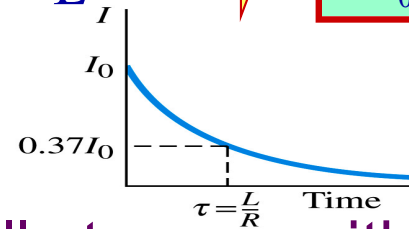- $I = I_0 e^{-\frac{R}{L} t} = I_0 e^{-t/\tau}$




- The current decays exponentially to zero with the time constant $\tau = L/R$

- So there always is a reaction time when a system with a coil, such as an electromagnet, is turned on or off.

- The current in LR circuit behaves almost the same as that in RC circuit but the time constant is inversely proportional to R in LR circuit unlike the RC circuit

AC Circuit w/ Resistance only

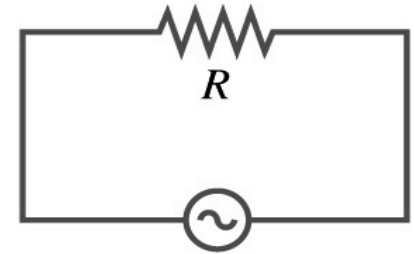- What do you think will happen when an AC source is connected to a resistor?
- From Kirchhoff's loop rule, we obtain




- Thus $V - IR = 0$

$$V = I_0 R \sin \omega t = V_0 \sin \omega t$$

– where $V_0 = I_0 R$

- What does this mean?

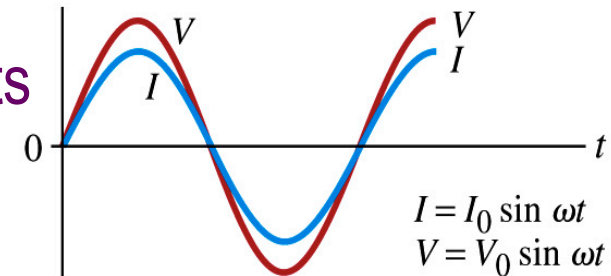- Current is 0 when voltage is 0 and current is in its peak when voltage is in its peak.
- Current and voltage are “in phase”



- Energy is lost via the transformation into heat at an average rate $\bar{P} = \bar{I} \bar{V} = I_{rms}^2 R = V_{rms}^2 / R$

AC Circuit w/ Inductance only

- From Kirchhoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus



$$V = L \frac{dI}{dt} = L \frac{d(I_0 \sin \omega t)}{dt} = \omega L I_0 \cos \omega t$$

- Using the identity $\cos \theta = \sin(\theta + 90^\circ)$
- $V = \omega L I_0 \sin(\omega t + 90^\circ) = V_0 \sin(\omega t + 90^\circ)$
 - where $V_0 = \omega L I_0$
- What does this mean?

- Current and voltage are “out of phase by $\pi/2$ or 90° ”. In other words the current reaches its peak $1/4$ cycle after the voltage

- What happens to the energy?

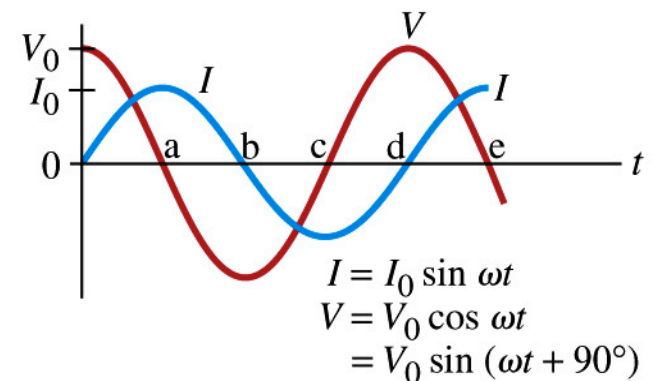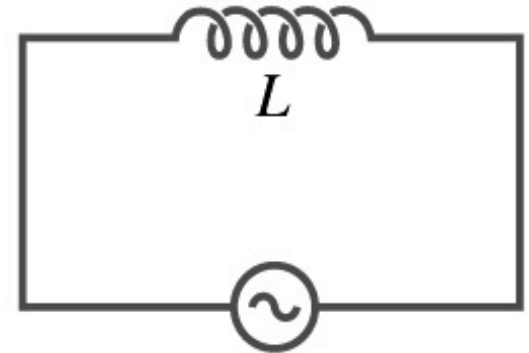- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the magnetic field
- Then released back to the source



AC Circuit w/ Inductance only

- How are the resistor and inductor different in terms of energy?
 - Inductor Stores the energy temporarily in the magnetic field and then releases it back to the emf source
 - Resistor Does not store energy but transforms it to thermal energy, losing it to the environment
- How are they similar?
 - They both impede the flow of charge
 - For a resistance R , the peak voltage and current are related to $V_0 = I_0 R$
 - Similarly, for an inductor we may write $V_0 = I_0 X_L$
 - Where X_L is the inductive reactance of the inductor $X_L = \omega L$ 0 when $\omega=0$.
 - What do you think is the unit of the reactance? Ω
 - The relationship $V_0 = I_0 X_L$ is not valid at a particular instance. Why not?
 - Since V_0 and I_0 do not occur at the same time



$$V_{rms} = I_{rms} X_L$$

is valid!

Example 30 – 9

Reactance of a coil. A coil has a resistance $R=1.00\Omega$ and an inductance of 0.300H . Determine the current in the coil if (a) 120 V DC is applied to it; (b) 120 V AC (rms) at 60.0Hz is applied.

Is there a reactance for DC? Nope. Why not? Since $\omega=0$, $X_L = \omega L = 0$

So for DC power, the current is from Kirchhoff's rule $V - IR = 0$

$$I_0 = \frac{V_0}{R} = \frac{120\text{V}}{1.00\Omega} = 120\text{A}$$

For an AC power with $f=60\text{Hz}$, the reactance is

$$X_L = \omega L = 2\pi fL = 2\pi \cdot (60.0\text{s}^{-1}) \cdot 0.300\text{H} = 113\Omega$$

Since the resistance can be ignored compared to the reactance, the rms current is


$$I_{rms} \approx \frac{V_{rms}}{X_L} = \frac{120\text{V}}{113\Omega} = 1.06\text{A}$$



AC Circuit w/ Capacitance only

- What happens when a capacitor is connected to a DC power source?

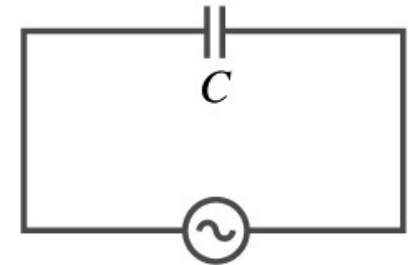- The capacitor quickly charges up.
- There is no steady current flow in the circuit
 - Since the capacitor prevents the flow of the DC current



- What do you think will happen if it is connected to an AC power source?
 - The current flows continuously. Why?
 - When the AC power turns on, charge begins to flow one direction, charging up the plates
 - When the direction of the power reverses, the charge flows in the opposite direction

AC Circuit w/ Capacitance only

- From Kirchhoff's loop rule, we obtain

$$V = \frac{Q}{C}$$

- The current at any instance is $I = \frac{dQ}{dt} = I_0 \sin \omega t$

- The charge Q on the plate at any instance is

$$Q = \int_{Q=0}^Q dQ = \int_{t=0}^t I_0 \sin \omega t dt = -\frac{I_0}{\omega} \cos \omega t$$

- Thus the voltage across the capacitor is


$$V = \frac{Q}{C} = -I_0 \frac{1}{\omega C} \cos \omega t$$

- Using the identity $\cos \theta = -\sin(\theta - 90^\circ)$

$$V = I_0 \frac{1}{\omega C} \sin(\omega t - 90^\circ) = V_0 \sin(\omega t - 90^\circ)$$

- Where

- $V_0 = \frac{I_0}{\omega C}$

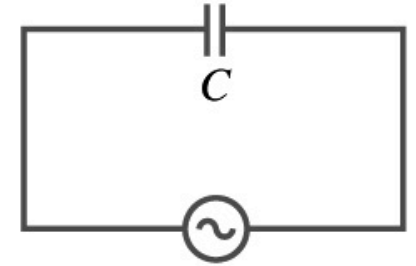


AC Circuit w/ Capacitance only

- So the voltage is $V = V_0 \sin(\omega t - 90^\circ)$
- What does this mean?
 - Current and voltage are “out of phase by $\pi/2$ or 90° ” but in this case, the voltage reaches its peak $\frac{1}{4}$ cycle after the current

- What happens to the energy?

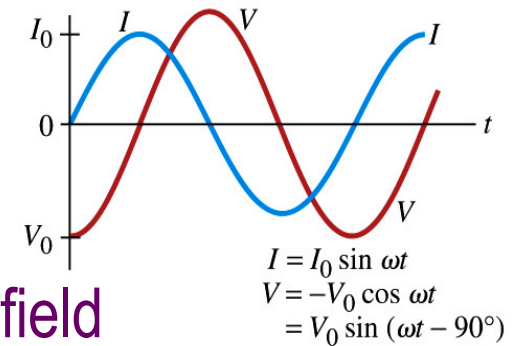- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the electric field
- Then released back to the source



- Applied voltage and the current in the capacitor can be written as $V_0 = I_0 X_C$

- Where the capacitive reactance X_C is defined as
- Again, this relationship is only valid for rms quantities

$$X_C = \frac{1}{\omega C}$$


Infinite
when
 $\omega=0$.

$$V_{rms} = I_{rms} X_C$$



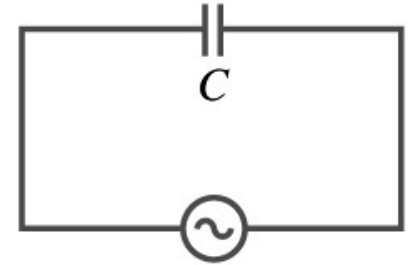Example 30 – 10

Capacitor reactance. What are the peak and rms current in the circuit in the figure if $C=1.0\mu\text{F}$ and $V_{\text{rms}}=120\text{V}$? Calculate for (a) $f=60\text{Hz}$, and then for (b) $f=6.0\times 10^5\text{Hz}$.



The peak voltage is $V_0 = \sqrt{2}V_{\text{rms}} = 120\text{V} \cdot \sqrt{2} = 170\text{V}$

The capacitance reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot (60\text{s}^{-1}) \cdot 1.0 \times 10^{-6}\text{F}} = 2.7\text{k}\Omega$$

Thus the peak current is

$$I_0 = \frac{V_0}{X_C} = \frac{170\text{V}}{2.7\text{k}\Omega} = 63\text{mA}$$

The rms current is

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120\text{V}}{2.7\text{k}\Omega} = 44\text{mA}$$