

PHYS 1444 – Section 501

Lecture #21

Wednesday, Apr. 19, 2006

Dr. Jaehoon Yu

- Energy Stored in the Magnetic Field
- LR circuit
- LC Circuit and EM Oscillation
- LRC circuit
- AC Circuit w/ Resistance only
- AC Circuit w/ Inductance only

Today's homework is homework #11, due 7pm, next Thursday!!



Announcements

- Quiz Monday, Apr. 24 early in class
 - Covers: CH 29 to CH30
- Reading assignments:
 - CH29-8



Energy Stored in a Magnetic Field

- When an inductor of inductance \mathcal{L} is carrying current I which is changing at a rate dI/dt , energy is supplied to the inductor at a rate
 - $P = I\varepsilon = IL\frac{dI}{dt}$
- What is the work needed to increase the current in an inductor from 0 to I ?
 - The work, dW , done in time dt is $dW = Pdt = LI dI$
 - Thus the total work needed to bring the current from 0 to I in an inductor is
$$W = \int dW = \int_0^I LI dI = L \left[\frac{1}{2} I^2 \right]_0^I = \frac{1}{2} LI^2$$



Energy Stored in a Magnetic Field

- The work done to the system is the same as the energy stored in the inductor when it is carrying current I

- $$U = \frac{1}{2} LI^2$$

Energy Stored in a magnetic field inside an inductor

- This is compared to the energy stored in a capacitor, C , when the potential difference across it is V $U = \frac{1}{2} CV^2$
- Just like the energy stored in a capacitor is considered to reside in the electric field between its plates
- The energy in an inductor can be considered to be stored in its magnetic field



Stored Energy in terms of B

- So how is the stored energy written in terms of magnetic field B?

- Inductance of an ideal solenoid without a fringe effect

$$L = \mu_0 N^2 A / l$$

- The magnetic field in a solenoid is $B = \mu_0 NI / l$

- Thus the energy stored in an inductor is

$$U = \frac{1}{2} LI^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{l} \left(\frac{Bl}{\mu_0 N} \right)^2 = \frac{1}{2} \frac{B^2}{\mu_0} \underbrace{Al}$$

$$U = \frac{1}{2} \frac{B^2}{\mu_0} Al \quad \boxed{E}$$

- Thus the energy density is

$$u = \frac{U}{V} = \frac{U}{Al} = \frac{1}{2} \frac{B^2}{\mu_0}$$

What is this?

Volume V

$$u = \frac{1}{2} \frac{B^2}{\mu_0} \quad \boxed{E \text{ density}}$$

- This formula is valid to any region of space
- If a ferromagnetic material is present, μ_0 becomes μ .


What volume does Al represent?

The volume inside a solenoid!!



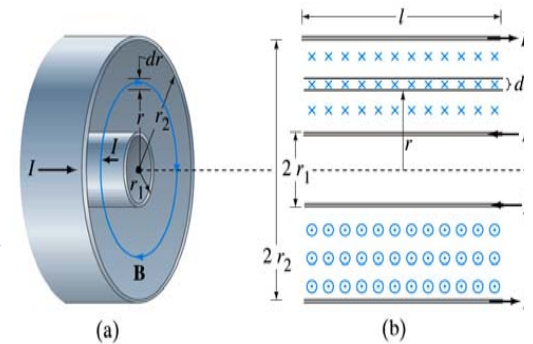Example 30 – 5

Energy stored in a coaxial cable. (a) How much energy is being stored per unit length in a coaxial cable whose conductors have radii r_1 and r_2 and which carry a current I ? (b) Where is the energy density highest?



(a) The inductance per unit length for a coaxial cable is $\frac{L}{l} = \frac{\mu_0}{2\pi} \ln \frac{r_2}{r_1}$

Thus the energy stored per unit length is $\frac{U}{l} = \frac{1}{2} \frac{LI^2}{l} = \frac{\mu_0 I^2}{4\pi} \ln \frac{r_2}{r_1}$


(b) Since the magnetic field is $B = \frac{\mu_0 I}{2\pi r}$

And the energy density is $u = \frac{1}{2} \frac{B^2}{\mu_0}$

The energy density is highest where B is highest. B is highest close to $r=r_1$, near the surface of the inner conductor.

LR Circuits

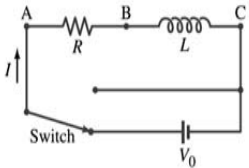- What happens when an emf is applied to an inductor?
 - An inductor has some resistance, however negligible




- So an inductor can be drawn as a circuit of separate resistance and coil. What is the name this kind of circuit? **LR Circuit**

- What happens at the instance the switch is thrown to apply emf to the circuit?
 - The current starts to flow, gradually increasing from 0
 - This change is opposed by the induced emf in the inductor → the emf at point B is higher than point C
 - However there is a voltage drop at the resistance which reduces the voltage across inductance
 - Thus the current increases less rapidly
 - The overall behavior of the current is gradual increase, reaching to the maximum current $I_{\max} = V_0/R$.


Wednesday, Apr. 19, 2006



PHYS 1444-501, Spr
Dr. Jaehoon Y

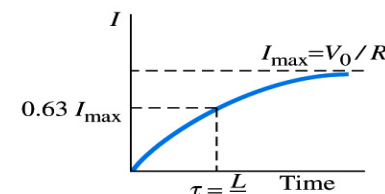

LR Circuits

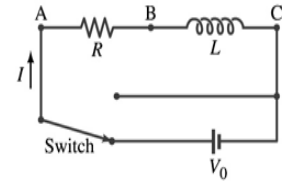

- This can be shown w/ Kirchhoff rule loop rules

- The emfs in the circuit are the battery voltage V_0 and the emf $\mathcal{E} = -L(dI/dt)$ in the inductor opposing the current increase

- The sum of the potential changes through the circuit is

$$V_0 + \mathcal{E} - IR = V_0 - L dI/dt - IR = 0$$

- Where I is the current at any instance


- By rearranging the terms, we obtain a differential eq.

- $L dI/dt + IR = V_0$

- We can integrate just as in RC circuit

- So the solution is $-\frac{1}{R} \ln\left(\frac{V_0 - IR}{V_0}\right) = \frac{t}{L}$

- Where $\tau = L/R$

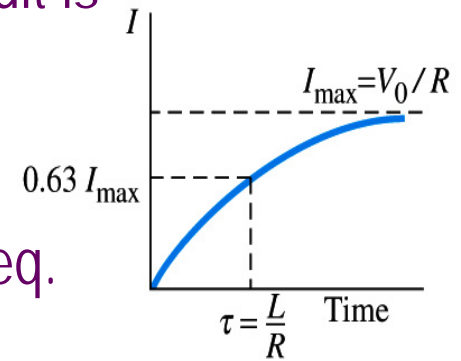


$$\int_{I=0}^I \frac{dI}{V_0 - IR} = \int_{t=0}^t \frac{dt}{L}$$

$$I = V_0 (1 - e^{-t/\tau}) / R = I_{\max} (1 - e^{-t/\tau})$$

- This is the time constant τ of the LR circuit and is the time required for the current I to reach 0.63 of the maximum

Discharge of LR Circuits

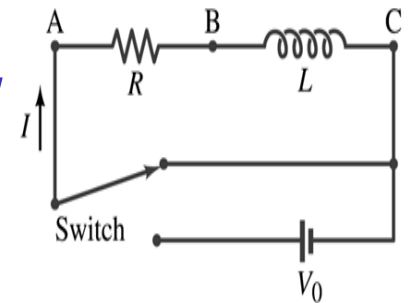- If the switch is flipped away from the battery



- The differential equation becomes


- $L \frac{dI}{dt} + IR = 0$

- So the integration is $\int_{I=0}^I \frac{dI}{IR} = \int_{t=0}^t \frac{dt}{L}$

$$\ln \frac{I}{I_0} = -\frac{R}{L} t$$

- Which results in the solution

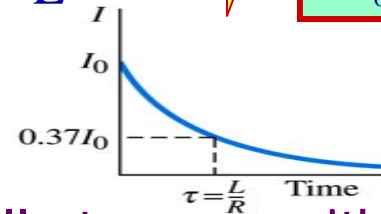
$$I = I_0 e^{-\frac{R}{L} t} = I_0 e^{-t/\tau}$$



- The current decays exponentially to zero with the time constant $\tau = L/R$
- So there always is a reaction time when a system with a coil, such as an electromagnet, is turned on or off.
- The current in LR circuit behaves almost the same as that in RC circuit but the time constant is inversely proportional to R in LR circuit unlike the RC circuit


LC Circuit and EM Oscillations

- What's an LC circuit?
 - A circuit that contains only an inductor and a capacitor
 - How is this possible? There is no source of emf!!
 - Well, you can imagine a circuit with a fully charged capacitor
 - In this circuit, we assume the inductor does not have any resistance
- Let's assume that the capacitor originally has $+Q_0$ on one plate and $-Q_0$ on the other
 - Suppose the switch is closed at $t=0$
 - The capacitor starts discharging
 - The current flow through the inductor increases
 - Applying Kirchhoff's loop rule, we obtain $-L dI/dt + Q/C = 0$
 - Since the current flows out of the plate with positive charge, the charge on the plate reduces, so $I = -dQ/dt$. Thus the differential equation can be rewritten

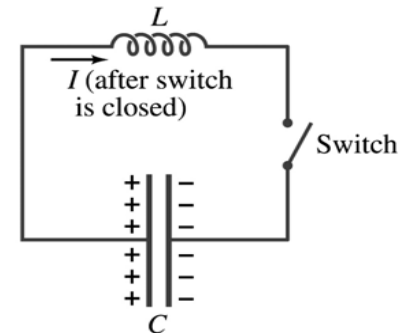

$$\frac{d^2 Q}{dt^2} + \frac{Q}{LC} = 0$$

LC Circuit and EM Oscillations

- This equation looks the same as that of the harmonic oscillation
 - So the solution for this second order differential equation is
 - $Q = Q_0 \cos(\omega t + \phi)$  The charge on the capacitor oscillates sinusoidally
 - Inserting the solution back into the differential equation
 - $\frac{d^2 Q}{dt^2} + \frac{Q}{LC} = -\omega^2 Q_0 \cos(\omega t + \phi) + Q_0 \cos(\omega t + \phi)/LC = 0$
 - Solving this equation for ω , we obtain $\omega = 2\pi f = 1/\sqrt{LC}$
 - The current in the inductor is
 - $I = -dQ/dt = \omega Q_0 \sin(\omega t + \phi) = I_0 \sin(\omega t + \phi)$
 - So the current also is sinusoidal with the maximum value

$$I_0 = \omega Q_0 = Q_0 / \sqrt{LC}$$




Energies in LC Circuit & EM Oscillation

- The energy stored in the electric field of the capacitor at any time t is $U_E = \frac{1}{2} \frac{Q^2}{C} = \frac{Q_0^2}{2C} \cos^2(\omega t + \phi)$
- The energy stored in the magnetic field in the inductor at the same instant is $U_B = \frac{1}{2} LI^2 = \frac{Q_0^2}{2C} \sin^2(\omega t + \phi)$
- Thus, the total energy in LC circuit at any instant is
$$U = U_E + U_B = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} LI^2 = \frac{Q_0^2}{2C} [\cos^2(\omega t + \phi) + \sin^2(\omega t + \phi)] = \frac{Q_0^2}{2C}$$
- So the total EM energy is constant and is conserved.
- This LC circuit is an LC oscillator or EM oscillator
 - The charge Q oscillates back and forth, from one plate of the capacitor to the other
 - The current also oscillates back and forth as well




LC Circuit Behaviors


$$Q = Q_0 \cos(\omega t)$$

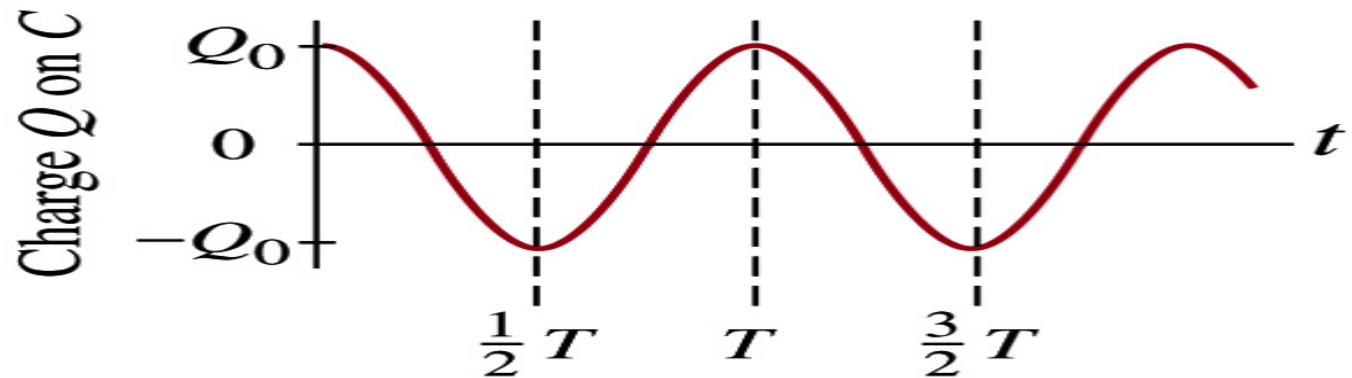

$$I = \omega Q_0 \sin(\omega t)$$

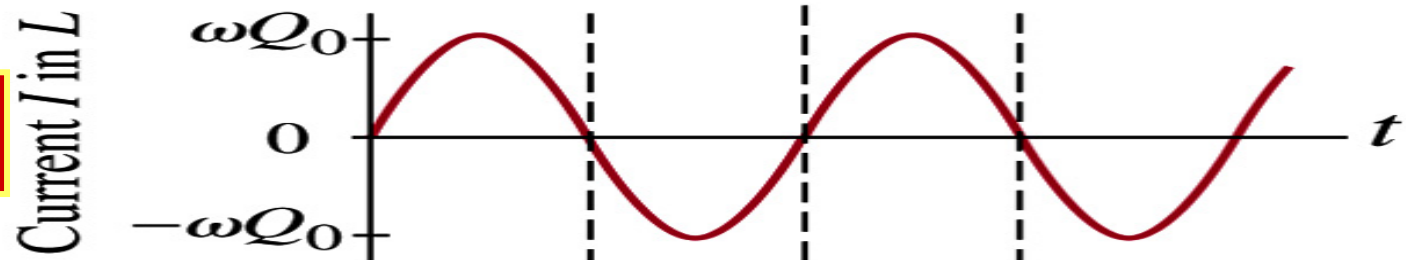

$$U = \frac{Q_0^2}{2C}$$

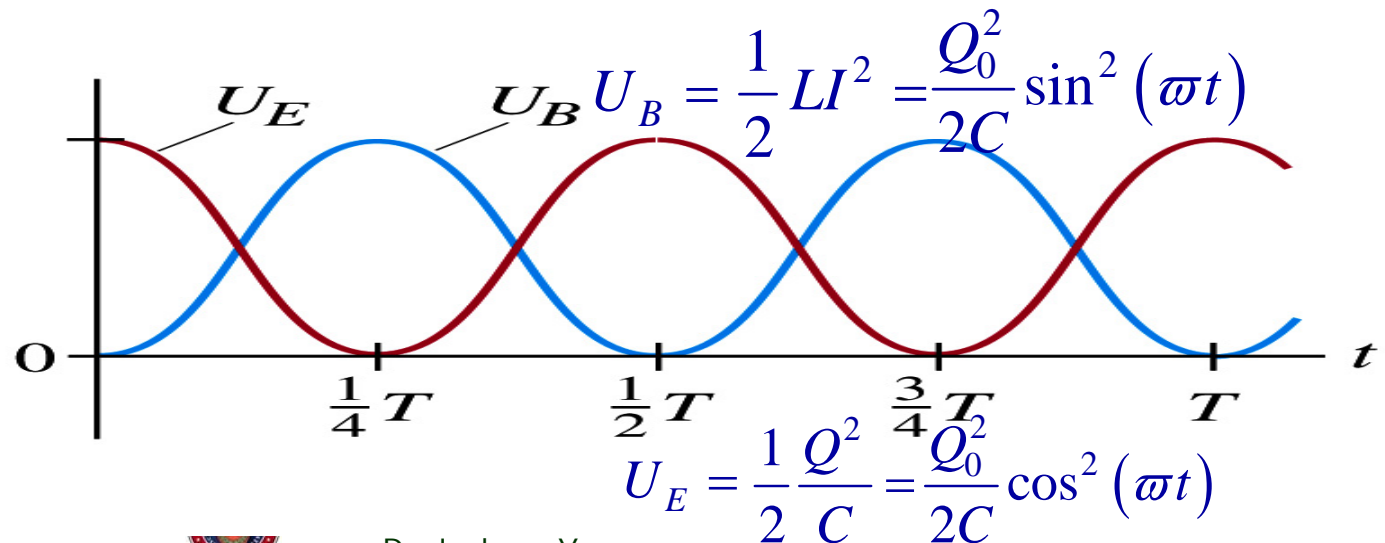

Wednesday, Apr. 19,



Dr. Jaehoon Yu

Example 30 – 7

LC Circuit. A 1200-pF capacitor is fully charged by a 500-V dc power supply. It is disconnected from the power supply and is connected, at $t=0$, to a 75-mH inductor. Determine: (a) The initial charge on the capacitor, (b) the maximum current, (c) the frequency f and period T of oscillation; and (d) the total energy oscillating in the system.

(a) The 500-V power supply, charges the capacitor to

$$Q = CV = (1200 \times 10^{-12} \text{ F}) \cdot 500 \text{ V} = 6.0 \times 10^{-7} \text{ C}$$

(b) The maximum current is $I_{\max} = \omega Q_0 = \frac{Q_0}{\sqrt{LC}} = \frac{6.0 \times 10^{-7} \text{ C}}{\sqrt{75 \times 10^{-3} \text{ H} \times 1.2 \times 10^{-9} \text{ F}}} = 63 \text{ mA}$

(c) The frequency is $f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{7.5 \times 10^{-3} \text{ H} \cdot 1.2 \times 10^{-9} \text{ F}}} = 1.7 \times 10^3 \text{ Hz}$


The period is $T = \frac{1}{f} = 6.0 \times 10^{-5} \text{ s}$

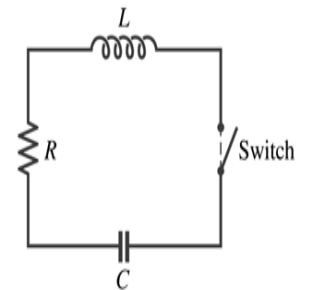(d) The total energy in the system $U = \frac{Q_0^2}{2C} = \frac{(6.0 \times 10^{-7} \text{ C})^2}{2 \cdot 1.2 \times 10^{-9} \text{ F}} = 1.5 \times 10^{-4} \text{ J}$



LC Oscillations w/ Resistance (LRC circuit)

- There is no such thing as zero resistance coil so all LC circuits have some resistance
 - So to be more realistic, the effect of the resistance should be taken into account
 - Suppose the capacitor is charged up to Q_0 initially and the switch is closed in the circuit at $t=0$
 - What do you expect to happen to the energy in the circuit?
 - Well, due to the resistance we expect some energy will be lost through the resistor via a thermal conversion
 - What about the oscillation? Will it look the same as the ideal LC circuit we dealt with?
 - No? OK then how would it be different?
 - The oscillation would be damped due to the energy loss.



LC Oscillations w/ Resistance (LRC circuit)

- Now let's do some analysis
- From Kirchhoff's loop rule, we obtain
- Since $I=dQ/dt$, the equation becomes

$$-L \frac{dI}{dt} - IR + \frac{Q}{C} = 0$$

$$-L \frac{d^2 Q}{dt^2} - R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

– Which is identical to that of a damped oscillator

- The solution of the equation is $Q = Q_0 e^{-\frac{R}{2L}t} \cos(\omega' t + \phi)$

– Where the angular frequency is $\omega' = \sqrt{1/LC - R^2/4L^2}$

- $R^2 < 4L/C$: Underdamped
- $R^2 > 4L/C$: Overdamped

