

PHYS 1444 – Section 501

Lecture #22

Monday, Apr. 24, 2006

Dr. Jaehoon Yu

- AC Circuit w/ Resistance only
- AC Circuit w/ Inductance only
- AC Circuit w/ Capacitance only
- AC Circuit w/ LRC



Announcements

- Colloquium at 4pm this Wednesday, Apr. 26
 - Dr. Ian Hinchliffe from LBL
 - Title: "Early Physics with ATLAS at LHC"
 - Location: Planetarium
- Reading assignments
 - CH. 31 – 6, 31 – 7 and 31 – 8
- Final term exam
 - Time: 5:30pm – 7:00pm, Monday May. 8
 - Location: SH103
 - Covers: CH 29 – whichever chapter we finish Monday, May 1
 - Please do not miss the exam
 - Two best of the three exams will be used for your grades



Why do we care about circuits on AC?

- The circuits we've learned so far contain resistors, capacitors and inductors and have been connected to a DC source or a fully charged capacitor
 - What? This does not make sense.
 - The inductor does not work as an impedance unless the current is changing. So an inductor in a circuit with DC source does not make sense.
 - Well, actually it does. When does it impede the current flow?
 - Immediately after the circuit is connected to the source so the current is still changing.
 - So what?
 - It causes the change of magnetic flux.
 - Now does it make sense?
- Anyhow, learning the responses of resistors, capacitors and inductors in a circuit connected to an AC emf source is important. Why is this?
 - Since most the generators produce sinusoidal current
 - Any voltage that varies over time can be expressed in the superposition of sine and cosine functions



AC Circuits – the preamble

- Do you remember how the rms and peak values for current and voltage are related?

$$V_{rms} = \frac{V_0}{\sqrt{2}} \qquad I_{rms} = \frac{I_0}{\sqrt{2}}$$

- The symbol for an AC power source is



- We assume that the voltage gives rise to current

$$I = I_0 \sin 2\pi ft = I_0 \sin \omega t$$

– where $\omega = 2\pi f$

AC Circuit w/ Resistance only

- What do you think will happen when an ac source is connected to a resistor?
- From Kirchhoff's loop rule, we obtain

$$V - IR = 0$$


- Thus

$$V = I_0 R \sin \omega t = V_0 \sin \omega t$$

– where $V_0 = I_0 R$

- What does this mean?

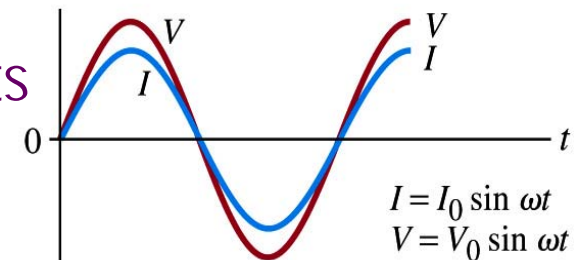- Current is 0 when voltage is 0 and current is in its peak when voltage is in its peak.
- Current and voltage are “in phase”



- Energy is lost via the transformation into heat at an average rate $\bar{P} = \bar{I} \bar{V} = I_{rms}^2 R = V_{rms}^2 / R$

AC Circuit w/ Inductance only

- From Kirchhoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus

$$V = L \frac{dI}{dt} = L \frac{d(I_0 \sin \omega t)}{dt} = \omega L I_0 \cos \omega t$$

- Using the identity $\cos \theta = \sin(\theta + 90^\circ)$

- $V = \omega L I_0 \sin(\omega t + 90^\circ) = V_0 \sin(\omega t + 90^\circ)$



- where $V_0 = \omega L I_0$

- What does this mean?

- Current and voltage are “out of phase by $\pi/2$ or 90° ”.
- In other words the current reaches its peak $\frac{1}{4}$ cycle after the voltage

- What happens to the energy?

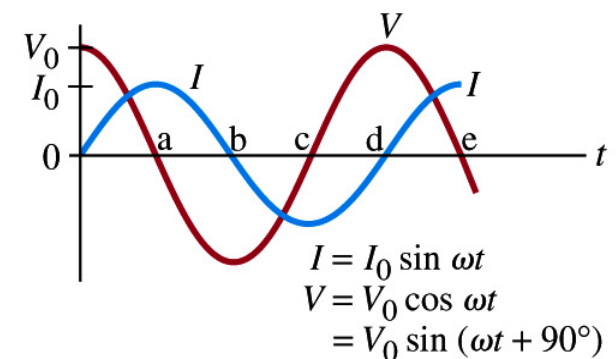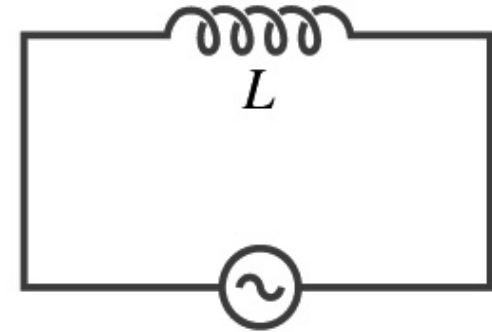- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the magnetic field
- Then released back to the source



Monday, Apr. 24, 2006



PHYS 1444-001, Spring 2
Dr. Jaehoon Yu

AC Circuit w/ Inductance only

- How are the resistor and inductor different in terms of energy?
 - Inductor Stores the energy temporarily in the magnetic field and then releases it back to the emf source
 - Resistor Does not store energy but transforms it to thermal energy, getting it lost to the environment
- How are they the same?
 - They both impede the flow of charge
 - For a resistance R , the peak voltage and current are related to $V_0 = I_0 R$
 - Similarly, for an inductor we can write $V_0 = I_0 X_L$
 - Where X_L is the inductive reactance of the inductor $X_L = \omega L$ 0 when $\omega=0$.
 - What do you think is the unit of the reactance? Ω
 - The relationship $V_0 = I_0 X_L$ is not valid at a particular instance. Why not?
 - Since V_0 and I_0 do not occur at the same time



$$V_{rms} = I_{rms} X_L$$

Example 31 – 1

Reactance of a coil. A coil has a resistance $R=1.00\Omega$ and an inductance of 0.300H . Determine the current in the coil if (a) 120 V dc is applied to it; (b) 120 V ac (rms) at 60.0Hz is applied.

Is there a reactance for dc? Nope. Why not? Since $\omega=0$, $X_L = \omega L = 0$

So for dc power, the current is from Kirchhoff's rule $V - IR = 0$

$$I_0 = \frac{V_0}{R} = \frac{120\text{V}}{1.00\Omega} = 120\text{A}$$

For an ac power with $f=60\text{Hz}$, the reactance is

$$X_L = \omega L = 2\pi fL = 2\pi \cdot (60.0\text{s}^{-1}) \cdot 0.300\text{H} = 113\Omega$$


Since the resistance can be ignored compared to the reactance, the rms current is

$$I_{rms} \approx \frac{V_{rms}}{X_L} = \frac{120\text{V}}{113\Omega} = 1.06\text{A}$$



AC Circuit w/ Capacitance only

- What happens when a capacitor is connected to a dc power source?
 - The capacitor quickly charges up.
 - There is no steady current flow in the circuit
 - Since a capacitor prevents the flow of a dc current
- What do you think will happen if it is connected to an ac power source?
 - The current flows continuously. Why?
 - When the ac power turns on, charge begins to flow one direction, charging up the plates
 - When the direction of the power reverses, the charge flows in the opposite direction

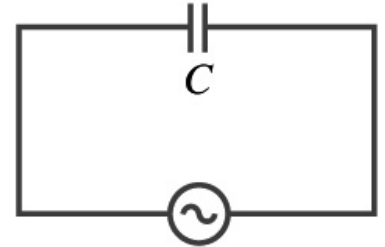

AC Circuit w/ Capacitance only

- From Kirchhoff's loop rule, we obtain

$$V = \frac{Q}{C}$$

- Current at any instance is $I = \frac{dQ}{dt} = I_0 \sin \omega t$

- Thus, the charge Q on the plate at any instance is

$$Q = \int_{Q=0}^Q dQ = \int_{t=0}^t I_0 \sin \omega t dt = -\frac{I_0}{\omega} \cos \omega t$$

- The voltage across the capacitor is


$$V = \frac{Q}{C} = -I_0 \frac{1}{\omega C} \cos \omega t$$

- Using the identity $\cos \theta = -\sin(\theta - 90^\circ)$

$$V = I_0 \frac{1}{\omega C} \sin(\omega t - 90^\circ) = V_0 \sin(\omega t - 90^\circ)$$


- Where

- $V_0 = \frac{I_0}{\omega C}$

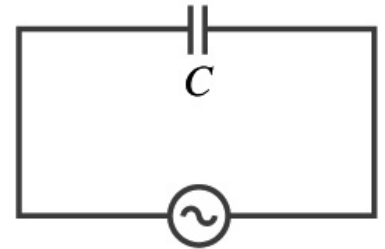

AC Circuit w/ Capacitance only

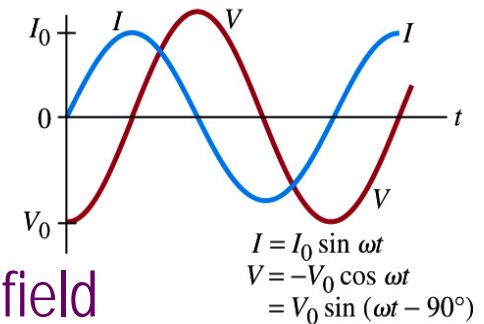- So the voltage is $V = V_0 \sin(\omega t - 90^\circ)$
- What does this mean?
 - Current and voltage are “out of phase by $\pi/2$ or 90° ” but in this case, the voltage reaches its peak $\frac{1}{4}$ cycle after the current




- What happens to the energy?
 - No energy is dissipated
 - The average power is 0 at all times
 - The energy is stored temporarily in the electric field
 - Then released back to the source
- Relationship between the peak voltage and the peak current in the capacitor can be written as $V_0 = I_0 X_C$
 - Where the capacitance reactance X_C is defined as $X_C = \frac{1}{\omega C}$
 - Again, this relationship is only valid for rms quantities

Infinite
when
 $\omega=0$.

$$V_{rms} = I_{rms} X_C$$

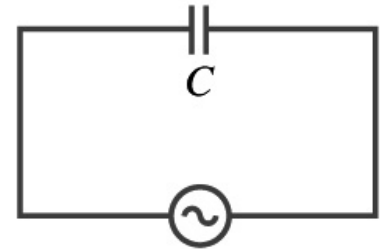Example 31 – 2

Capacitor reactance. What are the peak and rms current in the circuit in the figure if $C=1.0\mu\text{F}$ and $V_{\text{rms}}=120\text{V}$? Calculate for (a) $f=60\text{Hz}$, and then for (b) $f=6.0\times 10^5\text{Hz}$.



The peak voltage is $V_0 = \sqrt{2}V_{\text{rms}} = 120\text{V} \cdot \sqrt{2} = 170\text{V}$

The capacitance reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot (60\text{s}^{-1}) \cdot 1.0 \times 10^{-6}\text{F}} = 2.7\text{k}\Omega$$

Thus the peak current is


$$I_0 = \frac{V_0}{X_C} = \frac{170\text{V}}{2.7\text{k}\Omega} = 63\text{mA}$$

The rms current is

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120\text{V}}{2.7\text{k}\Omega} = 44\text{mA}$$


AC Circuit w/ LRC

- The voltage across each element is
 - V_R is in phase with the current
 - V_L leads the current by 90°
 - V_C lags the current by 90°
- From Kirchhoff's loop rule
- $V = V_R + V_L + V_C$
 - However since they do not reach the peak voltage at the same time, the peak voltage of the source V_0 will not equal $V_{R0} + V_{L0} + V_{C0}$
 - The rms voltage also will not be the simple sum of the three
- Let's try to find the total impedance, peak current I_0 and the phase difference between I_0 and V_0 .

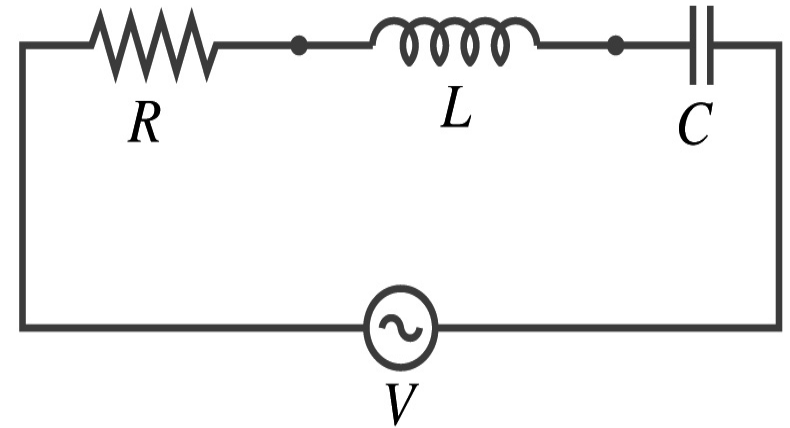

AC Circuit w/ LRC

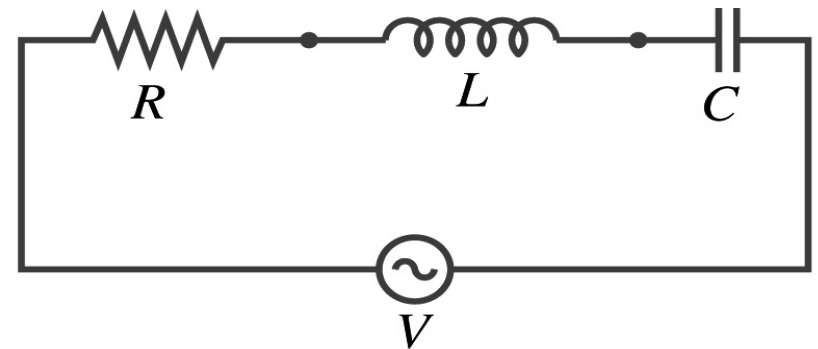- The current at any instance is the same at all point in the circuit
 - The currents in each elements are in phase
 - Why?
 - Since the elements are in series
 - How about the voltage?
 - They are not in phase.





- The current at any given time is

$$I = I_0 \sin \omega t$$

- The analysis of LRC circuit is done using the “phasor” diagram in which arrows are drawn in an xy plane to represent the amplitude of each voltage, just like vectors
 - The lengths of the arrows represent the magnitudes of the peak voltages across each element; $V_{R0} = I_0 R$, $V_{L0} = I_0 X_L$ and $V_{C0} = I_0 X_C$
 - The angle of each arrow represents the phase of each voltage relative to the current, and the arrows rotate at the angular frequency ω to take into account the time dependence.
 - The projection of each arrow on y axis represents voltage across each element at any given time

Phasor Diagrams

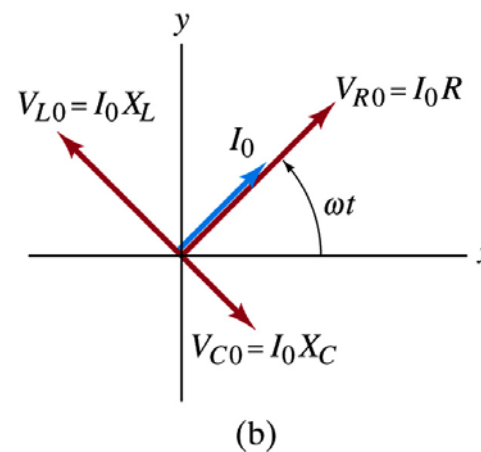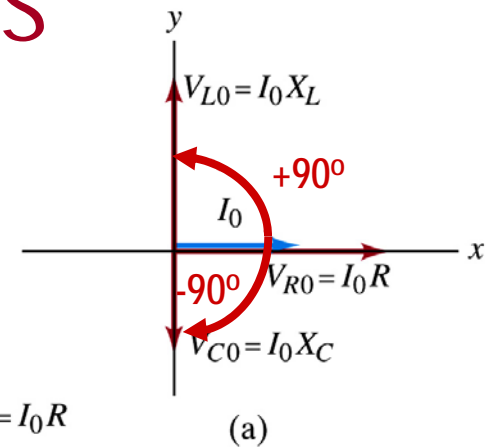- At $t=0$, $I=0$.
 - Thus $V_{R0}=0$, $V_{L0}=I_0X_L$, $V_{C0}=I_0X_C$
- At $t=t$, $I = I_0 \sin \omega t$




- Thus, the voltages (y-projections) are

$$V_R = V_{R0} \sin \omega t$$

$$V_L = V_{L0} \sin(\omega t + 90^\circ)$$
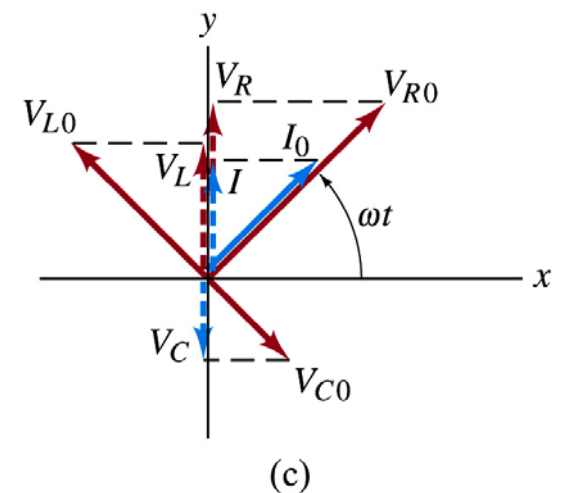
$$V_C = V_{C0} \sin(\omega t - 90^\circ)$$




Monday, Apr. 24, 2006



PHYS 1444-501, Spring 2006
Dr. Jaehoon Yu

AC Circuit w/ LRC

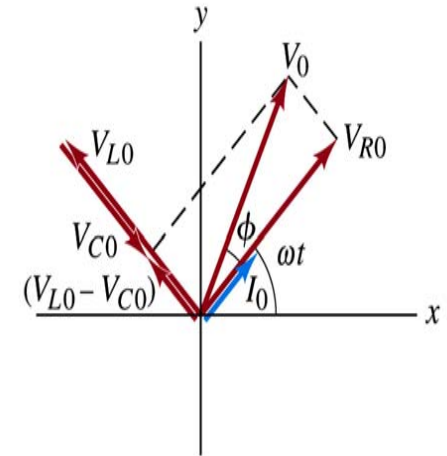- Since the sum of the projections of the three vectors on the y axis is equal to the projection of their sum,
 - The sum of the projections represents the instantaneous voltage across the whole circuit which is the source voltage
 - So we can use the sum of all vectors as the representation of the peak source voltage V_0 .



- V_0 forms an angle ϕ to V_{R0} and rotates together with the other vectors as a function of time, $V = V_0 \sin(\omega t + \phi)$
- We determine the total impedance Z of the circuit defined by the relationship $V_{rms} = I_{rms} Z$ or $V_0 = I_0 Z$
- From Pythagorean theorem, we obtain

$$V_0 = \sqrt{V_{R0}^2 + (V_{L0} - V_{C0})^2} = \sqrt{I_0^2 R^2 + I_0^2 (X_L - X_C)^2} = I_0 \sqrt{R^2 + (X_L - X_C)^2} = I_0 Z$$

- Thus the total impedance is $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$

AC Circuit w/ LRC

- The phase angle ϕ is

$$\tan \phi = \frac{V_{L0} - V_{C0}}{V_{R0}} = \frac{I_0 (X_L - X_C)}{I_0 R} = \frac{(X_L - X_C)}{R}$$

- or

$$\cos \phi = \frac{V_{R0}}{V_0} = \frac{I_0 R}{I_0 Z} = \frac{R}{Z}$$

- What is the power dissipated in the circuit?

- Which element dissipates the power?
- Only the resistor

- The average power is $\bar{P} = I_{rms}^2 R$

- Since $R = Z \cos \phi$

- We obtain $\bar{P} = I_{rms}^2 Z \cos \phi = I_{rms} V_{rms} \cos \phi$

- The factor $\cos \phi$ is referred as the power factor of the circuit

- For a pure resistor, $\cos \phi = 1$ and $\bar{P} = I_{rms} V_{rms}$

- For a capacitor or inductor alone $\phi = -90^\circ$ or $+90^\circ$, so $\cos \phi = 0$ and $\bar{P} = 0$.

