

PHYS 1442 – Section 001

Lecture #7

Thursday, June 13, 2013

Dr. Jaehoon Yu

- Chapter 18
 - Electric Power
 - Alternating Current
 - Power Delivered by AC
 - Microscopic View of Electric Current
 - Ohm's Law in Microscopic View
 - Superconductivity
- Chapter 19
 - EMF and Terminal Voltage
 - Resistors in Series and Parallel

Today's homework is homework #4, due 11pm, Tuesday, June 18!!

Thursday, June 13, 2013



PHYS 1442-001, Summer 2013

Dr. Jaehoon Yu

Announcements

- Term exam results
 - Class average: 48.5/92
 - Equivalent to 52.7/100
 - Top score: 76/92
 - Remember this exam is 12% and can be replaced by the next term exam!
 - Homework takes the largest portion of the grade at 25%!
 - Mid term (20%) and final exams (23%) will be comprehensive!
- Second quiz, Monday, June 17
 - Covers CH17.9 through what we finish today (CH19.2?)
- Mid-term exam
 - Wednesday, June 19
 - Comprehensive exam
 - Covers CH16.1 – what we finish Tuesday, June 18 plus Appendices A1 – A8
- Quest payment of \$25 each
 - Deadline is June 14.
 - If not paid, your homework access will be disabled.

Thursday, June 13, 2013



PHYS 1442-001, Summer 2013
Dr. Jaehoon Yu

Special Project #3

- Make a list of the power consumption and the resistance of all electric and electronic devices at your home and compiled them in a table. (5 points total for the first 10 items and 0.25 points each additional item.)
- Estimate the cost of electricity for each of the items on the table using your own electric cost per kWh (if you don't find your own, use \$0.12/kWh) and put them in the relevant column. (2 points total for the first 10 items and 0.1 points each additional items)
- Estimate the the total amount of energy in Joules and the total electricity cost per day, per month and per year for your home. (6 points)
- Due: Beginning of the class Thursday, June 20

Thursday, June 13, 2013



PHYS 1442-001, Summer 2013
Dr. Jaehoon Yu

How does an electric heater work?

- Electrons flow through a circuit that includes the heater under a potential difference.
- Flowing electrons collide with the vibrating atoms in the wire.
- In each collision, part of electron's kinetic energy is transferred to the atom it collides with.
- The kinetic energy of wire's atoms increases, and thus the temperature of the wire increases.
- The increased thermal energy can be transferred as heat through conduction and convection to the air.
- So then what happens to the electrons that lost their kinetic energy?
 - Since they are still under potential difference, they will still flow to the other side of the electrode, gaining kinetic energy!



Electric Power

- Why is the electric energy useful?
 - It can transform into different forms of energy easily.
 - Motors, pumps, etc, transform electric energy to mechanical energy
 - Heaters, dryers, cook-tops, etc, transform electricity to thermal energy
 - Light bulb filament transforms electric energy to optical energy
 - Only about 10% of the energy turns to light and the 90% lost via heat
 - Typical household light bulb and heating elements have resistance of order few ohms to few hundred of ohms
- How does the electric energy transforms to thermal energy (toaster)?
 - Flowing electrons collide with the vibrating atoms of the wire.
 - In each collision, part of electron's kinetic energy is transferred to the atom it collides with.
 - The kinetic energy of wire's atoms increases, and thus the temperature of the wire increases.
 - The increased thermal energy can be transferred as heat through conduction and convection to the air in a heater or to food on a pan, through radiation to bread in a toaster or radiated as light.




Electric Power

- How do we find out the power transformed by an electric device?
 - What is definition of power?
 - The rate at which the work is done or the energy is transformed
- What is the energy transformed when an infinitesimal charge Δq moves through a potential difference V ?
 - $\Delta U = V\Delta q$
 - If Δt is the time required for an amount of charge Δq to move through the potential difference V , the power P is
 - $P = \Delta U / \Delta t = V \Delta q / \Delta t$ ← **What is this?**
 - Thus, we obtain $P = VI$. In terms of resistance $P = I^2 R = \frac{V^2}{R}$
 - What is the unit? **Watts = J/s**
 - What kind of quantity is the electrical power?
 - Scalar
 - $P = IV$ can apply to any devices while the formula with resistance can only apply to resistors.

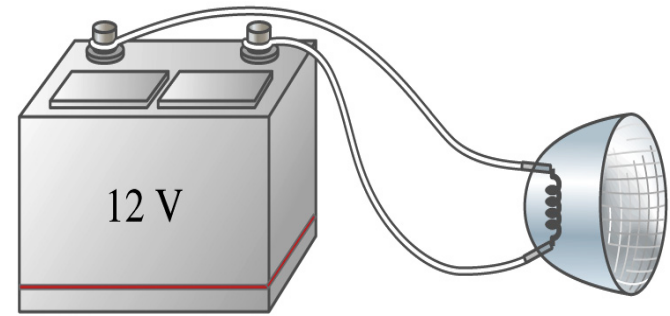Example 18 – 8

Headlights: Calculate the resistance of a 40-W automobile headlight designed for 12V.



40-W Headlight

Since the power is 40W and the voltage is 12V, we use the formula with V and R.




$$P = \frac{V^2}{R}$$

Solve for R

$$R = \frac{V^2}{P} = \frac{(12V)^2}{40W} = 3.6\Omega$$

Power in Household Circuits

- Household devices usually have small resistance
 - But since they draw current, if they become large enough, wires can heat up (overloaded)
 - Why is using thicker wires safer?
 - Thicker wires have less resistance, lower heat
 - Overloaded wire can set off a fire at home
 - How do we prevent this?
 - Put in a switch that would disconnect the circuit when overloaded
 - Fuse or circuit breakers
 - They open up the circuit when the current is over certain value

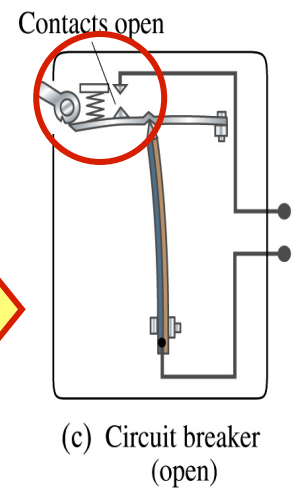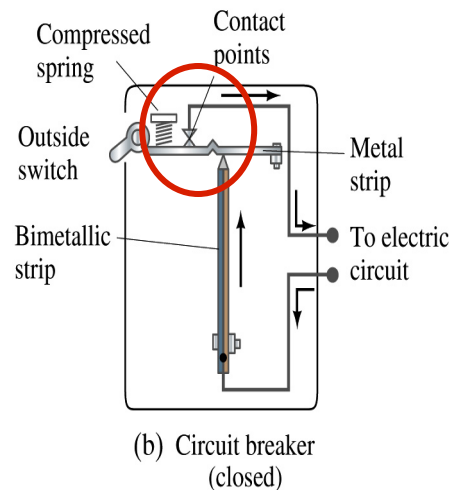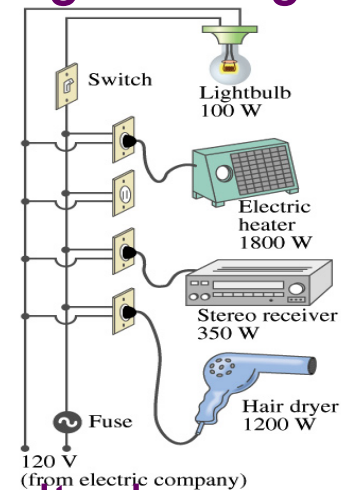


Example 18 – 11

Will the fuse blow?: Calculate
Determine the total current drawn
by all the devices in the circuit in
the figure.

The total current is the sum of current
drawn by individual device.
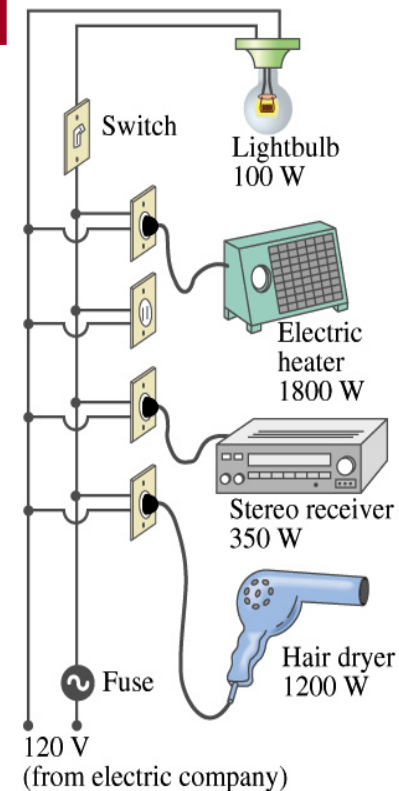
$$P = IV \quad \text{Solve for } I \quad I = P/V$$



Bulb $I_B = 100W/120V = 0.8A$

Heater $I_H = 1800W/120V = 15.0A$

Stereo $I_S = 350W/120V = 2.9A$

Dryer $I_D = 1200W/120V = 10.0A$



Total current

$$I_T = I_B + I_H + I_S + I_D = 0.8A + 15.0A + 2.9A + 10.0A = 28.7A$$

What is the total power? $P_T = P_B + P_H + P_S + P_D = 100W + 1800W + 350W + 1200W = 3450W$

Alternating Current

- Does the direction of the flow of current change when a battery is connected to a circuit?
 - No. Why?
 - Because its source of potential difference stays put.
 - This kind of current is called the Direct Current (DC), and it does not change its direction of flow.
 - How would DC look as a function of time?
 - A straight line
- Electric generators at electric power plant produce alternating current (AC)
 - AC reverses direction many times a second
 - AC is sinusoidal as a function of time
- Most the currents supplied to homes and business are AC.

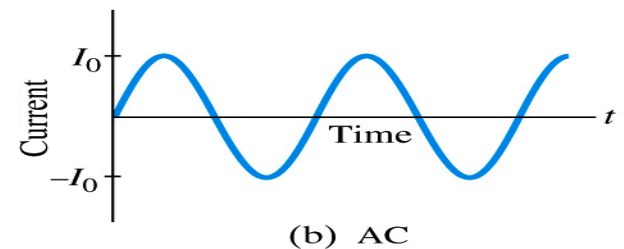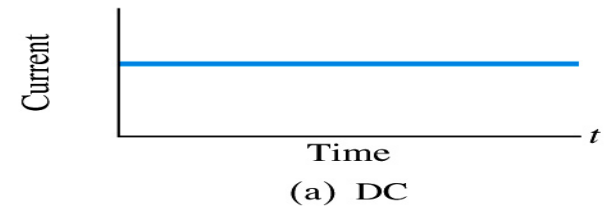

Thursday, June 13, 2013




PHYS 1442-001, Sumr
Dr. Jaehoon Yi

Alternating Current


- The voltage produced by an AC electric generator is sinusoidal

- This is why the current is sinusoidal

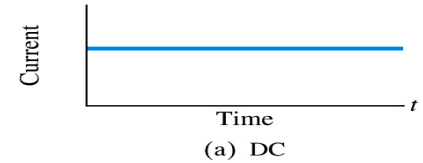

- Voltage produced can be written as
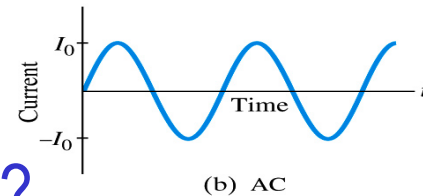
$$V = V_0 \sin 2\pi ft = V_0 \sin \omega t$$



- What are the maximum and minimum voltages?

- V_0 and $-V_0$

- The potential oscillates between $+V_0$ and $-V_0$, the peak voltages or the amplitude

- What is f ?

- The frequency, the number of complete oscillations made per second. What is the unit of f ? What is the normal size of f in the US?

- $f=60\text{Hz}$ (1/sec) in the US and Canada.

- Many European countries have $f=50\text{Hz}$.

- $\omega=2\pi f$



Alternating Current

- Since $V=IR$, if the voltage V exists across a resistance R , the current I is

$$I = \frac{V}{R} = \frac{V_0}{R} \sin 2\pi ft = I_0 \sin \omega t$$


What is this?

- What are the maximum and minimum currents?
 - I_0 and $-I_0$
 - The current oscillates between $+I_0$ and $-I_0$, the peak currents or amplitude. The current is positive when electron flows to one direction and negative when they flow opposite.
 - AC is as many times positive as negative. What's the average current?
 - Zero. So there is no power and no heat is produced in a heater?
 - Yes there is! The electrons actually flow back and forth, so power is delivered.

Power Delivered by Alternating Current

- AC power delivered to a resistance is:

$$P = I^2 R = I_0^2 R \sin^2 \omega t$$

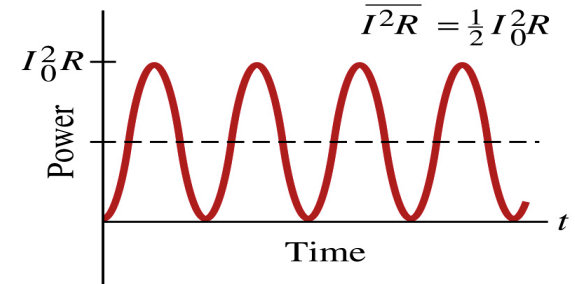

- Since the current is squared, the power is always positive

- The average power delivered is $\bar{P} = \frac{1}{2} I_0^2 R$

- Since the power is also $P = V^2 / R$, we can obtain

$$P = \left(V_0^2 / R \right) \sin^2 \omega t$$

Average power

$$\bar{P} = \frac{1}{2} \left(\frac{V_0^2}{R} \right)$$

- The average of the square of current and voltage are important in calculating power:

$$\overline{I^2} = \frac{1}{2} I_0^2$$

$$\overline{V^2} = \frac{1}{2} V_0^2$$

Power Delivered by Alternating Current

- The square root of each of these are called root-mean-square, or rms:

$$I_{rms} = \sqrt{I^2} = \frac{I_0}{\sqrt{2}} = 0.707 I_0$$

$$V_{rms} = \sqrt{V^2} = \frac{V_0}{\sqrt{2}} = 0.707 V_0$$

- rms values are sometimes called effective values
 - These are useful quantities since they can substitute current and voltage directly in power, as if they are in DC

$$\bar{P} = \frac{1}{2} I_0^2 R = I_{rms}^2 R$$

$$\bar{P} = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{rms}^2}{R}$$


$$\bar{P} = I_{rms} V_{rms}$$

- In other words, an AC of peak voltage V_0 or peak current I_0 produces as much power as DC voltage V_{rms} or DC current I_{rms} .
- So normally, rms values in AC are specified or measured.
 - US uses 115V rms voltage. What is the peak voltage?
 - $V_0 = \sqrt{2} V_{rms} = \sqrt{2} \cdot 115V = 162.6V$
 - Europe uses 240V
 - $V_0 = \sqrt{2} V_{rms} = \sqrt{2} \cdot 240V = 340V$



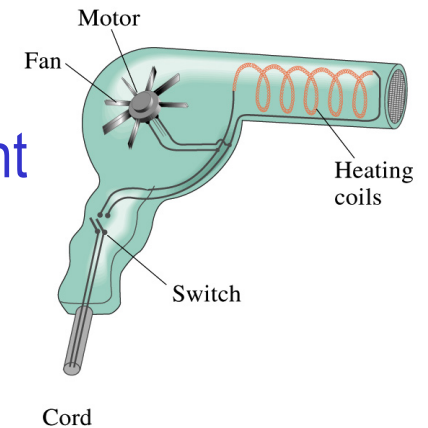Example 18 – 12

Hair Dryer. (a) Calculate the resistance and the peak current in a 1000-W hair dryer connected to a 120-V AC line. (b) What happens if it is connected to a 240-V line in Britain?



The rms current is:
$$I_{rms} = \frac{\bar{P}}{V_{rms}} = \frac{1000W}{120V} = 8.33A$$

The peak current is:
$$I_0 = \sqrt{2}I_{rms} = \sqrt{2} \cdot 8.33A = 11.8A$$

Thus the resistance is:
$$R = \frac{\bar{P}}{I_{rms}^2} = \frac{1000W}{(8.33A)^2} = 14.4\Omega$$

(b) If connected to 240V in Britain ...


The average power provide by the AC in UK is

$$\bar{P} = \frac{V_{rms}^2}{R} = \frac{(240V)^2}{14.4\Omega} = 4000W$$

So? The heating coils in the dryer will melt!

Microscopic View of Electric Current

- When a potential difference is applied to the two ends of a wire w/ a uniform cross-section, the direction of the electric field is parallel to the walls of the wire, this is possible since the charges are moving
- Let's define a microscopic vector quantity, the current density $\mathbf{j}$, the electric current per unit cross-sectional area
 - $\mathbf{j} = I/A$ or $I = jA$ if the current density is uniform
 - If not uniform $I = \int \vec{j} \cdot d\vec{A}$
 - The direction of $\mathbf{j}$ is the direction the positive charge would move when placed at that position, generally the same as that of $\mathbf{E}$
- The current density exists on any point in space while the current I refers to a conductor as a whole so it's macroscopic

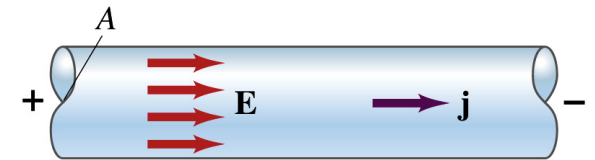


Microscopic View of Electric Current

- The direction of $\mathbf{j}$ is the direction of a positive charge. So in a conductor, since negatively charged electrons move, the direction is $-\mathbf{j}$.
- Let's think about the current in a microscopic view again:
 - When voltage is applied to the ends of a wire
 - Electric field is generated by the potential difference
 - Electrons feel force and get accelerated
 - Electrons soon reach to a steady average velocity due to collisions with atoms in the wire, called drift velocity, $\mathbf{v}_d$
 - The drift velocity is normally much smaller than the electrons' average random speed.

Thursday, June 13, 2013



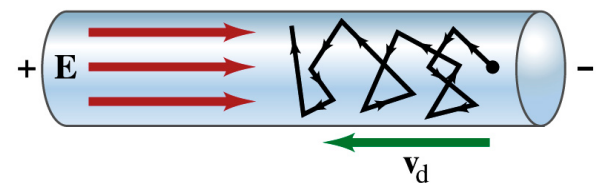PHYS 1442-001, Summer 2013
Dr. Jaehoon Yu



Microscopic View of Electric Current

- The drift velocity of electrons in a wire is only about 0.05mm/s. How could we get light turned on immediately then?
 - While the electrons in a wire travels slow, the electric field travels essentially at the speed of light. Then what is all the talk about electrons flowing through?
 - It is just like water. When you turn on the facet, water flows right off the facet despite the fact that the water travels slow.
 - Electricity is the same. Electrons fill the conductor wire and when the switch is flipped on or a potential difference is applied, the electrons closed to the positive terminal flows into the bulb.
 - Interesting, isn't it? Why is the field travel at the speed of light then?



Ohm's Law in Microscopic View

- Ohm's law can be written in microscopic quantities.
 - Resistance in terms of resistivity is $R = \rho \frac{l}{A}$
 - We can rewrite V and I as: $I = jA$, $V = El$
 - If electric field is uniform, from $V = IR$, we obtain
 - $V = IR$
 - $El = (jA) \left(\rho \frac{l}{A} \right) = j\rho l$
 - So $j = \frac{E}{\rho} = \sigma E$
 - In a metal conductor, ρ or σ does not depend on V , thus, the current density $\mathbf{j}$ is proportional to the electric field $\mathbf{E} \rightarrow$
Microscopic statement of Ohm's Law
 - In vector form, the density can be written as $\vec{j} = \frac{\vec{E}}{\rho} = \sigma \vec{E}$