

PHYS 1442 – Section 001

Lecture #9

Tuesday, June 18, 2013

Dr. Jaehoon Yu

- Chapter 19
 - Kirchhoff's Rules
 - EMFs in Series and Parallel
 - Capacitors in Series and Parallel
 - RC Circuit
- Chapter 20
 - Magnets and Magnetic Field
 - Electric Current and Magnetism
 - Magnetic Forces on Electric Current

Today's homework is homework #5, due 11pm, Monday, June 24!! ¹

Announcements

- Quiz results
 - Class average: 58.1/95
 - Equivalent to 61.2/100
 - Previous result 51.7/100
 - Top score: 87/95
- Mid-term exam
 - Tomorrow, Wednesday, June 19
 - Comprehensive exam
 - Covers CH16.1 – what we finish today (CH20.1?) plus Appendices A1 – A8
- Mid-term grade discussion
 - Between 2 – 3:30 pm this Friday, June 21
 - In Dr. Yu's office (CPB342)



Special Project #3

- Make a list of the power consumption and the resistance of all electric and electronic devices at your home and compiled them in a table. (5 points total for the first 10 items and 0.25 points each additional item.)
- Estimate the cost of electricity for each of the items on the table using your own electric cost per kWh (if you don't find your own, use \$0.12/kWh) and put them in the relevant column. (2 points total for the first 10 items and 0.1 points each additional items)
- Estimate the the total amount of energy in Joules and the total electricity cost per day, per month and per year for your home. (6 points)
- Due: Beginning of the class Thursday, June 20
 - Print the entire width of the table to be contained in one page!!




Spread Sheet

Item Name	Rated power (W)	Number of devices	Number of Hours per day	Daily Power Consumption (kWh)	Energy Cost per kWh (cents)	Daily Energy Consumption (J).	Daily Energy Cost (\$)	Monthly Energy Consumption (J)	Monthly Energy Cost (\$)	Yearly Energy Consumption (J)	Yearly Energy Cost (\$)
Light Bulbs	30	4									
	40	6									
	60	15									
Heaters	1000	2									
	1500	1									
	2000	1									
Fans											
Air Conditioners											
Fridgers, Freezers											
Computers (desktop, laptop, ipad)											
Game consoles											
Total				0		0	0	0	0	0	0



Kirchhoff's Rules – 1st Rule

- Some circuits are very complicated to analyze using the simple combinations of resistors
 - G. R. Kirchhoff devised two rules to deal with complicated circuits.
- Kirchhoff's rules are based on conservation of charge and energy
 - Kirchhoff's 1st rule: Junction rule, charge conservation.
 - At any junction point, the sum of all currents entering the junction must equal to the sum of all currents leaving the junction.
 - In other words, what goes in must come out.
 - At junction a in the figure, I_3 comes into the junction while I_1 and I_2 leaves: $I_3 = I_1 + I_2$

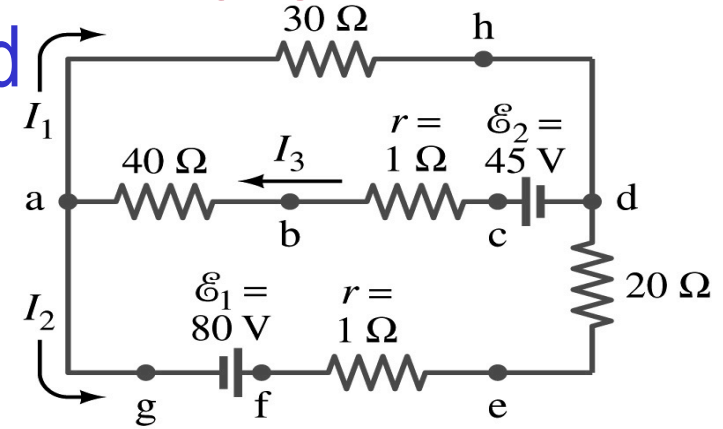

Kirchhoff's Rules – 2nd Rule

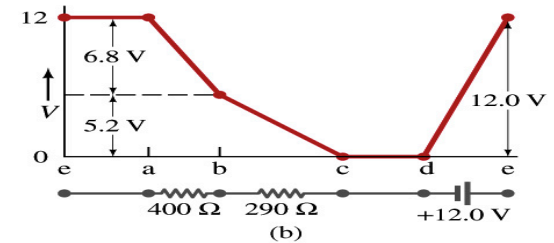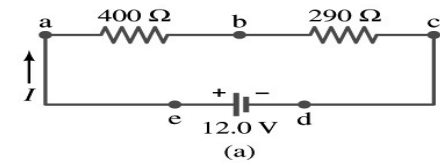- Kirchoff's 2nd rule: Loop rule, uses conservation of energy.
 - The sum of the changes in potential around any closed path of a circuit must be zero.



- The current in the circuit in the figure is $I=12/690=0.017\text{A}$.
 - Point e is the highest potential point while point d is the lowest potential.
 - When the test charge starts at e and returns to e , the total potential change is 0.
 - Between point e and a , no potential change since there is no source of potential or any resistance to drop potential.
 - Between a and b , there is a 400Ω resistance, causing $IR=0.017*400 = 6.8\text{V}$ drop.
 - Between b and c , there is a 290Ω resistance, causing $IR=0.017*290 = 5.2\text{V}$ drop.
 - Since these are voltage drops, we use negative sign for these, -6.8V and -5.2V .
 - No change between c and d while from d to e there is $+12\text{V}$ change.
 - Thus the total change of the voltage through the loop is: $-6.8\text{V}-5.2\text{V}+12\text{V}=0\text{V}$.


Using Kirchhoff's Rules

1. Determine the flow of currents at the junctions.
 - It does not matter which direction of the current you choose.
 - If the value of the current after completing the calculations are negative, you just flip the direction of the current flow.
2. Write down the current equation based on Kirchhoff's 1st rule at various junctions.
 - Be sure to see if any of them are the same.
3. Choose independent closed loops in the circuit
4. Write down the potential in each interval of the junctions, keeping the signs properly.
5. Write down the potential equations for each loop.
6. Solve the equations for unknowns.



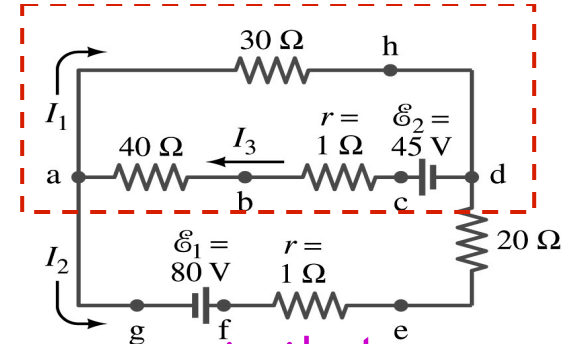Example 19 – 8

Using Kirchhoff's rules. Calculate the currents I_1 , I_2 and I_3 in each of the branches of the circuit in the figure.



The directions of the current through the circuit is not known *a priori* but since the current tends to move away from the positive terminal of a battery, we arbitrarily choose the direction of the currents as shown.

We have three unknowns so we need three equations.

Using Kirchhoff's junction rule at point a , we obtain $I_3 = I_1 + I_2$

This is the same for junction d as well, so no additional information.

Now the second rule on the loop $ahdcba$.

$$V_{ah} = -I_1 30 \quad V_{hd} = 0 \quad V_{dc} = +45 \quad V_{cb} = -I_3 \cdot 1 \quad V_{ba} = -40I_3$$

The total voltage change in loop $ahdcba$ is.


$$V_{ahdcba} = -30I_1 + 45 - I_3 - 40I_3 = 45 - 30I_1 - 41I_3 = 0$$

Example 19 – 8, cnt'd

Now the second rule on the other loop *agfedcba*.

$$V_{ag} = 0 \quad V_{gf} = +80 \quad V_{fe} = -I_2 \cdot 1 \quad V_{ed} = -I_2 20$$
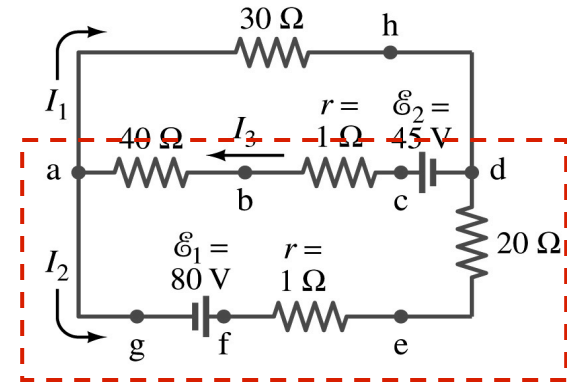
$$V_{dc} = +45 \quad V_{cb} = -I_3 \cdot 1 \quad V_{ba} = -40I_3$$



The total voltage change in loop *agfedcba* is. $V_{agfedcba} = -21I_2 + 125 - 41I_3 = 0$

So the three equations become $I_3 = I_1 + I_2$

$$45 - 30I_1 - 41I_3 = 0$$

$$125 - 21I_2 - 41I_3 = 0$$

We can obtain the three current by solving these equations for I_1 , I_2 and I_3 .

EMF's in Series and Parallel: Charging a Battery

- When two or more sources of emf's, such as batteries, are connected in series

- The total voltage is the algebraic sum of their voltages, if their direction is the same


- $V_{ac} = 1.5 + 1.5 = 3.0\text{V}$ in figure (a).

- If the batteries are arranged in an opposite direction, the total voltage is the difference between them

- $V_{ac} = 20 - 12 = 8.0\text{V}$ in figure (b)

This is the way we jump start a car


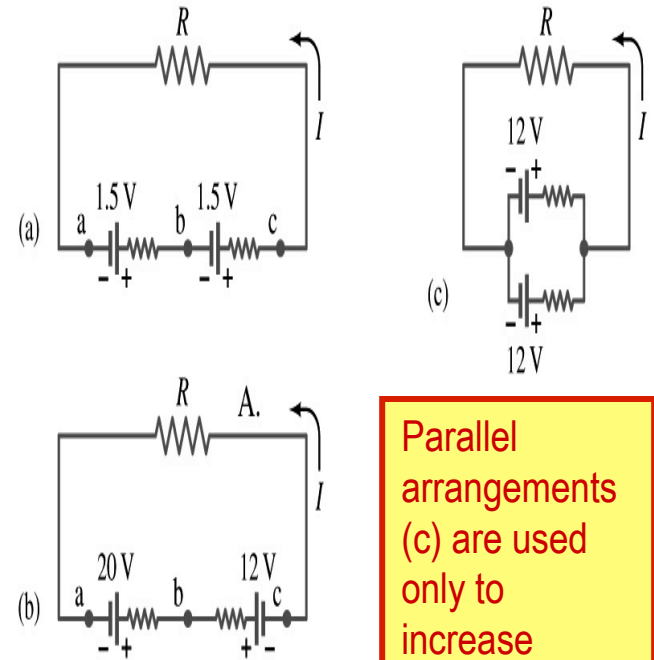
- Connecting batteries in opposite direction is wasteful.
- This, however, is the way a battery charger works.
- Since the 20V battery is at a higher voltage, it forces charges into 12V battery
- Some battery are rechargeable since their chemical reactions are reversible but most the batteries can not reverse their chemical reactions



Parallel arrangements (c) are used only to increase currents.

Capacitors in Series or Parallel

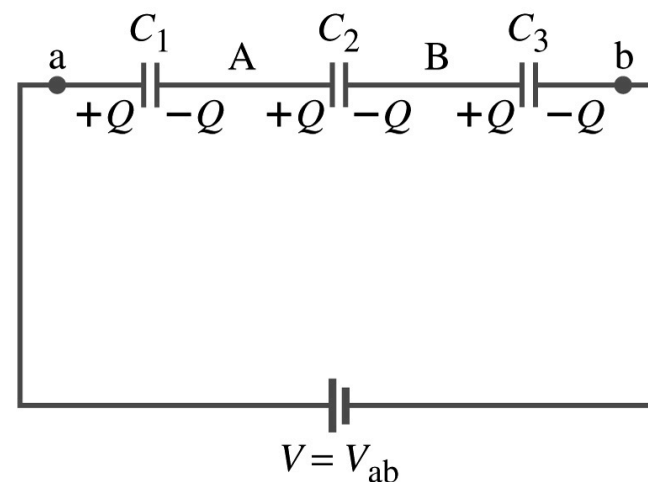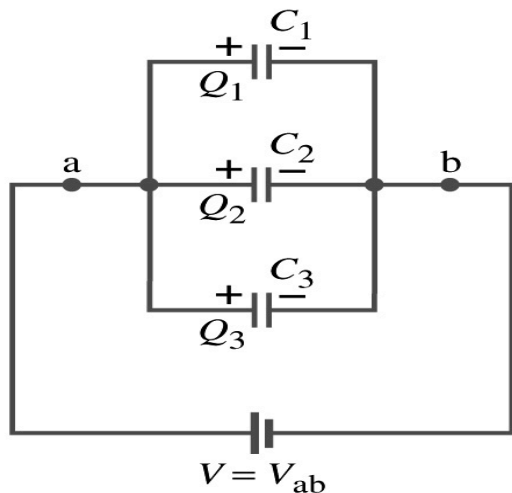- Capacitors are also used in many electric circuits.
- So what is an electric circuit again?
 - A closed path of conductors, usually wires, connecting capacitors, resistors and other electrical devices, in which
 - charges can flow
 - And includes a source of potential such as a battery
- Capacitors can be connected in various ways.
 - In parallel and in Series or in combination




Capacitors in Parallel

- Parallel arrangement provides the same voltage across all the capacitors.

- Left hand plates are at V_a and right hand plates are at V_b
- So each capacitor plate acquires charges given by the formula

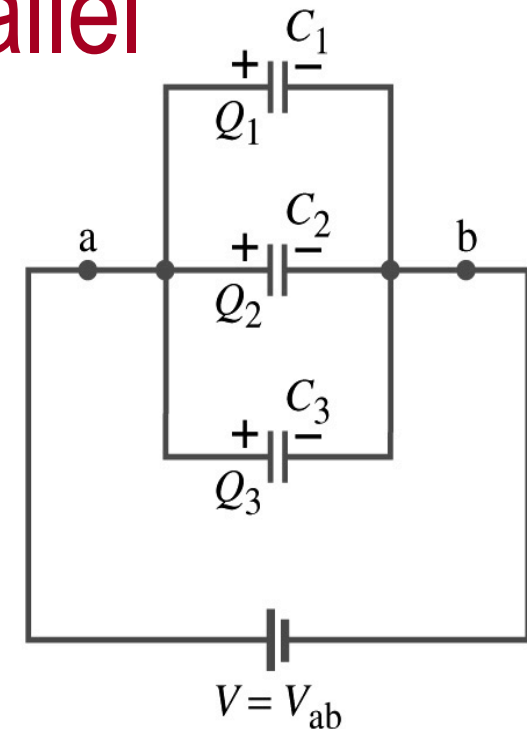- $Q_1 = C_1 V$, $Q_2 = C_2 V$, and $Q_3 = C_3 V$



- The total charge Q that must leave the battery is then
 - $Q = Q_1 + Q_2 + Q_3 = V(C_1 + C_2 + C_3)$
- Consider that the three capacitors behave like an equivalent one
 - $Q = C_{eq} V = V(C_1 + C_2 + C_3)$
- Thus the equivalent capacitance in parallel is $C_{eq} = C_1 + C_2 + C_3$


Tu What is the net effect?

PH The capacitance increases!!!

Capacitors in Series

- Series arrangement is more interesting

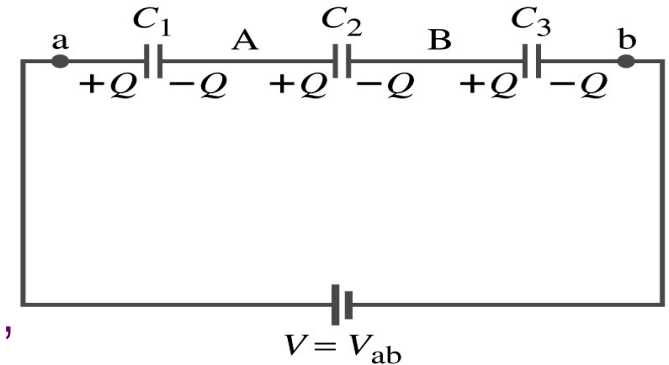- When a battery is connected, $+Q$ flows to the left plate of C_1 and $-Q$ flows to the right plate of C_3 inducing opposite sign charges on the other plates.
- Since the capacitor in the middle was originally neutral, charges get induced to neutralize the induced charges
- So the charge on each capacitor is the same value, Q . (**Same charge**)



- Consider that the three capacitors behave like an equivalent one

- $Q = C_{eq} V \rightarrow V = Q / C_{eq}$

- The total voltage V across the three capacitors in series must be equal to the sum of the voltages across each capacitor.

- $V = V_1 + V_2 + V_3 = (Q/C_1 + Q/C_2 + Q/C_3)$

- Putting all these together, we obtain:

- $V = Q / C_{eq} = Q(1/C_1 + 1/C_2 + 1/C_3)$

- Thus the equivalent capacitance is

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


What is the net effect?



The capacitance smaller than the smallest C !!!

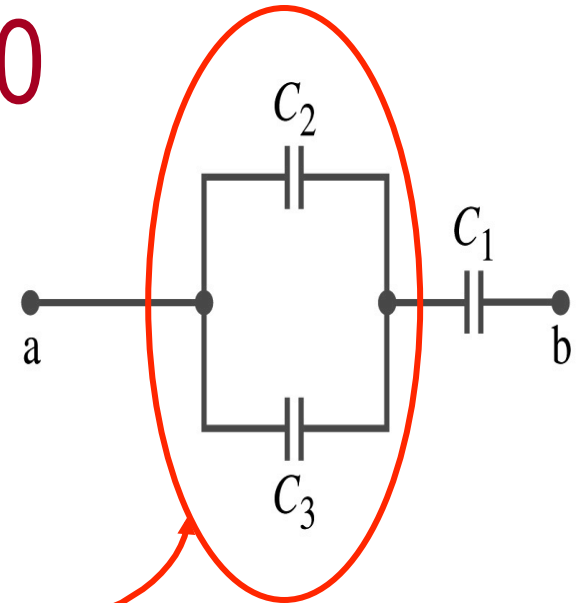Example 19 – 10

Equivalent Capacitor: Determine the capacitance of a single capacitor that will have the same effect as the combination shown in the figure. Assume $C_1 = C_2 = C_3 = C$.



We should do these first!!

How? These are in parallel so the equivalent capacitance is:

$$C_{eq1} = C_1 + C_2 = 2C$$

Now the equivalent capacitor is in series with C_1 .

$$\frac{1}{C_{eq}} = \frac{1}{C_{eq1}} + \frac{1}{C_2} = \frac{1}{2C} + \frac{1}{C} = \frac{3}{2C} \quad \text{Solve for } C_{eq} \quad C_{eq} = \frac{2C}{3}$$

Resister and Capacitor Arrangements

- Parallel Capacitor arrangements

$$C_{eq} = \sum_i C_i$$

- Parallel Resister arrangements

$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$$

- Series Capacitor arrangements

$$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$$


- Series Resister arrangements

$$R_{eq} = \sum_i R_i$$



RC Circuits

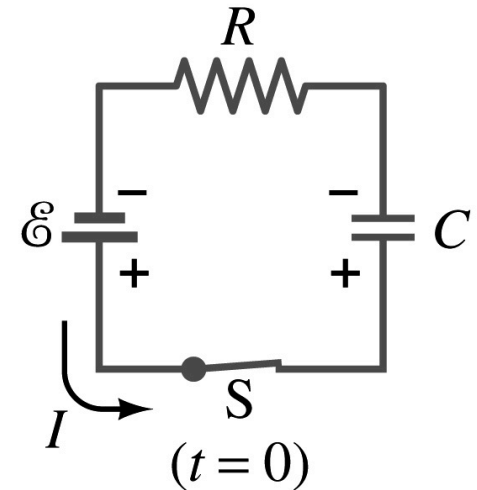- Circuits containing both resistors and capacitors
 - RC circuits are used commonly in everyday life
 - Control windshield wiper
 - Timing of traffic light color change
 - Camera flashes and heart pacemakers
- How does an RC circuit look?
- There should be a source of emf, capacitors and resistors
- What happens when the switch S is closed?



- Current immediately starts flowing through the circuit.
- Electrons flow out of the negative terminal of the emf source, through the resistor R and accumulate on the upper plate of the capacitor
- The electrons from the bottom plate of the capacitor flow into the positive terminal of the battery, leaving only positive charge on the bottom plate
- As the charge accumulates on the capacitor, the potential difference across it increases
- The current reduces gradually to 0 until the voltage across the capacitor is the same as emf.
- The charge on the capacitor increases until it reaches its maximum, $C\mathcal{E}$.
- What happens when the battery in the circuit is replaced with a wire?

Tuesday, June 18, 2013




PHYS 1442-001, Summer 2013
Dr. Jaehoon Yu

Capacitor
discharges

RC Circuits

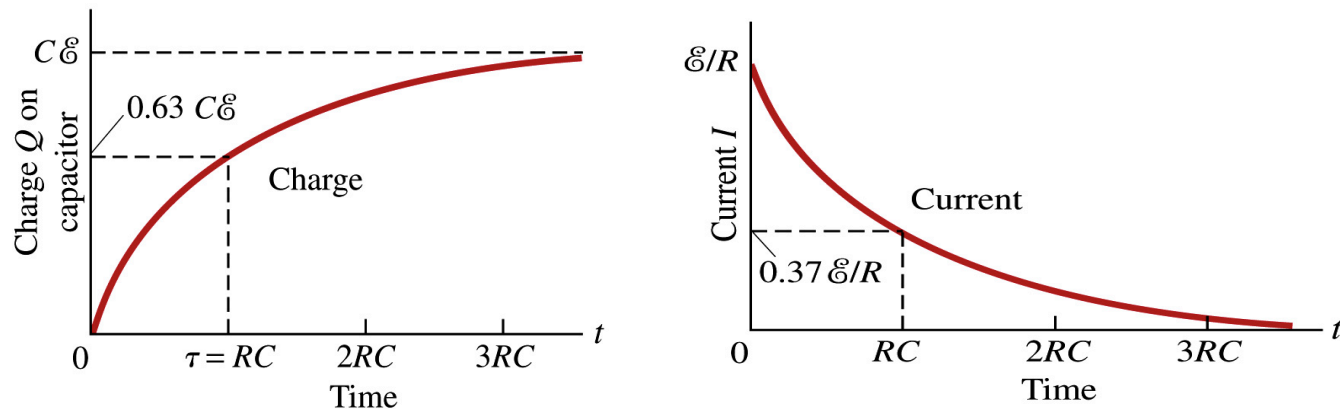- How does all this look like in graphs?
 - Charge and the current on the capacitor as a function of time



- From energy conservation (Kirchhoff's 2nd rule), the emf \mathcal{E} must be equal to the voltage drop across the capacitor and the resistor
 - $\mathcal{E} = IR + Q/C$
 - R includes all resistance in the circuit, including the internal resistance of the battery, I is the current in the circuit at any instant, and Q is the charge of the capacitor at that same instance.


Analysis of RC Circuits

- Charge $Q = C\varepsilon(1 - e^{-t/RC})$ and voltage $V_C = \varepsilon(1 - e^{-t/RC})$
- What can we see from the above equations?
 - Q and V_C increase from 0 at $t=0$ to maximum value $Q_{\max} = C\varepsilon$ and $V_C = \varepsilon$.
- In how much time?
 - The quantity RC is called the time constant, τ , of the circuit
 - $\tau = RC$, What is the unit? **Sec.**
 - What is the physical meaning?
 - The time required for the capacitor to reach $(1 - e^{-1}) = 0.63$ or 63% of its full charge
- The current is $I = \frac{\varepsilon}{R} e^{-t/RC}$



Discharging RC Circuits

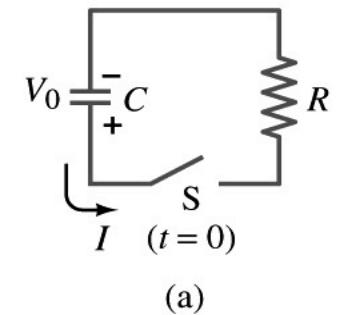- When a capacitor is already charged, it is allowed to discharge through a resistance R .



- When the switch S is closed, the voltage across the resistor at any instant equals that across the capacitor. Thus $IR=Q/C$.
- The rate at which the charge leaves the capacitor equals the negative of the current flows through the resistor

- $I = -\Delta Q/\Delta t$. Why negative?


- Since the current is leaving the capacitor

- Thus the voltage equation becomes a differential equation

$$-\frac{\Delta Q}{\Delta t} R = \frac{Q}{C} \quad \xrightarrow{\text{Rearrange terms}} \quad \frac{\Delta Q}{Q} = -\frac{\Delta t}{RC}$$

Discharging RC Circuits

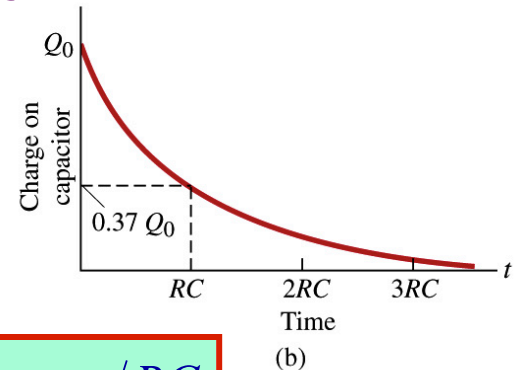- What happens when an RC circuit discharges from its original charge of Q_0 ?



- Charge at any given time t is

$$Q(t) = Q_0 e^{-t/RC}$$

- What does this tell you about the charge on the capacitor?

- It decreases exponentially with time at a time constant RC
- Just like the case of charging

- The current is:


$$I(t) = I_0 e^{-t/RC}$$

- The voltage is:

$$V(t) = V_0 e^{-t/RC}$$

Ex. 19 – 12

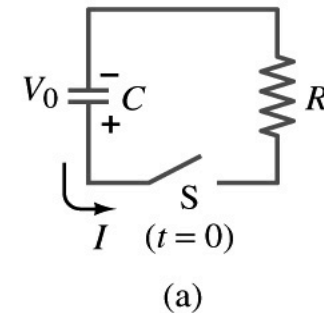Discharging RC circuit. If a charged capacitor $C=35\mu\text{F}$ is connected to a resistance $R=120\Omega$ as in the figure, how much time will elapse until the voltage falls to 10% of its original (maximum) value?



What is the RC time of this circuit?

The RC time $\tau = RC = 120 \cdot 35 \times 10^{-6} = 4.2 \text{ ms}$

Since we are looking for the time it takes for $V_c=10\%$ of V_0 , we obtain

$$V(t) = V_0 e^{-t/RC} \quad \xrightarrow{\text{For } 0.1 V_0} \quad 0.1 V_0 = V_0 e^{-t/RC}$$


$$\xrightarrow{\text{Rearrange terms}} \quad -t/RC = \ln 0.1 = -\ln 10 = -2.3$$

$$\xrightarrow{\text{Solve for } t} \quad t = RC \cdot (2.3) = 4.2 \times 10^{-3} \cdot (2.3) = 9.7 \times 10^{-3} \text{ (sec)}$$

Application of RC Circuits

- What do you think the charging and discharging characteristics of RC circuits can be used for?

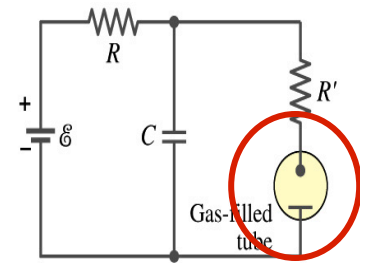- To produce voltage pulses at a regular frequency
- How?




- The capacitor charges up to a particular voltage and discharges
- A simple way of doing this is to use breakdown of voltage in a gas filled tube

- The discharge occurs when the voltage breaks down at V_0
- After the completion of discharge, the tube no longer conducts
- Then the voltage is at V_0' and it starts charging up
- How do you think the voltage as a function of time look?


» A sawtooth shape

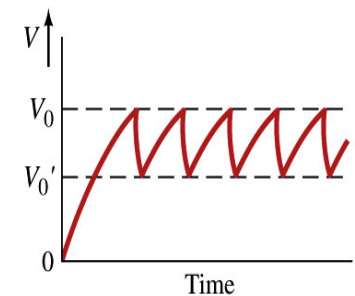- Pace maker, intermittent windshield wiper, etc



Magnetism

- What are magnets?
 - Objects with two poles, north and south poles
 - The pole that points to geographical north is the north pole and the other is the south pole
 - Principle of compass
 - These are called magnets due to the name of the region, Magnesia, where rocks that attract each other were found
- What happens when two magnets are brought to each other?
 - They exert force onto each other
 - What kind?
 - Both repulsive and attractive forces depending on the configurations
 - Like poles repel each other while the unlike poles attract

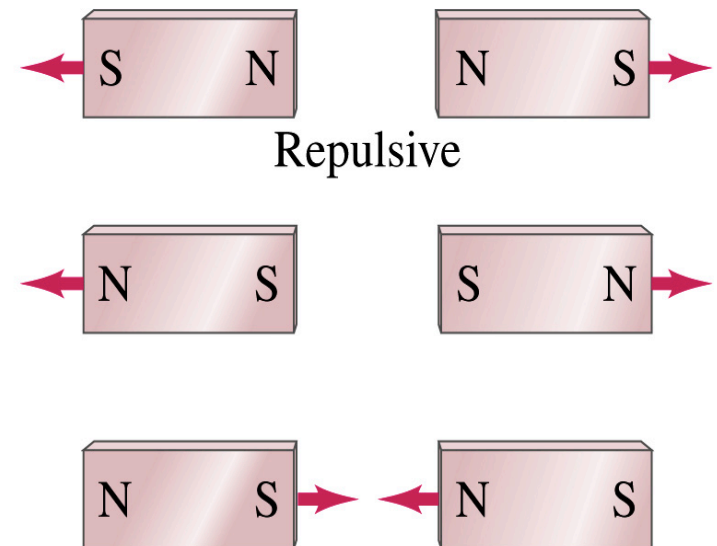

Magnetism

- So the magnet poles are the same as the electric charge?
 - No. Why not?
 - While the electric charges (positive and negative) can be isolated the magnet poles cannot be isolated.
 - So what happens when a magnet is cut?
 - If a magnet is cut, two magnets are made.
 - The more they get cut, the more magnets are made
 - Single pole magnets are called the monopole but it has not been seen yet
- Ferromagnetic materials: Materials that show strong magnetic effects
 - Iron, cobalt, nickel, gadolinium and certain alloys
- Other materials show very weak magnetic effects



Magnetic Field

- Just like the electric field that surrounds electric charge, a magnetic field surrounds a magnet
- What does this mean?
 - Magnetic force is also a field force
 - The force one magnet exerts onto another can be viewed as the interaction between the magnet and the magnetic field produced by the other magnet
 - What kind of quantity is the magnetic field? Vector or Scalar? **Vector**
- So one can draw magnetic field lines, too.
 - The direction of the magnetic field is tangent to a line at any point
 - The direction of the field is the direction the north pole of a compass would point to
 - The number of lines per unit area is proportional to the strength of the magnetic field
 - Magnetic field lines continue inside the magnet
 - Since magnets always have both the poles, magnetic field lines form closed loops unlike electric field lines

