



PHYS 1444 – Section 04

Lecture #22

Tuesday November 27, 2012

Dr. Andrew Brandt

- AC Circuits

Last HW on ch 29-30 TBA
tomorrow due Monday
Dec. 3 @ 11 pm

Exam: Thursday Dec. 6,
2012 11 - 1:30 p.m.



AC Circuits – the preamble

- Do you remember how the rms and peak values for current and voltage are related?

$$V_{rms} = \frac{V_0}{\sqrt{2}} \quad I_{rms} = \frac{I_0}{\sqrt{2}}$$

- The symbol for an AC power source is



- We assume that the voltage gives rise to current


$$I = I_0 \sin 2\pi ft = I_0 \sin \omega t$$

where $\omega = 2\pi f$



AC Circuit w/ Resistance only

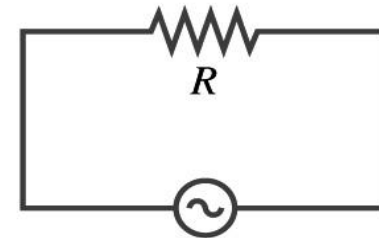- What do you think will happen when an ac source is connected to a resistor?
- From Kirchhoff's loop rule, we obtain



$$V - IR = 0$$


- Thus

$$V = I_0 R \sin \omega t = V_0 \sin \omega t$$

– where $V_0 = I_0 R$

- What does this mean?

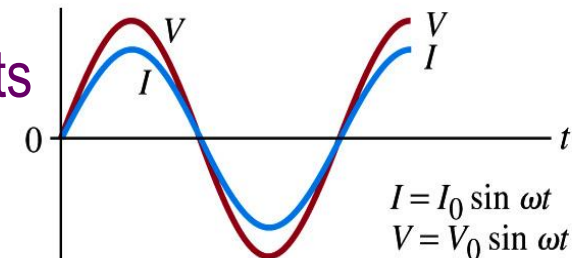- Current is 0 when voltage is 0 and current is at its peak when voltage is at its peak.
- Current and voltage are “in phase”



- Energy is lost via the transformation into heat at an average rate

$$\bar{P} = \bar{I} \bar{V} = I_{rms}^2 R = V_{rms}^2 / R$$



AC Circuit w/ Inductance only

- From Kirchoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus

$$V = L \frac{dI}{dt} = L \frac{d I_0 \sin \omega t}{dt} = \omega L I_0 \cos \omega t$$

- Using the identity $\cos \theta = \sin \theta + 90^\circ$

$$V = \omega L I_0 \sin \omega t + 90^\circ = V_0 \sin \omega t + 90^\circ$$


- where $V_0 = \omega L I_0$

- What does this mean?

- Current and voltage are “out of phase by $\pi/2$ or 90° ”.
- In other words the current reaches its peak $\frac{1}{4}$ cycle after the voltage

- What happens to the energy?

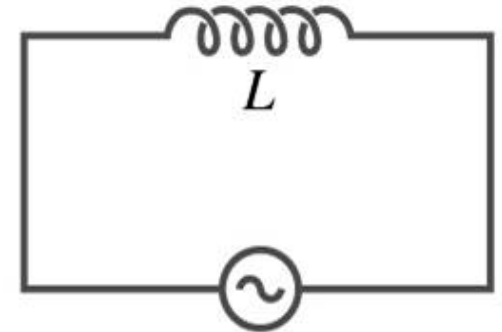- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the magnetic field then released back to the source





AC Circuit w/ Inductance only



- From Kirchoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus

$$V = L \frac{dI}{dt} = L \frac{d I_0 \sin \omega t}{dt} = \omega L I_0 \cos \omega t$$

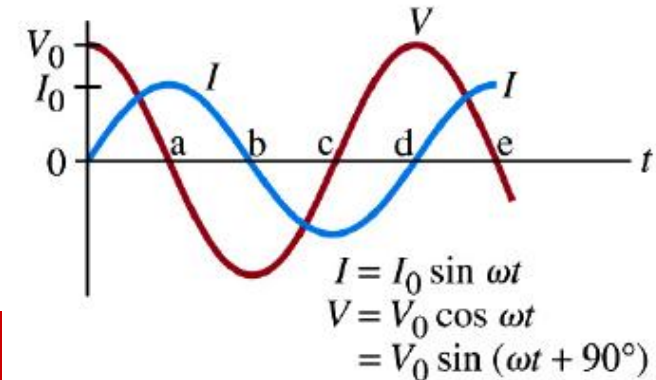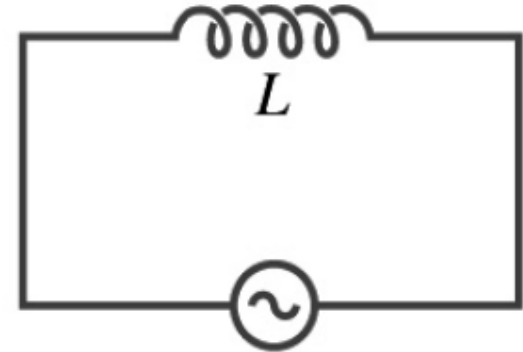- Using the identity $\cos \theta = \sin \theta + 90^\circ$
- $V = \omega L I_0 \sin \omega t + 90^\circ = V_0 \sin \omega t + 90^\circ$
- where $V_0 = \omega L I_0$
- Current and voltage are "out of phase by $\pi/2$ or 90° ".



– For an inductor we can write $V_0 = I_0 X_L$

- Where X_L is the inductive reactance of the inductor

$$X_L = \omega L$$

- The relationship $V_0 = I_0 X_L$ is not generally valid since V_0 and I_0 do not occur at the same time, but $V_{rms} = I_{rms} X_L$ is valid



AC Circuit w/ Inductance only


- How are the resistor and inductor different in terms of energy?
 - Inductor Stores the energy temporarily in the magnetic field and then releases it back to the emf source
 - Resistor Does not store energy but transforms it to thermal energy, losing it to the environment
- How are they the same?
 - They both impede the flow of charge
 - For a resistance R, the peak voltage and current are related by $V_0 = I_0 R$
 - Similarly, for an inductor we can write $V_0 = I_0 X_L$, where $X_L = \omega L$ and X_L is the inductive reactance of the inductor

BUT since the voltage and current are out of phase this equation is not valid at any particular time. However $V_{rms} = I_{rms} X_L$ is valid!

Note the unit of X_L is Ω , while the unit of L is Henry (what is a Henry?)



LR Circuits

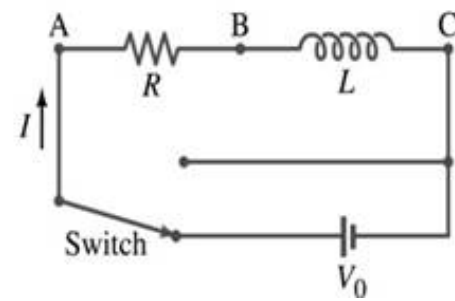


- This can be shown w/ Kirchoff rule loop rules
 - The emfs in the circuit are the battery voltage V_0 and the emf $\varepsilon = -\mathcal{L}(dI/dt)$ (opposes the ΔI after the bat. switched on)

- The sum of the potential changes through the circuit is

$$V_0 + \varepsilon - IR = V_0 - L dI/dt - IR = 0$$

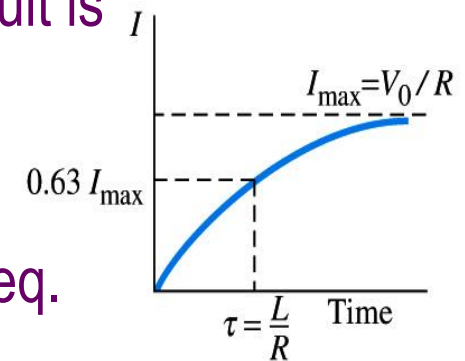- Where I is the current at any instance
- By rearranging the terms, we obtain a differential eq.
- $L dI/dt + IR = V_0$



- We can integrate just as in RC circuit

$$\int_{I=0}^I \frac{dI}{V_0 - IR} = \int_{t=0}^t \frac{dt}{L}$$

- So the solution is $-\frac{1}{R} \ln\left(\frac{V_0 - IR}{V_0}\right) = \frac{t}{L}$


$$I = V_0 \left(1 - e^{-t/\tau}\right) / R = I_{\max} \left(1 - e^{-t/\tau}\right)$$

- Where $\tau = L/R$

- This is the time constant τ of the LR circuit and is the time required for the current I to reach 0.63 of the maximum



Discharge of LR Circuits

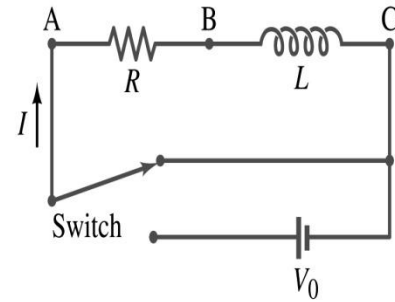


- If the switch is flipped away from the battery

- The differential equation becomes

- $L \frac{dI}{dt} + IR = 0$

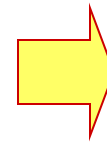
- So the integration is $\int_{I=0}^I \frac{dI}{IR} = \int_{t=0}^t \frac{dt}{L}$



$$\ln \frac{I}{I_0} = -\frac{R}{L} t$$

- Which results in the solution
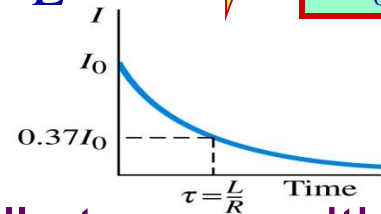
$$I = I_0 e^{-\frac{R}{L} t} = I_0 e^{-t/\tau}$$



- The current decays exponentially to zero with the time constant $\tau=L/R$

- So there always is a reaction time when a system with a coil, such as an electromagnet, is turned on or off.

- The current in LR circuit behaves in a similar manner as for the RC circuit, except that in steady state RC current is 0, and the time constant is inversely proportional to R in



Example 31 – 1

Reactance of a coil. A coil has a resistance $R=1.00\Omega$ and an inductance of $0.300H$. Determine the current in the coil if (a) 120 V dc is applied to it; (b) 120 V ac (rms) at 60.0Hz is applied.

Is there a reactance for dc? Nope. Why not? Since $\omega=0$, $X_L = \omega L = 0$

So for dc power, the current is from Kirchhoff's rule $V - IR = 0$

$$I_0 = \frac{V_0}{R} = \frac{120\text{V}}{1.00\Omega} = 120\text{A}$$

For an ac power with $f=60\text{Hz}$, the reactance is

$$X_L = \omega L = 2\pi fL = 2\pi \cdot 60.0\text{s}^{-1} \cdot 0.300\text{H} = 113\Omega$$


Since the resistance can be ignored compared to the reactance, the rms current is

$$I_{rms} \approx \frac{V_{rms}}{X_L} = \frac{120\text{V}}{113\Omega} = 1.06\text{A}$$



AC Circuit w/ Capacitance only

- What happens when a capacitor is connected to a dc power source?
 - The capacitor quickly charges up.
 - There is no steady current flow in the circuit
 - Since a capacitor prevents the flow of a dc current
- What do you think will happen if it is connected to an ac power source?
 - The current flows continuously. Why?
 - When the ac power turns on, charge begins to flow one direction, charging up the plates
 - When the direction of the power reverses, the charge flows in the opposite direction

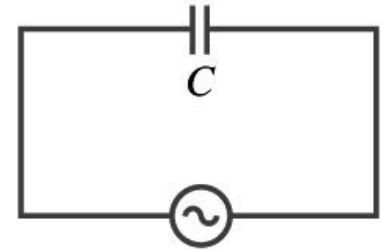




AC Circuit w/ Capacitance only

- From Kirchoff's loop rule, we obtain

$$V = \frac{Q}{C}$$

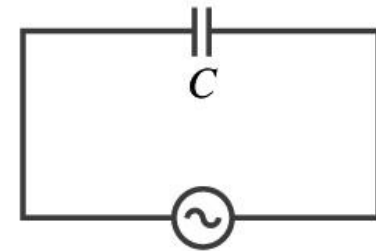- Current at any instant is $I = \frac{dQ}{dt} = I_0 \sin \omega t$



- Thus, the charge Q on the plate at any instance is

$$Q = \int_{Q=0}^Q dQ = \int_{t=0}^t I_0 \sin \omega t dt = -\frac{I_0}{\omega} \cos \omega t$$

- The voltage across the capacitor is

$$V = \frac{Q}{C} = -I_0 \frac{1}{\omega C} \cos \omega t$$

- Using the identity $\cos \theta = -\sin \theta - 90^\circ$

$$V = I_0 \frac{1}{\omega C} \sin \omega t - 90^\circ = V_0 \sin \omega t - 90^\circ$$

- Where

- $V_0 = \frac{I_0}{\omega C}$




AC Circuit w/ Capacitance only

- So the voltage is $V = V_0 \sin \omega t - 90^\circ$
- What does this mean?
 - Current and voltage are “out of phase by $\pi/2$ or 90° ” but in this case, the voltage reaches its peak $1/4$ cycle after the current

- What happens to the energy?

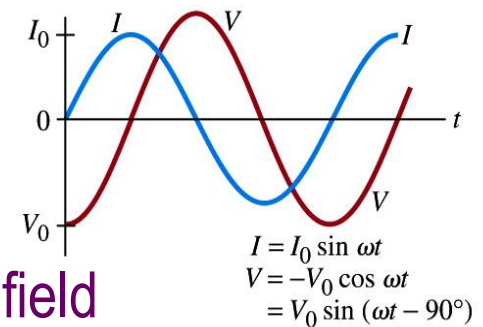- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the electric field
- Then released back to the source



- Relationship between the peak voltage and the peak current in the capacitor can be written as $V_0 = I_0 X_C$

- Where the capacitance reactance X_C is defined as
- Again, this relationship is only valid for rms quantities

$$X_C = \frac{1}{\omega C}$$


Infinite when $\omega=0$.

$$V_{rms} = I_{rms} X_C$$



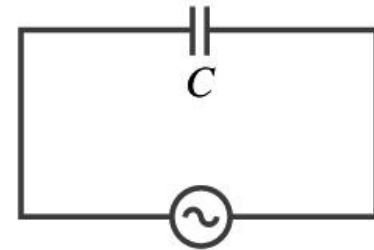Example 31 – 2

Capacitor reactance. What are the peak and rms current in the circuit in the figure if $C=1.0\mu\text{F}$ and $V_{\text{rms}}=120\text{V}$? Calculate for $f=60\text{Hz}$.



The peak voltage is $V_0 = \sqrt{2}V_{\text{rms}} = 120\text{V} \cdot \sqrt{2} = 170\text{V}$

The capacitance reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 60\text{s}^{-1} \cdot 1.0 \times 10^{-6}\text{F}} = 2.7\text{k}\Omega$$

Thus the peak current is

$$I_0 = \frac{V_0}{X_C} = \frac{170\text{V}}{2.7\text{k}\Omega} = 63\text{mA}$$


The rms current is

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120\text{V}}{2.7\text{k}\Omega} = 44\text{mA}$$



AC Circuit w/ LRC

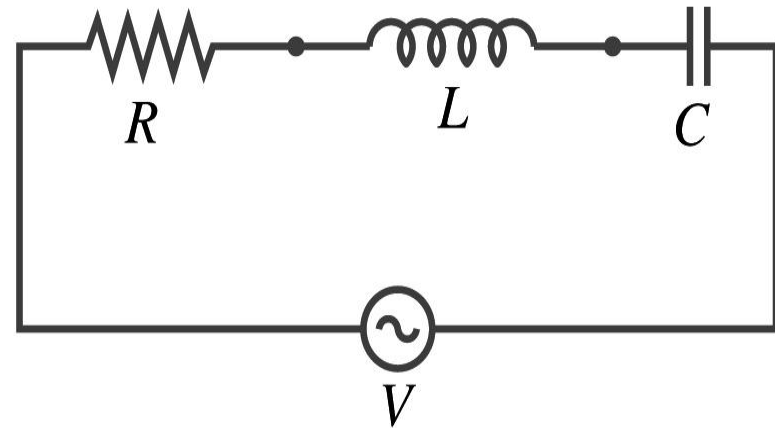
- The voltage across each element is
 - V_R is in phase with the current
 - V_L leads the current by 90°
 - V_C lags the current by 90°
- From Kirchoff's loop rule
- $V = V_R + V_L + V_C$
 - However since they do not reach the peak voltage at the same time, the peak voltage of the source V_0 will not equal $V_{R0} + V_{L0} + V_{C0}$
 - The rms voltage also will not be the simple sum of the three





AC Circuit w/ LRC

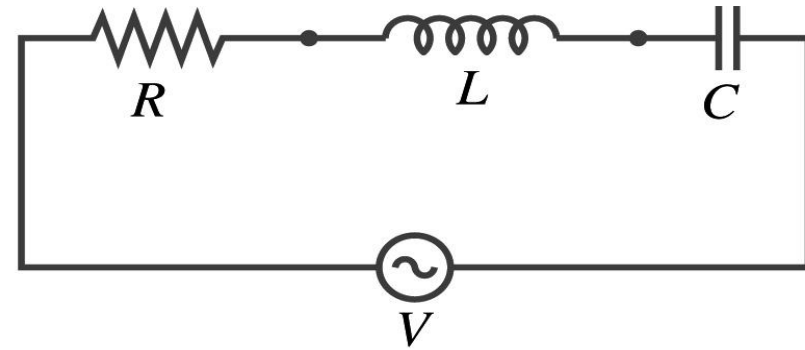- The current at any instant is the same at all point in the circuit
 - The currents in each elements are in phase
 - Why?
 - Since the elements are in series
 - How about the voltage?
 - They are not in phase.



- The current at any given time is

$$I = I_0 \sin \omega t$$

- The analysis of LRC circuit can be done using the “phasor” diagram (but not by us!)