



PHYS 1444 – Section 003

Lecture #8

Thursday Sep. 20, 2012

Ian Howley

- Chapter 24
 - Capacitors and Capacitance
 - Capacitors in Series and Parallel
 - Energy Stored in Capacitors
 - Dielectrics





Capacitors (or Condensers)

- What is a capacitor?
 - A device that can store electric charge without letting the charge flow
- What does it consist of?
 - Usually consists of two oppositely charged conducting objects (plates or sheets) placed near each other without touching
 - Why can't they touch each other?
 - The charges will neutralize each other
- Can you give some examples?
 - Camera flash, surge protectors, computer keyboard, binary circuits...
- How is a capacitor different than a battery?
 - Battery provides potential difference by storing energy (usually chemical energy) while the capacitor stores charge but very little energy.






Capacitors

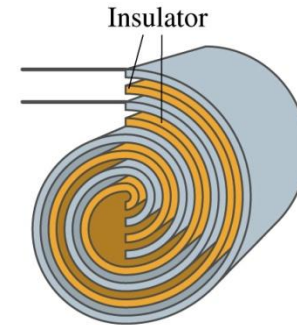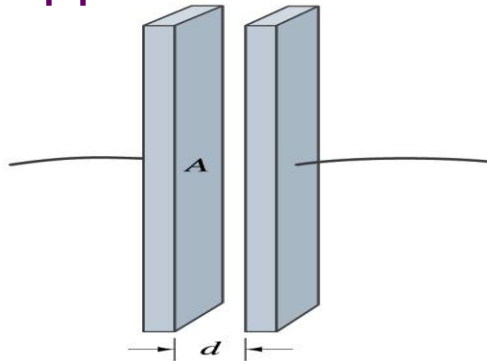- A simple capacitor consists of a pair of parallel plates of area \mathcal{A} separated by a distance d .
 - A cylindrical capacitor is essentially parallel plates wrapped around as a cylinder.



- Symbols for a capacitor and a battery:

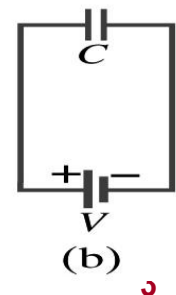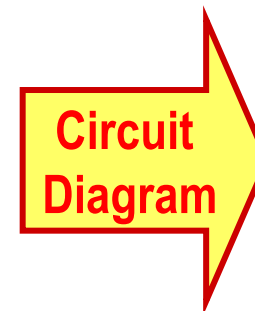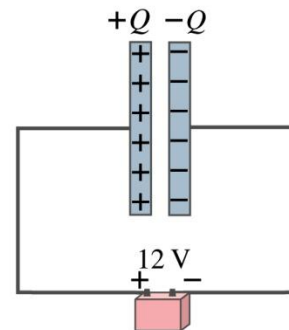
- Capacitor $\parallel\text{-}$
- Battery $(+) \text{-} \parallel\text{-} (-)$





Capacitors

- What do you think will happen if a battery is connected (voltage is applied) to a capacitor?
 - The capacitor gets charged quickly, one plate positive and the other negative with an equal amount. of charge
- Each battery terminal, the wires and the plates are conductors. What does this mean?
 - All conductors are at the same potential.
 - the full battery voltage is applied across the capacitor plates.
- So for a given capacitor, the amount of charge stored in the capacitor is proportional to the potential difference V_{ba} between the plates. How would you write this formula?

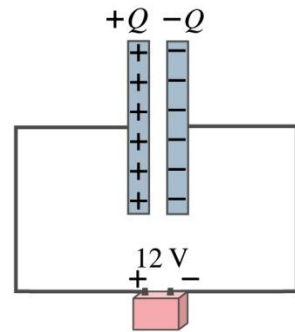

$$Q = CV_{ba}$$

C is a property of a capacitor so does not depend on Q or V.

- C is a proportionality constant, called capacitance of the device.
- What is the unit? **C/V or Farad (F)** **Normally use μF or pF.**



Determination of Capacitance

- C can be determined analytically for capacitors w/ simple geometry and air in between.

- Let's consider a parallel plate capacitor.

- Plates have area A each and separated by d.

- d is smaller than the length, so E is uniform.

- For parallel plates $E = \sigma / \epsilon_0$, where σ is the surface charge density.

- E and V are related $V_{ba} = - \int_a^b \vec{E} \cdot d\vec{l}$


- Since we take the integral from the lower potential point a to the higher potential point b along the field line, we obtain

- $V_{ba} = V_b - V_a = - \int_a^b E dl \cos 180^\circ = + \int_a^b E dl = \int_a^b \frac{\sigma}{\epsilon_0} dl = \int_a^b \frac{Q}{\epsilon_0 A} dl = \frac{Q}{\epsilon_0 A} \int_a^b dl = \frac{Q}{\epsilon_0 A} (b - a) = \frac{Qd}{\epsilon_0 A}$

- So from the formula:

- What do you notice?
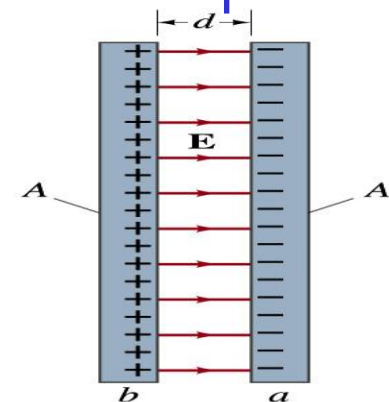
$$C = \frac{Q}{V_{ba}} = \frac{Q}{Qd/\epsilon_0 A} = \frac{\epsilon_0 A}{d}$$



C only depends on the area (A) and the separation (d) of the plates and the permittivity of the medium between them.



Example 24 – 1

Capacitor calculations: (a) Calculate the capacitance of a capacitor whose plates are 20 cm x 3.0 cm and are separated by a 1.0 mm air gap. (b) What is the charge on each plate if the capacitor is connected to a 12 V battery? (c) What is the electric field between the plates? (d) Estimate the area of the plates needed to achieve a capacitance of 1F, given the same air gap.

(a) Using the formula for a parallel plate capacitor, we obtain

$$C = \frac{\epsilon_0 A}{d} =$$
$$= 8.85 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2 \frac{0.2 \times 0.03 \text{ m}^2}{1 \times 10^{-3} \text{ m}} = 53 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m} = 53 \text{ pF}$$

(b) From $Q=CV$, the charge on each plate is

$$Q = CV = 53 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m} \quad 12\text{V} = 6.4 \times 10^{-10} \text{ C} = 640 \text{ pC}$$



Example 24 – 1

(c) Using the formula for the electric field in two parallel plates

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0} = \frac{6.4 \times 10^{-10} \text{ C}}{6.0 \times 10^{-3} \text{ m}^2 \times 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2} = 1.2 \times 10^4 \text{ N/C} = 1.2 \times 10^4 \text{ V/m}$$

Or, since $V = Ed$ we can obtain $E = \frac{V}{d} = \frac{12\text{V}}{1.0 \times 10^{-3} \text{ m}} = 1.2 \times 10^4 \text{ V/m}$

(d) Solving the capacitance formula for A, we obtain

$$C = \frac{\epsilon_0 A}{d}$$

Solve for A 


$$A = \frac{Cd}{\epsilon_0} = \frac{1\text{F} \cdot 1 \times 10^{-3} \text{ m}}{9 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2} \approx 10^8 \text{ m}^2 \approx 100 \text{ km}^2$$

About 40% the area of Arlington (256km²).



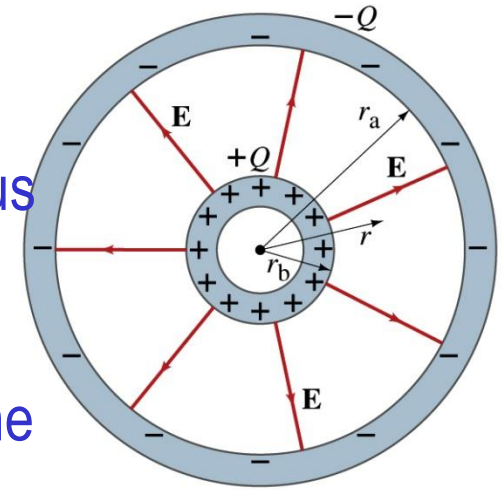Example 24 – 3

Spherical capacitor: A spherical capacitor consists of two thin concentric spherical conducting shells, of radius r_a and r_b , as in the figure. The inner shell carries a uniformly distributed charge Q on its surface and the outer shell an equal but opposite charge $-Q$. Determine the capacitance of this configuration.



Using Gauss' law, the electric field outside a uniformly charged conducting sphere is

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

So the potential difference between a and b is

$$\begin{aligned} V_{ba} &= - \int_a^b \vec{E} \cdot d\vec{l} = \\ &= - \int_a^b E \cdot dr = - \int_a^b \frac{Q}{4\pi\epsilon_0 r^2} dr = - \frac{Q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r} \right)_{r_a}^{r_b} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_b} - \frac{1}{r_a} \right) = \frac{Q}{4\pi\epsilon_0} \left(\frac{r_a - r_b}{r_b r_a} \right) \end{aligned}$$

Thus capacitance is

$$C = \frac{Q}{V} = \frac{Q}{\frac{Q}{4\pi\epsilon_0} \left(\frac{r_a - r_b}{r_b r_a} \right)} = \frac{4\pi\epsilon_0 r_b r_a}{r_a - r_b}$$



Capacitor Cont'd

- A single isolated conductor can be said to have a capacitance, C .
- C can still be defined as the ratio of the charge to absolute potential V on the conductor.
 - So $Q=CV$.
- The potential of a single conducting sphere of radius r_b can be obtained as



$$V = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_b} - \frac{1}{r_a} \right) = \frac{Q}{4\pi\epsilon_0 r_b} \quad \text{where } r_a \rightarrow \infty$$

- So its capacitance is $C = Q / V = 4\pi\epsilon_0 r_b$
- Although it has capacitance, a single conductor is not considered to be a capacitor, as a second nearby charge is required to store charge



Capacitors in Series or Parallel

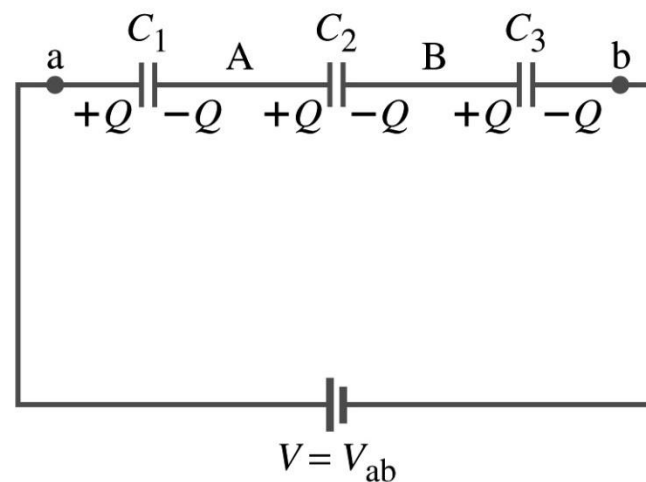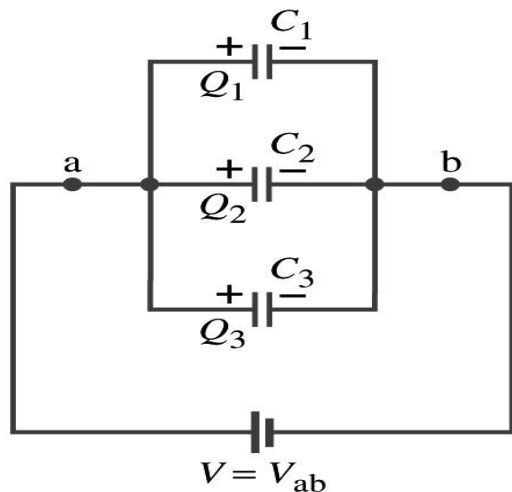
- Capacitors are used in many electric circuits
- What is an electric circuit?
 - A closed path of conductors, usually wires connecting capacitors and other electrical devices, in which
 - charges can flow
 - there is a voltage source such as a battery
- Capacitors can be connected in various ways.
 - In parallel
 - and
 - in Series
 - or in combination





Capacitors in Parallel

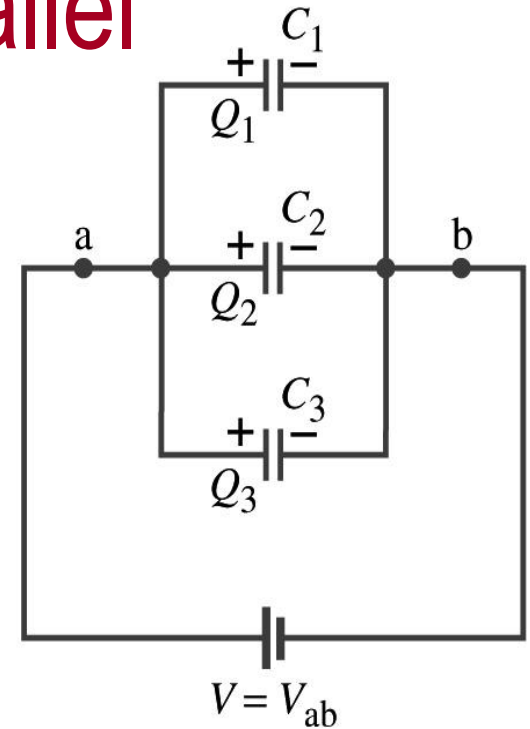- Parallel arrangement provides the **same voltage** across all the capacitors.
 - Left hand plates are at V_a and right hand plates are at V_b
 - So each capacitor plate acquires charges given by the formula
 - $Q_1=C_1V$, $Q_2=C_2V$, and $Q_3=C_3V$



- The total charge Q that must leave battery is then
 - $Q=Q_1+Q_2+Q_3=V(C_1+C_2+C_3)$
- Consider that the three capacitors behave like a single “equivalent” one
 - $Q=C_{eq}V=V(C_1+C_2+C_3)$
- Thus the equivalent capacitance in parallel is $C_{eq} = C_1 + C_2 + C_3$

For capacitors in parallel the capacitance is the sum of the individual capacitors


$$C_{eq} = C_1 + C_2 + C_3$$



Capacitors in Series

- Series arrangement is more “interesting”

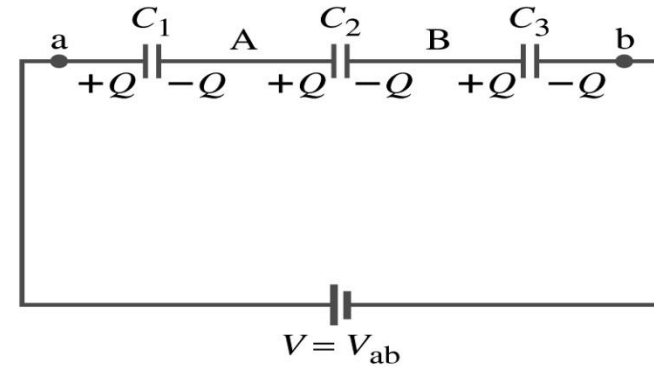- When battery is connected, +Q flows to the left plate of C_1 and $-Q$ flows to the right plate of C_3
- This induces opposite sign charges on the other plates.
- Since the capacitor in the middle is originally neutral, charges get induced to neutralize the induced charges
- So the charge on each capacitor is the same value, Q. (**Same charge**)



- Consider that the three capacitors behave like an equivalent one

- $Q = C_{eq} V \rightarrow V = Q / C_{eq}$

- The total voltage V across the three capacitors in series must be equal to the sum of the voltages across each capacitor.

- $V = V_1 + V_2 + V_3 = (Q / C_1 + Q / C_2 + Q / C_3)$

- Putting all these together, we obtain:

- $V = Q / C_{eq} = Q (1 / C_1 + 1 / C_2 + 1 / C_3)$


- Thus the equivalent capacitance is

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



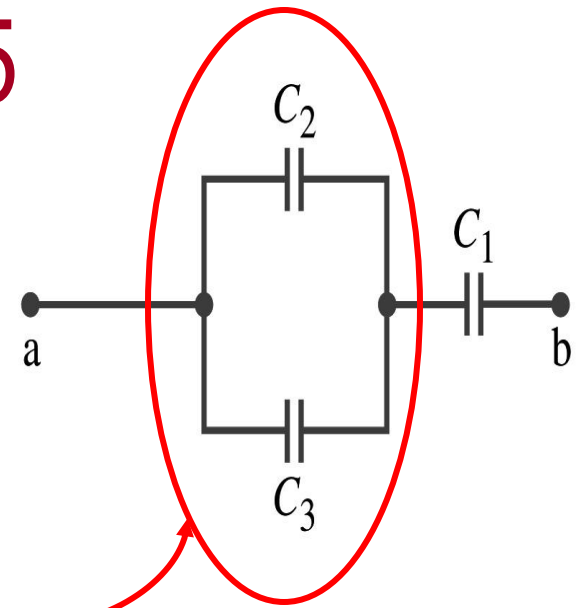Example 24 – 5

Equivalent Capacitor: Determine the capacitance of a single capacitor that will have the same effect as the combination shown in the figure. Take $C_1 = C_2 = C_3 = C$.



We should do these first!!

How? These are in parallel so the equivalent capacitance is:

$$C_{eq} = C_3 + C_2 = 2C$$

Now the equivalent capacitor is in series with C_1 .

$$\frac{1}{C_{eq}} = \frac{1}{C_{eq1}} + \frac{1}{C_2} = \frac{1}{2C} + \frac{1}{C} = \frac{3}{2C} \quad \text{Solve for } C_{eq} \rightarrow C_{eq} = \frac{2C}{3}$$



Electric Energy Storage

- A charged capacitor stores energy.
 - The stored energy is the work done to charge it.
- The net effect of charging a capacitor is removing one type of charge (+ or -) from a plate and moving it to the other plate.
 - Battery does this when it is connected to a capacitor.
- Capacitors do not charge immediately.
 - Initially when the capacitor is uncharged, no work is necessary to move the first bit of charge. Why?
 - Since there is no charge, there is no field that the external work needs to overcome.
 - When some charge is on each plate, it requires work to add more charge due to electric repulsion.



Electric Energy Storage

- What work is needed to add a small amount of charge (dq) when the potential difference across the plates is V ? $dW=Vdq$
- Since $V=q/C$, the work needed to store total charge Q is

$$W = \int_0^Q V dq = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

- Thus, the energy stored in a capacitor when the capacitor carries charges $+Q$ and $-Q$ is

$$U = \frac{Q^2}{2C}$$

- Since $Q=CV$, we can rewrite

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$



Example 24 – 7

Energy store in a capacitor: A camera flash unit stores energy in a $150\mu\text{F}$ capacitor at 200V . How much electric energy can be stored?

Use the formula for stored energy. Umm.. Which one?

What do we know from the problem? C and V

So we use the one with C and V: $U = \frac{1}{2} CV^2$

$$U = \frac{1}{2} CV^2 = \frac{1}{2} 150 \times 10^{-6} \text{ F } 200\text{V}^2 = 3.0\text{J}$$

How do we get J from FV^2 ? $FV^2 = \left(\frac{C}{V}\right)V^2 = CV = C\left(\frac{J}{C}\right) = J$



Electric Energy Density

- The energy stored in a capacitor can be considered as being stored in the electric field between the two plates
- For a uniform field E between two plates, $V=Ed$ and $C=\epsilon_0 A/d$
- Thus the stored energy is

$$U = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) Ed^2 = \frac{1}{2} \epsilon_0 E^2 Ad$$

- Since Ad is the gap volume, we can obtain the energy density, stored energy per unit volume, as

$$u = \frac{1}{2} \epsilon_0 E^2$$

Valid for plates
with a vacuum gap

Electric energy stored per unit volume in any region of space
is proportional to the square of the electric field in that region.



Dielectrics

- Capacitors generally have an insulating sheet of material, called a dielectric, between the plates to
 - Increase the breakdown voltage above that in air
 - Allows the plates get closer together without touching
 - Increases capacitance (recall $C = \epsilon_0 A/d$)
 - Also increases the capacitance by the dielectric constant

$$C = KC_0$$

- Where C_0 is the intrinsic capacitance when the gap is vacuum, and K or κ is the dielectric constant



Dielectrics

- The value of dielectric constant varies depending on material (Table 24 – 1)
 - K for vacuum is 1.0000
 - K for air is 1.0006 (this is why permittivity of air and vacuum are used interchangeably.)
- The maximum electric field before breakdown occurs is the dielectric strength. What is its unit?
 - V/m
- The capacitance of a parallel plate capacitor with a dielectric (K) filling the gap is

$$C = KC_0 = K\epsilon_0 \frac{A}{d}$$



Dielectrics

- A new quantity, the permittivity of dielectric, is defined as $\underline{\varepsilon = K\varepsilon_0}$
- The capacitance of a parallel plate with a dielectric medium filling the gap is

$$C = \varepsilon \frac{A}{d}$$

- The energy density stored in an electric field E in a dielectric is

$$u = \frac{1}{2} K \varepsilon_0 E^2 = \frac{1}{2} \varepsilon E^2$$


Valid for any space with dielectric of permittivity ε .




Effect of a Dielectric Material

- Let's consider the two cases below:

Case #1 :
constant V

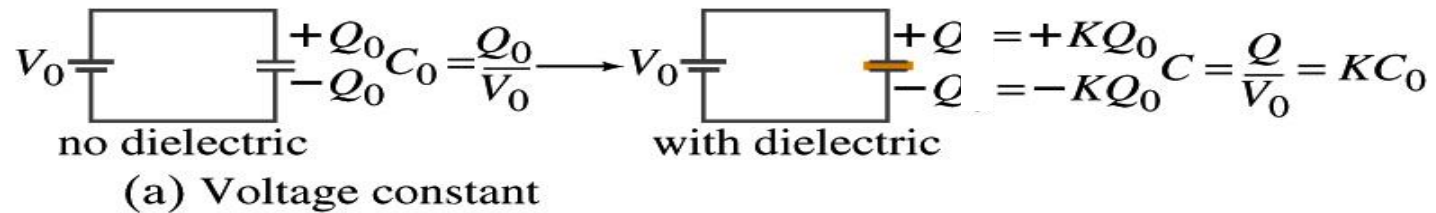

Case #2 :
constant Q

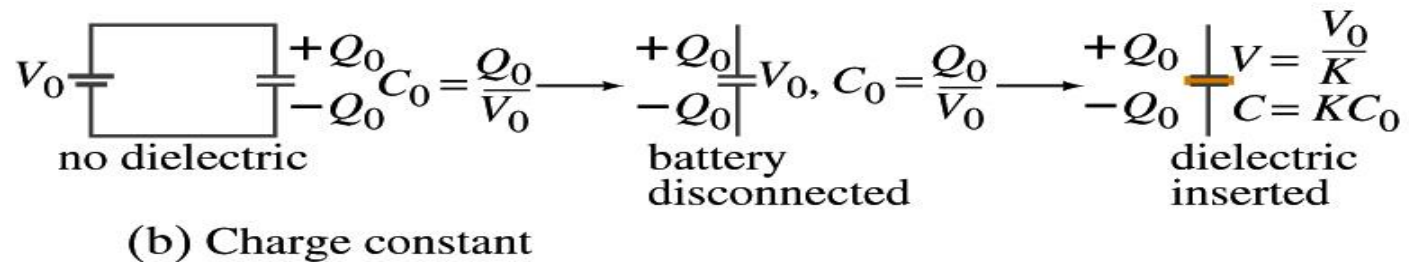

- Constant voltage: Experimentally observed that the total charge on each plate of the capacitor increases by K as the dielectric material is inserted between the gap $\rightarrow Q = KQ_0$
 - The capacitance increased to $C = Q/V_0 = KQ_0/V_0 = KC_0$
- Constant charge: Voltage found to drop by a factor $K \rightarrow V = V_0/K$
 - The capacitance increased to $C = Q_0/V = KQ_0/V_0 = KC_0$