

# PHYS 1444 – Section 003

## Lecture #8

*Monday, Sept. 26, 2005*

*Dr. Jaehoon Yu*

- Capacitors
- Determination of Capacitance
- Capacitors in Series and Parallel
- Electric Energy Storage
- Dielectrics
- Molecular Description of Dielectrics

Today's homework is homework #5, due noon, next Monday!!



# Electrostatic Potential Energy: electron Volt

- What is the unit of electrostatic potential energy?
  - Joules
- Joules is a very large unit in dealing with electrons, atoms or molecules atomic scale problems
- For convenience a new unit, electron volt (eV), is defined
  - 1 eV is defined as the energy acquired by a particle carrying the charge equal to that of an electron ( $q=e$ ) when it moves across a potential difference of 1V.
  - How many Joules is 1 eV then?  $1eV = 1.6 \times 10^{-19} C \cdot 1V = 1.6 \times 10^{-19} J$
- eV however is **not a standard SI unit**. You must convert the energy to Joules for computations.
- What is the speed of an electron with kinetic energy 5000eV?





# Capacitors (or Condensers)

- What is a capacitor?
  - A device that can store electric charge
  - But does not let them flow through
- What does it consist of?
  - Usually consists of two conducting objects (plates or sheets) placed near each other without touching
  - Why can't they touch each other?
    - The charge will neutralize...
- Can you give some examples?
  - Camera flash, UPS, Surge protectors, binary circuits, etc...
- How is a capacitor different than a battery?
  - Battery provides potential difference by storing energy (usually chemical energy) while the capacitor stores charges but very little energy.


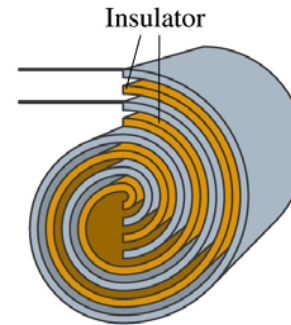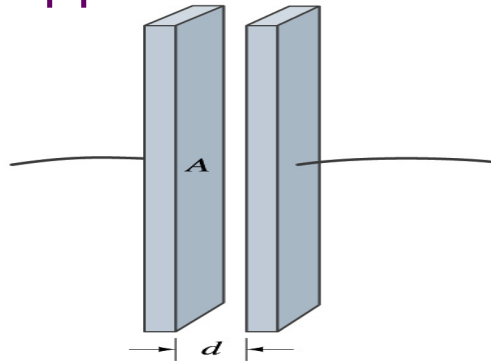
# Capacitors

- A simple capacitor consists of a pair of parallel plates of area  $\mathcal{A}$  separated by a distance  $d$ .
  - A cylindrical capacitors are essentially parallel plates wrapped around as a cylinder.






- How would you draw symbols for a capacitor and a battery?

- Capacitor  $-||-$
- Battery  $(+) -|i- (-)$

Monday, Sept. 26, 2005



PHYS 14  
Dr.

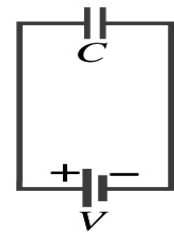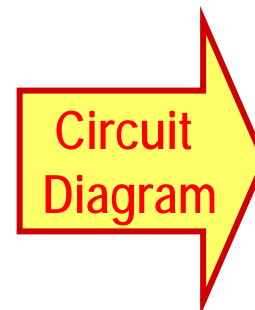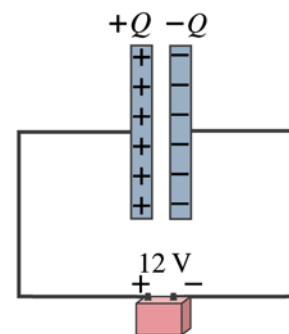

# Capacitors

- What do you think will happen if a battery is connected ( or the voltage is applied) to a capacitor?

- The capacitor gets charged quickly, one plate positive and other negative in equal amount.

- Each battery terminal, the wires and the plates are conductors. What does this mean?

- All conductors are at the same potential. And?
  - So the full battery voltage is applied across the capacitor plates.


- So for a given capacitor, the amount of charge stored in the capacitor is proportional to the potential difference  $V_{ba}$  between the plates. How would you write this formula?

$$Q = CV_{ba}$$

C is a property of a capacitor so does not depend on Q or V.

- C is a proportionality constant, called capacitance of the device.

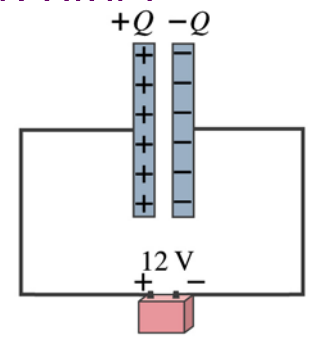- What is the unit? C/V or Farad (F) Normally use  $\mu\text{F}$  or pF.



# Determination of Capacitance


- C can be determined analytically for capacitors w/ simple geometry and air in between.

- Let's consider a parallel plate capacitor.

- Plates have area A each and separated by d.

- d is smaller than the length, and so E is uniform.

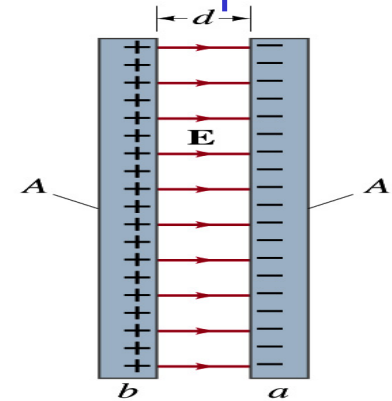- E for parallel plates is  $E = \sigma / \epsilon_0$ ,  $\sigma$  is the surface charge density.



- E and V are related  $V_{ba} = -\int_a^b \vec{E} \cdot d\vec{l}$

- Since we take the integral from lower potential (a) higher potential (b) along the field line, we obtain

- $$V_{ba} = V_b - V_a = -\int_a^b E dl \cos 180^\circ = +\int_a^b E dl = \int_a^b \frac{\sigma}{\epsilon_0} dl = \int_a^b \frac{Q}{\epsilon_0 A} dl = \frac{Q}{\epsilon_0 A} \int_a^b dl = \frac{Q}{\epsilon_0 A} (b - a) = \frac{Qd}{\epsilon_0 A}$$

- So from the formula:

- What do you notice?

$$C = \frac{Q}{V_{ba}} = \frac{Q}{Qd / \epsilon_0 A} = \frac{\epsilon_0 A}{d}$$

C only depends on the area and the distance of the plates and the permittivity of the medium between them.

# Example 24 – 1

**Capacitor calculations:** (a) Calculate the capacitance of a capacitor whose plates are 20cmx3.0cm and are separated by a 1.0mm air gap. (b) What is the charge on each plate if the capacitor is connected to a 12-V battery? (c) What is the electric field between the plates? (d) Estimate the area of the plates needed to achieve a capacitance of 1F, given the same air gap.

(a) Using the formula for a parallel plate capacitor, we obtain

$$C = \frac{\epsilon_0 A}{d} =$$
$$= \left( 8.85 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2 \right) \frac{0.2 \times 0.03 \text{ m}^2}{1 \times 10^{-3} \text{ m}} = 53 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m} = 53 \text{ pF}$$

(b) From  $Q=CV$ , the charge on each plate is

$$Q = CV = \left( 53 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m} \right) (12 \text{ V}) = 6.4 \times 10^{-10} \text{ C} = 640 \text{ pC}$$



# Example 24 – 1

(C) Using the formula for the electric field in two parallel plates

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0} = \frac{6.4 \times 10^{-10} \text{ C}}{6.0 \times 10^{-3} \text{ m}^2 \times 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2} = 1.2 \times 10^4 \text{ N/C} = 1.2 \times 10^4 \text{ V/m}$$

Or, since  $V = Ed$  we can obtain  $E = \frac{V}{d} = \frac{12\text{V}}{1.0 \times 10^{-3} \text{ m}} = 1.2 \times 10^4 \text{ V/m}$

(d) Solving the capacitance formula for A, we obtain

$$C = \frac{\epsilon_0 A}{d}$$

Solve for A

$$A = \frac{Cd}{\epsilon_0} = \frac{1\text{F} \cdot 1 \times 10^{-3} \text{ m}}{(9 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)} \approx 10^8 \text{ m}^2 \approx 100 \text{ km}^2$$


About 40% the area of Arlington (256km<sup>2</sup>).




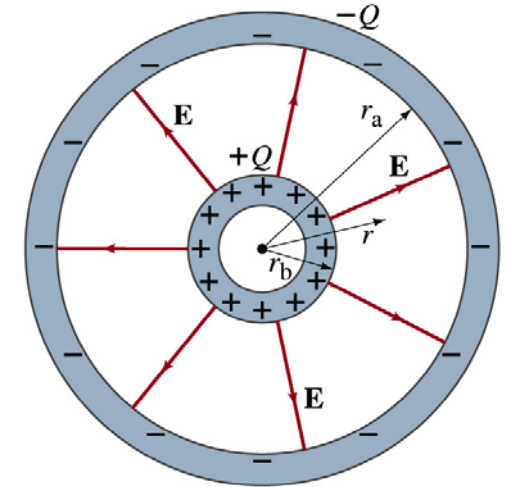
## Example 24 – 3

**Spherical capacitor:** A spherical capacitor consists of two thin concentric spherical conducting shells, of radius  $r_a$  and  $r_b$ , as in the figure. The inner shell carries a uniformly distributed charge  $Q$  on its surface and the outer shell has equal but opposite charge  $-Q$ .



$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

Using Gauss' law, the electric field outside a uniformly charged conducting sphere is

So the potential difference between a and b is

$$\begin{aligned} V_{ba} &= -\int_a^b \vec{E} \cdot d\vec{l} = \\ &= -\int_a^b E \cdot dr = -\int_a^b \frac{Q}{4\pi\epsilon_0 r^2} dr = -\frac{Q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left( \frac{1}{r} \right)_{r_a}^{r_b} = \frac{Q}{4\pi\epsilon_0} \left( \frac{1}{r_b} - \frac{1}{r_a} \right) = \frac{Q}{4\pi\epsilon_0} \left( \frac{r_a - r_b}{r_b r_a} \right) \end{aligned}$$

Thus capacitance is

$$C = \frac{Q}{V} = \frac{Q}{\frac{Q}{4\pi\epsilon_0} \left( \frac{r_a - r_b}{r_b r_a} \right)} = \frac{4\pi\epsilon_0 r_b r_a}{r_a - r_b}$$

# Capacitor Cont'd

- A single isolated conductor can be said to have a capacitance,  $C$ .
- $C$  can still be defined as the ratio of the charge to absolute potential  $V$  on the conductor.
  - So  $Q=CV$ .
- The potential of a single conducting sphere of radius  $r_b$  can be obtained as

$$V = \frac{Q}{4\pi\epsilon_0} \left( \frac{1}{r_b} - \frac{1}{r_a} \right) = \frac{Q}{4\pi\epsilon_0 r_b} \quad \text{where } r_a \rightarrow \infty$$



- So its capacitance is

$$C = \frac{Q}{V} = 4\pi\epsilon_0 r_b$$


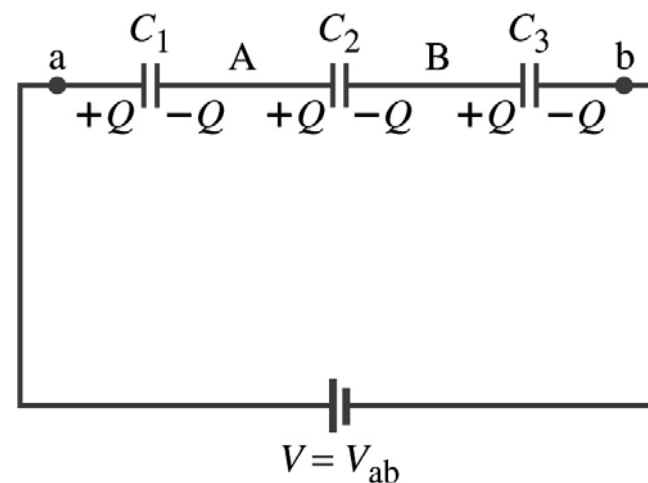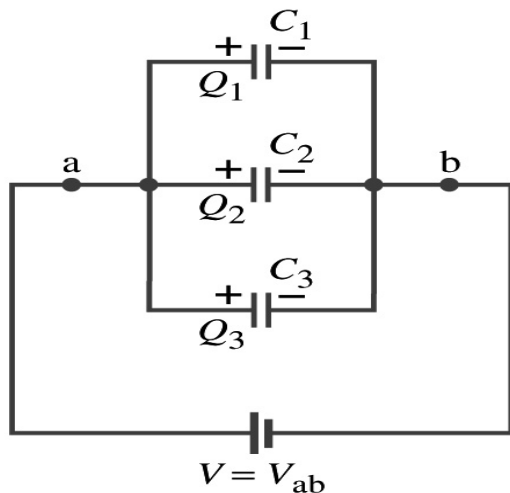
# Capacitors in Series or Parallel

- Capacitors are used in many electric circuits
- What is an electric circuit?
  - A closed path of conductors, usually wires connecting capacitors and other electrical devices, in which
    - charges can flow
    - And includes a voltage source such as a battery
- Capacitors can be connected in various ways.
  - In parallel
  - and
  - in Series
  - or in combination




# Capacitors in Parallel

- Parallel arrangement provides the same voltage across all the capacitors.

- Left hand plates are at  $V_a$  and right hand plates are at  $V_b$
- So each capacitor plate acquires charges given by the formula

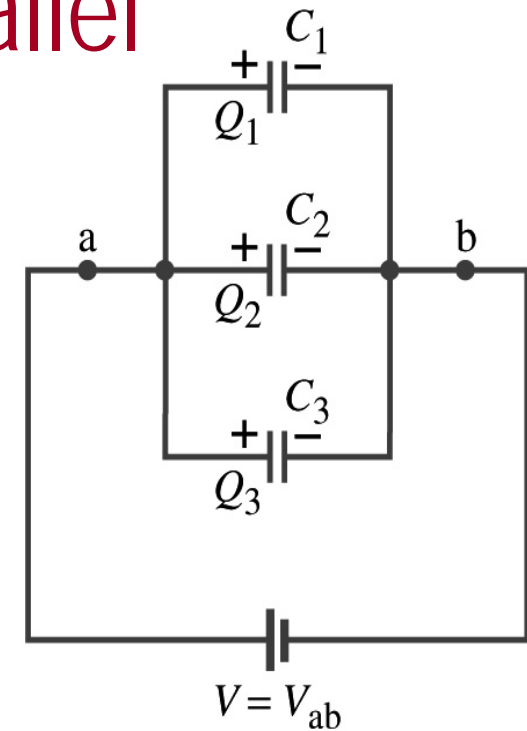- $Q_1 = C_1 V$ ,  $Q_2 = C_2 V$ , and  $Q_3 = C_3 V$




- The total charge  $Q$  that must leave battery is then
  - $Q = Q_1 + Q_2 + Q_3 = V(C_1 + C_2 + C_3)$
- Consider that the three capacitors behave like an equivalent one
  - $Q = C_{eq} V = V(C_1 + C_2 + C_3)$
- Thus the equivalent capacitance in parallel is  $C_{eq} = C_1 + C_2 + C_3$

M What is the net effect?

P The capacitance increases!!!
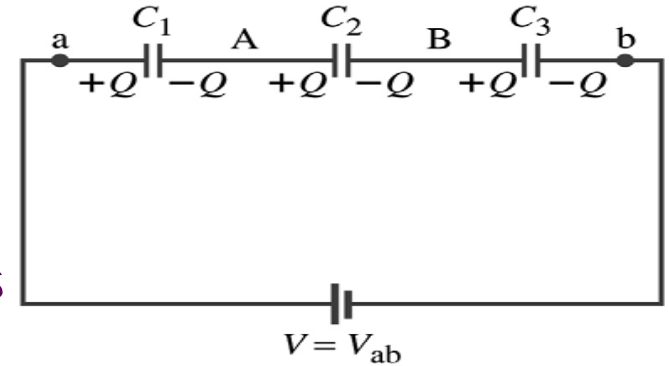
# Capacitors in Series

- Series arrangement is more interesting
  - When battery is connected,  $+Q$  flows to the left plate of  $C_1$  and  $-Q$  flows to the right plate of  $C_3$ .
  - Since the in between were originally neutral, charges get induced to neutralize the ones in the middle.
  - So the charge on each capacitor is the same value,  $Q$ . (Same charge)
- Consider that the three capacitors behave like an equivalent one
  - $Q = C_{eq} V$
- The total voltage  $V$  across the three capacitors in series must be equal to the sum of the voltages across each capacitor.
  - $V = V_1 + V_2 + V_3 = Q/C_1 + Q/C_2 + Q/C_3$
- Putting all these together, we obtain:
- $V = Q/C_{eq} = Q(1/C_1 + 1/C_2 + 1/C_3)$
- Thus the equivalent capacitance is



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


What is the net effect?



The capacitance smaller than the smallest  $C$ !!!
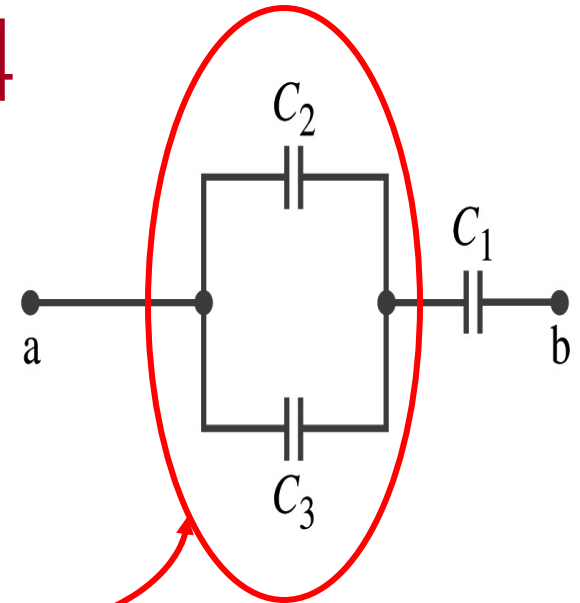
## Example 24 – 4

**Equivalent Capacitor:** Determine the capacitance of a single capacitor that will have the same effect as the combination shown in the figure. Take  $C_1 = C_2 = C_3 = C$ .



We should do these first!!

How? These are in parallel so the equivalent capacitance is:

$$C_{eq1} = C_1 + C_2 = 2C$$

Now the equivalent capacitor is in series with  $C_1$ .

$$\frac{1}{C_{eq}} = \frac{1}{C_{eq1}} + \frac{1}{C_2} = \frac{1}{2C} + \frac{1}{C} = \frac{3}{2C} \quad \text{Solve for } C_{eq} \rightarrow C_{eq} = \frac{2C}{3}$$

# Electric Energy Storage

- A charged capacitor stores energy.
  - The stored energy is the work done to charge it.
- The net effect of charging a capacitor is removing one type of charge from a plate and put them on to the other.
  - Battery does this when it is connected to a capacitor.
- Capacitors does not charge immediately.
  - Initially when the capacitor is uncharged, no work is necessary to move the first bit of charge. Why?
    - Since there is no charge, there is no field that the external work needs to overcome.
  - When some charge is on each plate, it requires work to add more charge due to electric repulsion.



# Electric Energy Storage

- The work needed to add a small amount of charge,  $dq$ , when a potential difference across the plate is  $V$ :  $dW=Vdq$ .
- Since  $V=q/C$ , the work needed to store total charge  $Q$  is

$$W = \int_0^Q V dq = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

- Thus, the energy stored in a capacitor when the capacitor carries charges  $+Q$  and  $-Q$  is

$$U = \frac{Q^2}{2C}$$

- Since  $Q=CV$ , we can rewrite

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$





## Example 24 – 7

**Energy store in a capacitor:** A camera flash unit stores energy in a  $150\mu\text{F}$  capacitor at  $200\text{V}$ . How much electric energy can be stored?

Using the formula for stored energy.      Umm.. Which one?

What do we know from the problem?      C and V

So we use the one with C and V:  $U = \frac{1}{2}CV^2$

$$U = \frac{1}{2}CV^2 = \frac{1}{2}(150 \times 10^{-6} \text{ F})(200\text{V})^2 = 3.0\text{J}$$

How do we get J from  $FV^2$ ?  $FV^2 = \left(\frac{C}{V}\right)V^2 = CV = C\left(\frac{J}{C}\right) = J$

