

# PHYS 1444 – Section 003

## Lecture #13

*Monday, Oct. 17, 2005*

*Dr. Jaehoon Yu*

- RC Circuits
- RC time
- Exam Problem Solutions

Today's homework is homework #7, due noon, next Tuesday!!




# Announcements

- How was the exam?
  - Do you want to know how you did?
  - I am sure you do... Right?
  - OK enough teasing around...
  - Here goes the average
    - 52.5
  - The top score: 85
- Reading Assignments
  - CH26 – 5
  - CH26 – 6


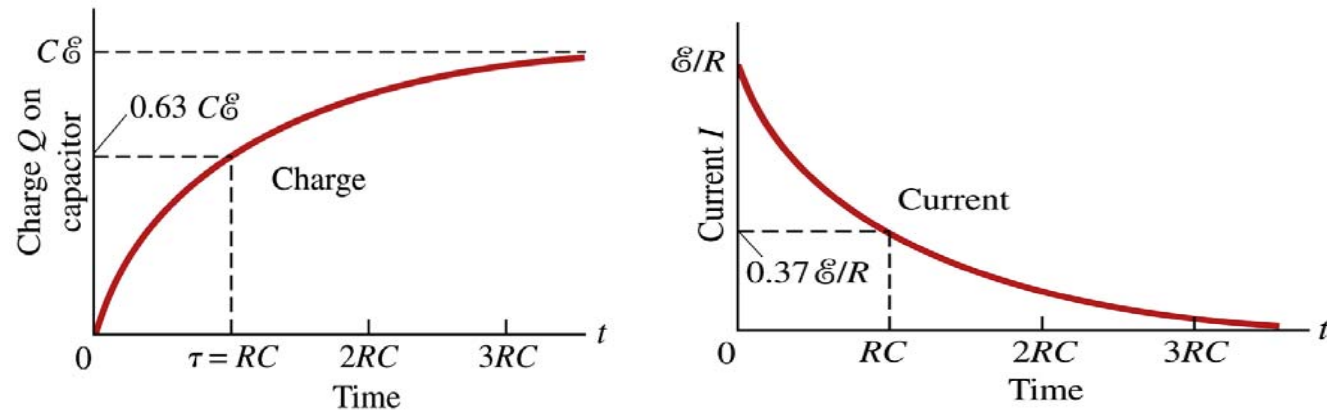
# RC Circuits

- How does all this look like in graphs?
  - Charge and the current on the capacitor as a function of time



- From energy conservation (Kirchhoff's 2<sup>nd</sup> rule), the emf  $\mathcal{E}$  must be equal to the voltage drop across the capacitor and the resistor
  - $\mathcal{E} = IR + Q/C$
  - R includes all resistance in the circuit, including the internal resistance of the battery, I is the current in the circuit at any instant, and Q is the charge of the capacitor at that same instance.

# Analysis of RC Circuits

- From the energy conservation, we obtain  $\varepsilon = IR + Q/C$
- Which ones are constant in the above equation?
  - $\varepsilon$ ,  $R$  and  $C$  are constant
  - $Q$  and  $I$  are functions of time
- How do we write the rate at which the charge accumulated on the capacitor?
  - We can rewrite the above equation as  $\varepsilon = R \frac{dQ}{dt} + \frac{1}{C} Q$
  - This equation can be solved by rearranging the terms as  $\frac{dQ}{C\varepsilon - Q} = \frac{dt}{RC}$



# Analysis of RC Circuits

- Now integrating from  $t=0$  when there was no charge on the capacitor to  $t$  when the capacitor is fully charged, we obtain

- $$\int_0^Q \frac{dQ}{C\mathcal{E} - Q} = \frac{1}{RC} \int_0^t dt \quad \rightarrow$$

- $$-\ln(C\mathcal{E} - Q)\Big|_0^Q = -\ln(C\mathcal{E} - Q) - (-\ln C\mathcal{E}) = \frac{t}{RC}\Big|_0^t = \frac{t}{RC}$$

- So, we obtain  $\ln\left(1 - \frac{Q}{C\mathcal{E}}\right) = -\frac{t}{RC} \quad \rightarrow \quad 1 - \frac{Q}{C\mathcal{E}} = e^{-t/RC}$

- Or  $Q = C\mathcal{E}(1 - e^{-t/RC})$

- The potential difference across the capacitor is  $V=Q/C$ , so  $V_C = \mathcal{E}(1 - e^{-t/RC})$



# Analysis of RC Circuits

- Since  $Q = C\varepsilon(1 - e^{-t/RC})$  and  $V_C = \varepsilon(1 - e^{-t/RC})$
- What can we see from the above equations?
  - $Q$  and  $V_C$  increase from 0 at  $t=0$  to maximum value  $Q_{\max}=C\varepsilon$  and  $V_C=\varepsilon$ .
- In how much time?
  - The quantity  $RC$  is called the time constant,  $\tau$ , of the circuit
    - $\tau=RC$ , What is the unit? **Sec.**
  - What is the physical meaning?
    - The time required for the capacitor to reach  $(1-e^{-1})=0.63$  or 63% of the full charge
- The current is  $I = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$

